

Homework #1

1. It is required to design a voltage amplifier to be driven from a signal source having a 10mV peak amplitude and a source resistance of  $10k\Omega$  to supply a peak output of 3V across a  $1k\Omega$  load.

(a) What is the required voltage gain from the source to the load?

(a) Required voltage gain  $= \frac{v_0}{v_5} = \frac{3 \text{ V}}{0.01 \text{ V}} = 300 \text{ V}/\text{V}$ 

(b) If the peak current available from the source is  $0.1\mu A$ , what is the smallest input resistance allowed? For the design with this value  $R_i$ , find the overall current gain and power gain.

(b) The smallest  $R_i$  allowed is obtained from  $0.1 \ \mu A = \frac{10 \text{ mV}}{R_s + R_i} \Rightarrow R_s + R_i = 100 \text{ k}\Omega$ Thus  $R_i = 90 \text{ k}\Omega$ . For  $R_i = 90 \text{ k}\Omega$ .  $i_i = 0.1 \ \mu A$  peak, and

Overall current gain =  $\frac{v_0 / R_L}{i_i} = \frac{3 \text{ mA}}{0.1 \text{ mA}} = 3 \times 10^4 \text{ A} / \text{A}$ Overall power gain =  $\frac{v_{orms}^2 / R_L}{v_{s(rms)} \times i_{i(rms)}}$ =  $\frac{\left(\frac{3}{\sqrt{2}}\right)^2 / 1000}{\left(\frac{10 \times 10^{-3}}{\sqrt{2}}\right) \times \left(\frac{0.1 \times 10^{-6}}{\sqrt{2}}\right)}$ 

 $= 9 \times 10^6 \,\mathrm{W/W}$ 

(c) If the amplifier power supply limits the peak value of the output open-circuit voltage to 5V, what is the largest output resistance allowed?

The voltage across Ro will be 5-3V = 2V. The current through RL and thus also Ro is 3V/1k=3mA so Ro= $2/3mA=667\Omega$ 

(d) For the design with  $R_i$  as in (b) and  $R_o$  as in (c), what is the required value of open-circuit voltage gain (ie, Vo/Vi as RL goes to  $\infty$ ) of the amplifier.



2. An amplifier with an input resistance of  $10k\Omega$ , when driven by a current source of  $1\mu$ A and a source resistance of  $100k\Omega$ , has a short-circuit output current of 10mA and an open-circuit output voltage of 10V. The device is driving a  $4k\Omega$  load. Give the values of the voltage gain, current gain, and power gain expressed as ratios and in decibels?



3. A voltage amplifier with an input resistance of  $10k\Omega$ , and output resistance of  $200\Omega$ , and a gain of 1000 V/V is connected to an input source with a  $100k\Omega$  resistance. It also has an opencircuit voltage of 10mV and a  $100\Omega$  load. For this situation:

(a) What output voltage results?

(b) What is the voltage gain from source to load?

(c) What is the voltage gain from the amplifier input to the load?

(d) If the output voltage across the load is twice that needed and there are signs of internal amplifier overload, suggest the location and value of a single resistor that would produce the desired output. Choose an arrangement that would cause minimum disruption to an operating circuit (*Hint:* Use parallel rather that series connections.)





(b) 
$$\frac{v_o}{v_s} = \frac{303 \text{ mV}}{10 \text{ mV}} = 30.3 \text{ V/V}$$
  
(c)  $\frac{v_o}{v_i} = 1000 \times \frac{100}{100 + 200} = 333.3 \text{ V/V}$   
(d)  
 $R_i$   
 $R_p \neq R_i \neq \cdots$ 

Connect a resistance  $R_P$  in parallel with the input and select its value from

$$\frac{(R_P \parallel R_i)}{(R_P \parallel R_i) + R_S} = \frac{1}{2} \frac{R_i}{R_i + R_S}$$
$$\Rightarrow 1 + \frac{R_S}{R_P \parallel R_i} = 22 \Rightarrow R_P \parallel R_i = \frac{R_S}{21} = \frac{1}{21}$$
$$\Rightarrow \frac{1}{R_P} + \frac{1}{R_i} = \frac{21}{100}$$
$$R_P = \frac{1}{0.21 - 0.1} = 9.1 \text{ k}\Omega$$

4. For the circuit below:

- (a) Find the resistances looking into node 1, R<sub>1</sub>; node 2, R<sub>2</sub>; node 3, R<sub>3</sub>; and node 4, R<sub>4</sub>.
- (b) Find the currents  $I_1$ ,  $I_2$ ,  $I_3$ , and  $I_4$  in terms of the input current I.
- (c) Find the voltage at nodes 1,2,3, and 4, that is  $V_1$ ,  $V_2$ ,  $V_3$ , and  $V_4$  in terms of IR.





c) 
$$v_1 = I_1 R = -IR$$
  
 $v_2 = -I_2 R = -2IR$   
 $v_3 = -I_3 R = -4IR$   
 $v_4 = -I_3 R + I_4 \frac{R}{2} = -4IR - 8I\frac{R}{2} = -8IR$ 

5. A particular enhancement MOSFET for which  $V_t=0.5V$  and  $k_n'(W/L)=0.1mA/V^2$  is to be operated in the saturation region. If  $i_D$  is to be 12.5µA, find the required  $V_{GS}$  and the minimum required  $V_{DS}$ , Repeat for  $i_D=50\mu$ A.

$$V_{tn} = 0.5 \text{ V} \quad k_n \frac{W}{L} = 0.1 \text{ mA/V}^2 \quad \begin{array}{l} \text{Saturation mode} & \text{for } i_D = 12.5 \text{ } \mu\text{A} \\ v_{DS} \ge (v_{GS} - V_{tn}) & v_{GS} = 1.0 \text{ V} \text{ and } v_{DS} \ge 0.5 \text{ V} \end{array}$$

$$for i_D = 50 \text{ } \mu\text{A} \\ v_{GS} = 1.5 \text{ V}, \text{ and } v_{DS} \ge 1.0 \text{ V}$$

6. Calculate the overall voltage gain of a CS amplifier fed with a 1M $\Omega$  source and connected to a 20k $\Omega$  load. The MOSFET has  $g_m$ =2mA/V and  $r_o$ =50k $\Omega$ , and a drain resistance  $R_D$ =10k $\Omega$  is utilized.

$$G_{v} = -\left(\frac{R_{G}}{R_{G} + R_{sig}}\right)g_{m}(r_{O}||R_{D}||R_{L})$$
SMALL SIGNAL MODEL
$$\int_{\mathbf{R}_{sig}=1M\Omega} f_{sig} + g_{gi} + g_{$$

If RG>>1Mohm, then Rsig can be neglected, and GV=-11.76 otherwise the gain if smaller.



7. A single measurement indicates the emitter voltage of the transistor in the circuit below to be 1.2V. Under the assumption that  $|V_{BE}|=0.7V$ , what are  $V_B$ ,  $I_B$ ,  $I_E$ ,  $I_C$ ,  $V_C$ ,  $\beta$  and  $\alpha$ ?



8. Two identical CE amplifiers are connected in cascade. The first stage is fed with a source *Vsig* having a resistance *Rsig*=10k $\Omega$ . A load resistance R<sub>L</sub>=10k $\Omega$  is connected to the collector of the second stage. Each BJT is biased at I<sub>c</sub>=0.25mA and has  $\beta$ =100 and a very large V<sub>A</sub>. Each stage utilizes a collector resistance R<sub>c</sub>=10k $\Omega$ .

(a) Sketch the equivalent circuit of the two-stage amplifier.

- (b) Calculate the voltage transmission from the signal source to the input of the first stage.
- (c) Calculate the voltage gain of the first stage,  $A_{V1}$ .
- (d) Calculate the voltage gain of the second stage,  $A_{V2}$ .
- (e) Find the overall voltage gain,  $V_{o2}/Vsig$ .



b) Voltage transfer from sig to first stage input  $v_{i1} / v_{sig} = \frac{r_{\pi 1}}{r_{\pi 1} + R_{sig}}$ Given  $I_c = 0.25 \text{ mA}; \beta = 100; V_A \rightarrow \infty;$   $R_c = 10 \text{ k}\Omega; R_{sig} = 10 \text{ k}\Omega$   $g_m = \frac{I_C}{V_T}, \quad r_\pi = \frac{\beta}{g_m} = \frac{\beta}{I_C} V_T$   $r_\pi = \frac{100}{0.25 \times 10^{-3}} (0.015) = 10 \text{ k}\Omega$   $v_{i1} / v_{sig} = \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 10 \text{ k}\Omega} = 1/2$   $c) A_{v1} = v_{i2} / v_{i1} = -g_m (R_{c1} || r_{\pi 2})$ Since  $r_\pi = v_{i2} \otimes R_c = R_{c1} = R_{c2} = 10 \text{ k}\Omega$   $A_{v1} = -\frac{I_c}{V_T} (10 \text{ k}\Omega || 10 \text{ k}\Omega)$   $= -\frac{0.25 \times 10^{-3}}{0.025} (5 \text{ k}\Omega) = -50$   $d) A_{v2} = v_0 / v_{i2} = -g_m \times (R_{c2} || R_L)$   $= -\frac{I_C}{V_T} (R_{c2} || R_L) = \frac{0.25 \times 10^{-3}}{0.025} (5 \text{ k}\Omega)$  = -50  $e) G_V = v_0 / v_{sig} = \frac{v_{i1}}{v_{sig}} \times \frac{v_{i2}}{v_{i3}} \times \frac{v_0}{v_{i2}}$  $= (0, 5)(-50)(-50) = G_V = -1250$ 



9. For the circuits below, find values for the labeled node voltages and branch currents. Assume  $\beta$  to be very high.



Fall 2010



## Homework #1

10. It is required to bias the transistor in the circuit to the right at  $I_c=1$ mA. The transistor is specified to be nominally 100, but it can fall in the range of 50 to 150. For  $V_{cc}=+3V$  and  $R_c=2k\Omega$ , find the required value of  $R_B$  to achieve  $I_c=1$ mA for the "nominal" transistor. What is the expected range for  $I_c$  and  $V_{CE}$ ? Comment on the efficacy of this bias design.

