

ECE 6130 Cross Talk


Portfolio:

What is cross talk? What causes it? How do you maximize, minimize it?


Given a pair of coupled lines, what signals do you receive from the forward and reverse cross talk?

Read Chapter 5 in Black Magic textbook.

CROSS TALK

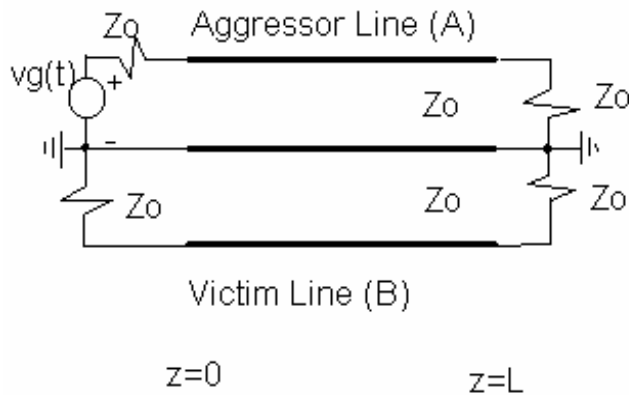

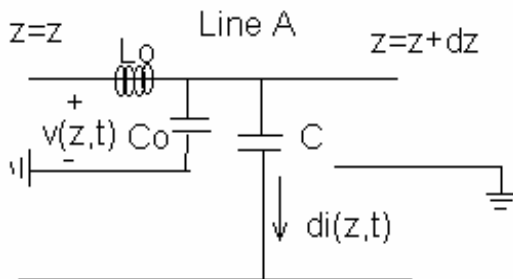
Examine effect of capacitive coupling on a small segment of line (dz) starting at z .



From capacitor equation:

$$di(z,t) = (C) (dz) (dv(z,t) / dt)$$

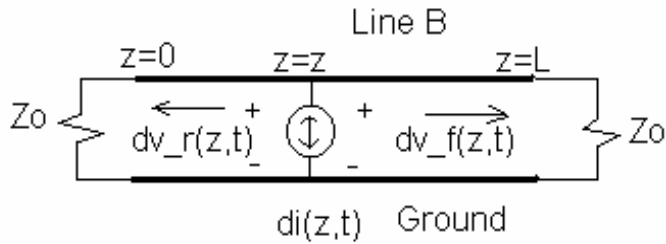This differential cross talk current feeds the victim line. We can model the current as either direction.




Differential Forward Voltage:

$$dv_f(z,t) = (di(z,t)/2)(Zo) = (C)(dz)(dv(z,t)/dt)(Zo)/2$$

Differential Reverse Voltage:


$$dv_r(z,t) = dv_f(z,t)$$

Analysis of Inductive Coupling:

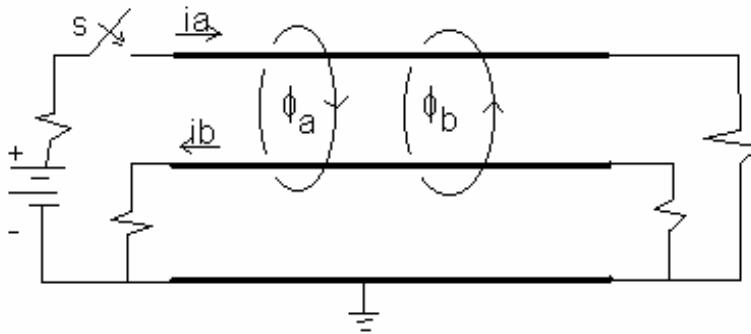


Lenz's Law:

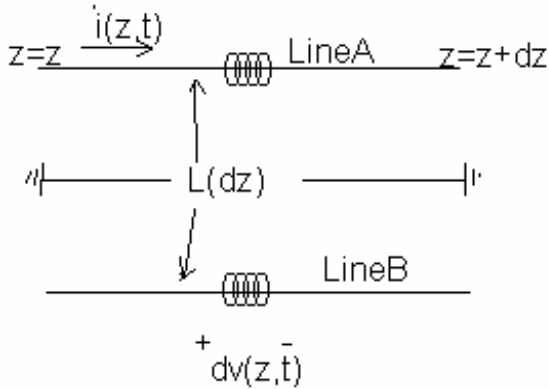- (1) When the switch is closed, a transient (changing) current i_a appears on line A.
- (2) This induces a changing magnetic flux density, ϕ_a around line A.
- (3) Flux ϕ_a also wraps around (couples to) line B.
- (4) Lenz Law states that line B will try to oppose the CHANGE in ϕ_a . So, Line B produces a current i_b in the opposite direction.
- (5) Current i_b creates an opposing magnetic flux ϕ_b .
- (6) After the transient has died away flux ϕ_b will be gone.



$$dv(z,t) = L (dz) (di(z,t) / dt)$$

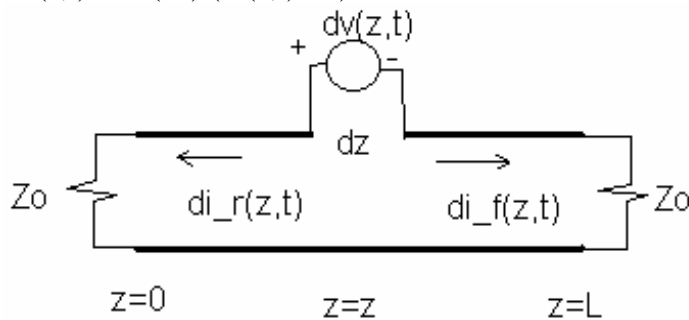

Differential Forward Current:

$$di_f(z,t) = (L) (dz) (di(z,t)/dt) / (2 Zo)$$

Differential Reverse Current:

$$di_r(z,t) = - di_f(z,t)$$

Differential Forward Voltage:

$$dv_f(z,t) = -(Zo) di_f(z,t) = -(L) (dz) (di(z,t)/dt) / 2$$

Differential Reverse Voltage:

$$dv_r(z,t) = - dv_f(z,t) = (L) (dz) (di(z,t)/dt) / 2$$

Add components from Inductive and Capacitive Coupling:

$$dv_f(z,t) = (C Zo - L / Zo) (dv(z,t) / dt) (dz) / 2$$

$$dv_r(z,t) = (C Zo + L / Zo) (dv(z,t) / dt) (dz) / 2$$

Cross talk Coefficients::

$$K_f = (C Zo - L / Zo) / 2 \quad (\text{seconds/meter})$$

$$K_r = v_p (C Zo + L / Zo) / 4 \quad (\text{dimensionless})$$

Forward Cross Talk Equation:

Assume voltage starts at $z=0$ at time $t=0$. It propagates down the line to $z=z$ at time $t=t + dt$, where $dt = z/v_p$

$$dv_f(z,t) = (K_f) (dv(t - dt) / dt) (dz)$$

$$= (K_f) (dv(z, t - z/v_p) / dt) (dz)$$

This cross talk voltage will propagate down the line to an observer located at z_0 . It is then given by:

$$\begin{aligned} dv_f(z_0, t) &= (K_f) (dv(t - z/v_p - (z_0 - z)/ v_p) / dt) (dz) \\ &= (K_f) (dv(t - z_0 / v_p) / dt) (dz) \end{aligned}$$

In the limit as (dz) goes to zero:

$$v_f(z_0, t) = (K_f) \int (0 \text{ to } z_0) (dv(t - z_0 / v_p) / dt) (dz)$$

Integrand is not a function of dz , so:

$$V_f(z_0, t) = (K_f) (z) (dv(t - z_0 / v_p) / dt)$$

Reverse Cross Talk Equation:

$$dv_r(z, t) = (2/ v_p) (K_r) (dv(t - z / v_p) / dt) (dz)$$

Wave travels to the left to z_0 .

$$\begin{aligned} dv_r(z, t) &= (2/ v_p) (K_r) (dv(t - z / v_p - (z - z_0)/ v_p) / dt) (dz) \\ &= (2/ v_p) (K_r) (dv(t + (z_0 - 2z)/ v_p) / dt) (dz) \end{aligned}$$

In the limit as (dz) goes to zero:

$$\begin{aligned} v_r(z, t) &= (2/ v_p) (K_r) \int (z_0 \text{ to } L) (dv(t + (z_0 - 2z)/ v_p) / dt) (dz) \\ &= -K_r v(t + (z_0 - 2z)/ v_p) \text{ from } z \text{ to } L \end{aligned}$$

$$v_r(z, t) = (K_r) [v(t - z/ v_p) - v(t - 2T + z/ v_p)]$$