

ECE 6130 Impedance and Admittance Matrices and S-Parameters

Text Sections: 4.2, 4.3

Describe Z and S matrices, how to compute them, and how to convert between them.
See for example Chapter 4, Problems 7,9

Impedance Matrix:

DRAW an N-port network.

Impedance matrix is used to model V and I relations for all ports.

$$Z_{ij} = V_i / I_j \text{ with } I_k = 0 \text{ for } k \neq j$$

- 1) Open all other ports except j
- 2) Drive port j with current I_j
- 3) Read V_i
- 4) Compute Z_{ij}

$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & \cdots & Z_{1N} \\ Z_{21} & \ddots & & \\ \vdots & & \ddots & \\ Z_{N1} & Z_{N2} & \cdots & Z_{NN} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix}$$

OR: $\mathbf{V} = \mathbf{Z} \mathbf{I}$

Admittance Matrix:

$$\mathbf{I} = \mathbf{Y} \mathbf{V}$$

$$\mathbf{Y} = \mathbf{Z}^{-1} \quad (\text{matrices are inverses of each other})$$

Reciprocal Network:

$$Z_{ij} = Z_{ji}$$


Examples of reciprocal networks: any R,L,C network

Examples of non-reciprocal networks: transistors, amplifiers, attenuators

Lossless Network:

Real (Z_{ij}) = 0 $\ll Z_{ij}$ is strictly imaginary (change of phase, but no attenuation)

EXAMPLE: T-Network

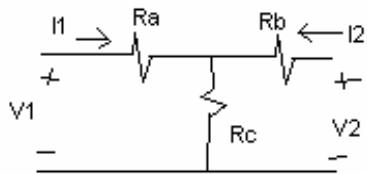

Find Z_{11} :

$$I2 = 0; V1 = I1 (Ra + Rc); Z_{11} = V1 / I1 = Ra + Rc$$

Find Z_{12} :

$$I1=0; V2 = I2 (Zb + Zc); V1 = V2 - Zc / (Zb+Zc); Z_{12} = V1 / I2 = Zc$$

Find Z_{21} :

$$I2 = 0; V1 = I1 (Za + Zc); V2 = V1 Zc / (Za+Zc); Z_{21} = V2 / I1 = Zc = Z_{12}$$

Find Z_{22} :

$$I1 = 0; V2 = I2 (Zb+Zc); Z_{22} = V2 / I2 = Zb + Zc$$

Scattering Matrix (S-parameters)


$$\begin{bmatrix} V_1^- \\ V_2^- \\ \vdots \\ V_N^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \cdots & S_{1N} \\ S_{21} & \ddots & & \\ \vdots & & \ddots & \\ S_{N1} & S_{N2} & \cdots & S_{NN} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \\ \vdots \\ V_N^+ \end{bmatrix}$$

Where

$$S_{ij} = V_i^- / V_j^+ \text{ when } V_k^+ = 0 \text{ for } k \neq j$$

- 1) Terminate all ports except j with matched load.
- 2) Drive port j with V_j^+
- 3) Measure reflected voltage V_i^- on port i.

EXAMPLE: 3dB attenuator

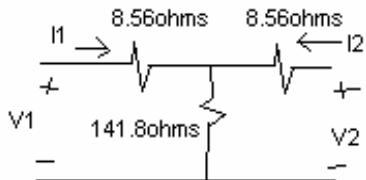

Find S_{11} :

$$Z2 = 50 \text{ ohms}; Zin(\text{port 1}) = 8.56 + (141.8 \parallel (8.56 + 50)) = 50 \text{ ohms}$$

$V1^- = 0$ (no reflection)

$$S_{11} = V1^- / V1^+ = 0$$

Find S₂₂:

Circuit is symmetric.

$$S_{22} = S_{11}$$

Find S₁₂: