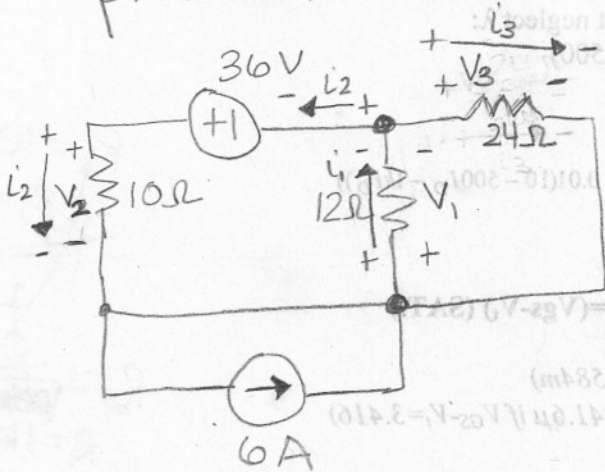


problem (Review) pg. 56



Step 1. Label all V's and I's in every R.

Step 2a: Ohm's Law's

$$V_1 = i_1 (12)$$

$$V_2 = i_2 (10)$$

$$V_3 = i_3 (24)$$

2b. V-loops:

2c. $\sum I$:

Sub in
Ohm's Law's

$$+V_2 - 36 + V_1 = 0$$

$$\rightarrow i_2 (10) - 36 + i_1 (12) = 0$$

$$+V_2 - 36 - V_3 = 0$$

$$\rightarrow i_2 (10) - 36 - i_3 (24) = 0$$

$$-V_1 - V_3 = 0$$

$$V_1 = -V_3$$

$$i_1 (12) = i_3 (24)$$

$$i_1 = 2i_3$$

$$+i_2 - i_1 + i_3 = 0$$

$$i_2 + 2i_3 + i_3 = 0$$

$$i_2 = -3i_3$$

(plug in)

$$-3i_3 (10) - 36 - 24i_3 = 0$$

$$-30i_3 - 36 - 24i_3 = 0$$


$$i_3 = -\frac{36}{54} = -\frac{2}{3} \text{ A}$$

$$\therefore V_1 = i_1 (12) = -2 \left(-\frac{2}{3}\right) (12) = +4(4) = \boxed{+16 \text{ V}}$$

Review Page 56 of notes - Solution

1. a. (5 points)

Calculate v_1 .

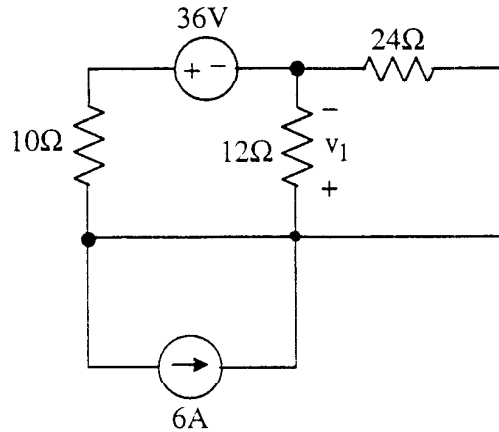


sol'n: The 6A source across the wire may be ignored. Its current flows through the wire but produces no V-drop. Without the 6A src we have a V-divider:


b. (5 points) $v_1 = 36V \cdot 12\Omega \parallel 24\Omega / 12\Omega \parallel 24\Omega + 10\Omega = 36V \cdot 8\Omega / 18\Omega = 16V$

$$v_1 = 16V$$

Calculate i_1 .

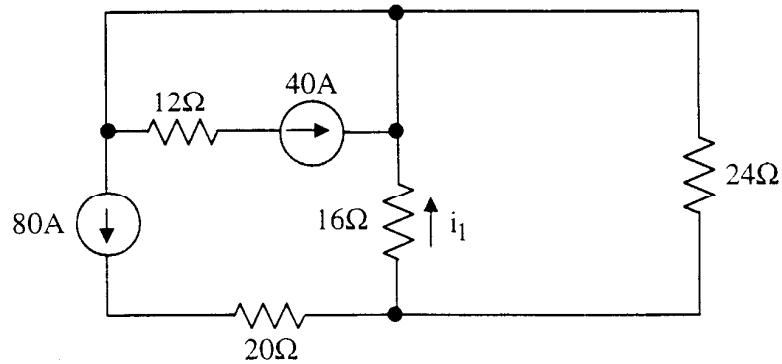

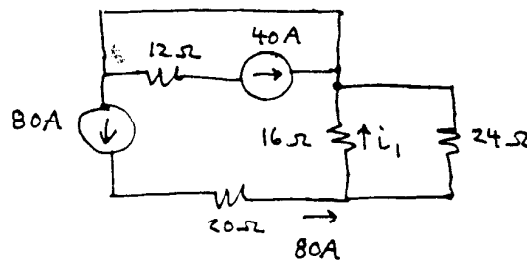sol'n: If we redraw the circuit, we see a current divider:




$$i_1 = 80A \cdot \frac{24\Omega}{16 + 24\Omega} = 80A \cdot \frac{24\Omega}{40\Omega}$$


$$i_1 = 48A$$

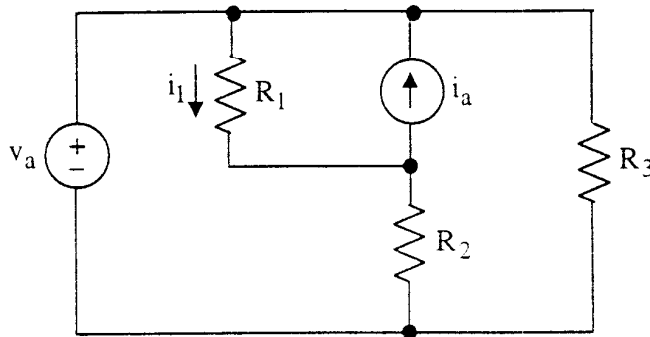2. (30 points)

Derive an expression for i_1 . The expression must not contain more than the circuit parameters v_a , i_a , R_1 , R_2 , and R_3 .



sol'n: Redraw with top as one node:

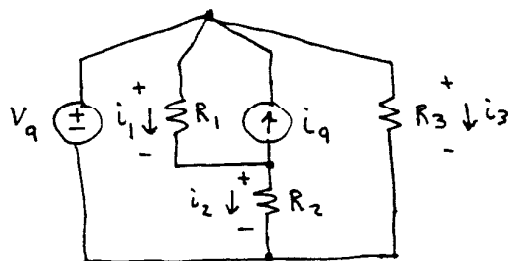

current sum at top or bottom node? No, because we would have to define a current for source V_a .

$$\text{Current at center node: } i_a - i_1 + i_2 = 0A$$

$$V\text{-loop around left inner loop: } v_a - i_1 R_1 - i_2 R_2 = 0V$$

No V -loop for other inner loops because we would have to define V -drop for i_a .

$$\text{Next larger loop is } R_1, R_2, R_3: i_2 R_2 + i_1 R_1 - i_3 R_3 = 0V$$


Now we have 3 eqns in 3 unknowns, and we want to find i_1 . We observe, however, that the first two eqns have only two unknowns. So we don't actually need the 3rd eqn. Use 1st eq'n to find $i_2 = i_1 - i_a$.

$$\text{Substitute into 2nd eq'n: } v_a - i_1 R_1 - (i_1 - i_a) R_2 = 0V$$

$$\text{or } i_1 (-R_1 - R_2) = -v_a - i_a R_2 \quad \text{or} \quad \boxed{i_1 = \frac{v_a + i_a R_2}{R_1 + R_2}}$$


3. (30 points)

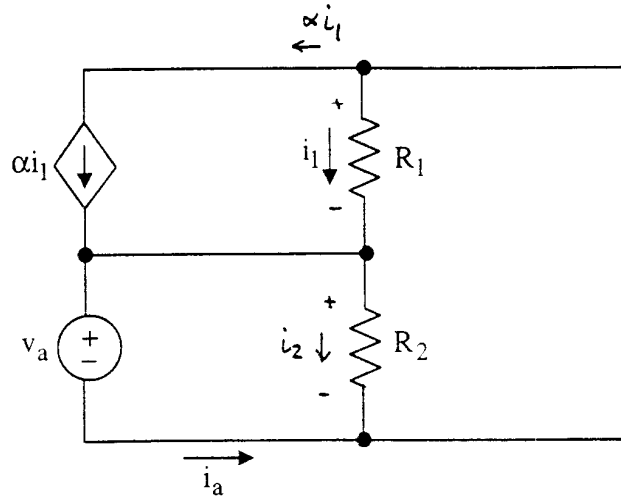- a. Derive an expression for i_a . The expression must not contain more than the circuit parameters α , v_a , R_1 , and R_2 .



- b. Make at least one consistency check (other than a units check) on your expression. Explain the consistency check clearly.

sol'n: a) Redraw circuit

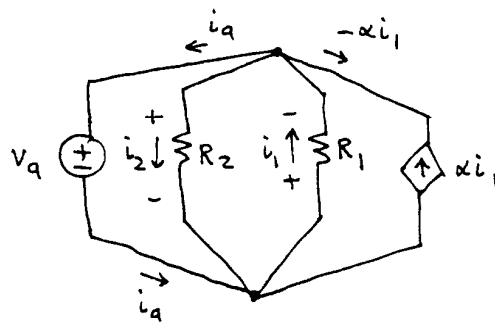

No current sums at nodes because of v_a .

$$V\text{-loop on left: } v_a - i_2 R_2 = 0V \Rightarrow i_2 = \frac{v_a}{R_2}$$

$$V\text{-loop in middle: } i_2 R_2 + i_1 R_1 = 0V \Rightarrow i_1 = -\frac{v_a}{R_1}$$

We could also just observe that v_a is across R_1 and R_2 .

Now that we have found i_1 and i_2 , we use a current at top node to find i_a :


$$i_a + i_2 - i_1 - \alpha i_1 = 0A \quad \text{or} \quad i_a + \frac{v_a}{R_2} + \frac{v_a}{R_1} + \alpha \frac{v_a}{R_1} =$$

$$\text{or } i_a = -v_a \left(\frac{1}{R_2} + \frac{1}{R_1} + \frac{\alpha}{R_1} \right) \quad \text{or } i_a = -\frac{v_a}{R_1 \parallel \frac{R_1}{\alpha} \parallel R_2}$$

soln: 3.b)

Many possible answers.

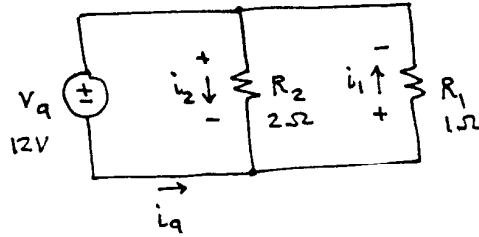Example: Suppose $\alpha = 0$. Choose other simple values:



We see that i_a is current thru $R_1 \parallel R_2$
with $R_1 \parallel R_2$ across $-V_a$.

$$R_1 \parallel R_2 = 1 \parallel 2 \Omega = \frac{1 \cdot 2}{1+2} = \frac{2}{3} \Omega$$

$$\therefore i_a = -V_a / R_1 \parallel R_2 = \frac{-12V}{\frac{2}{3} \Omega} = -12V \cdot \frac{3}{2} \Omega = -18A$$

Use formula from (a) with these component


values:

$$i_a = -12V \left(\frac{1}{2\Omega} + \frac{1}{1\Omega} + \frac{0}{1.5\Omega} \right) = -12V \cdot \frac{3}{2}$$


$i_a = -18V$ ✓ agrees with obvious soln
for this simple case

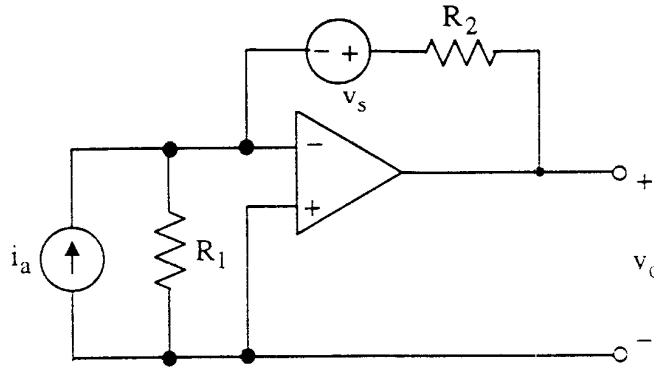4. (30 points)

The op-amp operates in the linear mode. Using an appropriate model of the op amp, derive an expression for v_o in terms of not more than v_s , i_a , R_1 , and R_2 .



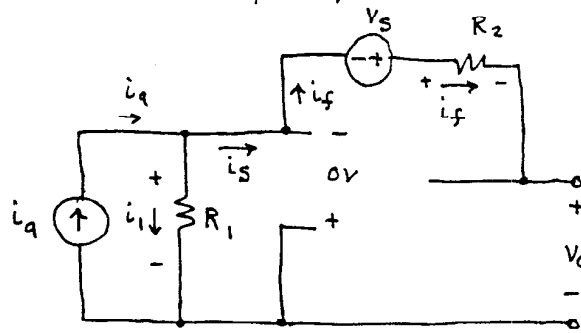sol'n: Redraw without op-amp and 0V drop across + and - inputs:



V-loop on left thru R_1 and 0V drop:

$$i_1 R_1 + 0V = 0V \quad \text{or} \quad i_1 = 0$$

Current sum at node above R_1 :

$$-i_a + \underset{0}{i_1} + i_s = 0A \quad \text{or} \quad i_s = i_a$$

V-loop on right thru 0V drop, v_s , R_2 , and v_o :

$$-0V + v_s - i_f R_2 - v_o = 0V \quad \text{or} \quad i_f = \frac{v_s - v_o}{R_2}$$

Now use $i_s = i_f$.

$$i_a = \frac{v_s - v_o}{R_2}$$

Thus $v_s - v_o = i_a R_2$

$$\text{or} \quad v_o = v_s - i_a R_2$$