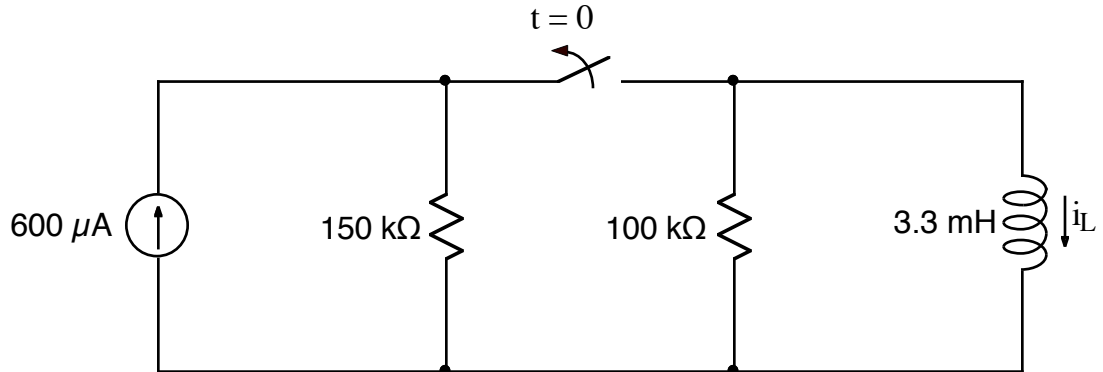


Ex:



After being closed for a long time, the switch opens at  $t = 0$ . Find  $i_L(t)$  for  $t > 0$ .

sol'n: Use the general form of solution for RL problems:

$$i_L(t > 0) = i_L(t \rightarrow \infty) + [i_L(t = 0^+) - i_L(t \rightarrow \infty)] e^{-t/\tau_{Th}}$$


To find  $i_L(0^+)$ , we consider  $t = 0^-$ .

At  $t = 0^-$ , the circuit has reached stable values, and all time derivatives of  $i$  and  $v$  are zero. Thus,  
 $v_L = L \frac{di_L}{dt} = L \cdot 0 = 0$  and  $L$  acts like a wire.

Since the switch is closed at  $t = 0^-$ , we have a current source shorted by a wire.

We are only interested in the energy variable,  $i_L(0^-)$ . All other currents and voltages may change instantly when the switch opens.

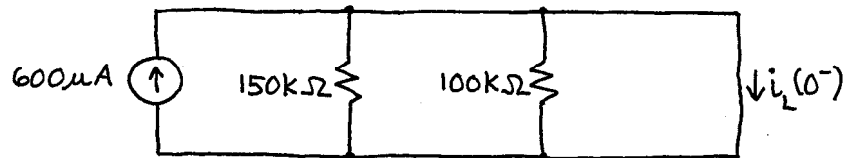
$t=0^-$ :  $L = \text{wire}$ , switch closed, find  $i_L(0^-)$



$i_L(0^-) = 600 \mu\text{A}$  since all the current will flow thru the  $L = \text{wire}$

$i_L(0^+) = i_L(0^-)$  since energy variables (like  $i_L$  and  $v_L$ ) cannot change instantly

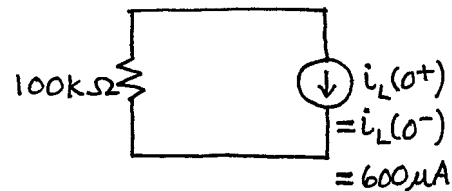
$t=0^+$ :  $L = \text{current source}$ ,  $i_L(0^+) = i_L(0^-)$ , switch open (left side of circuit disconnected)



$$i_L(0^+) = i_L(0^-) = 600 \mu\text{A}$$

Now we find  $i_L(t \rightarrow \infty)$ . As  $t \rightarrow \infty$ , the circuit again reaches stable values, and the  $L$  again acts like a wire.


$t \rightarrow \infty$ :

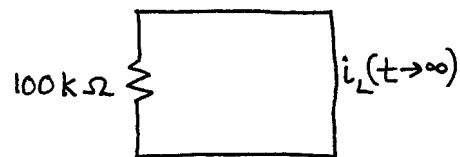

$i_L(t \rightarrow \infty) = 0$  since there is no power source.

The last quantity we need is  $R_{Th}$ , the Thevenin equivalent resistance of the circuit as seen from the terminals where the  $L$  is connected. In other words, we remove the  $L$  and find the Thevenin equivalent of the remaining circuit.

Since  $t > 0$ , the switch is open.

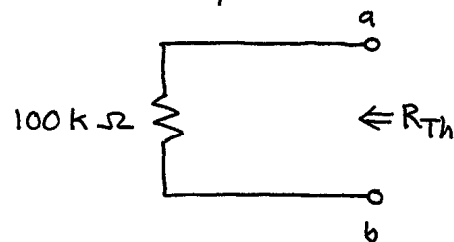

The circuit is already in Thevenin equivalent form with  $V_{Th} = 0V$  and  $R_{Th} = 100k\Omega$ .

Thus, the time constant of the circuit is

$$\frac{L}{R_{Th}} = \frac{3.3 \text{ mH}}{100 \text{ k}\Omega} = \frac{33 \text{ mH}}{1 \text{ M}\Omega} = 33 \text{ ns}$$

Substituting values into the general form of solution, we have our desired answer:

$$i_L(t > 0) = 0 \text{ A} + (600 \mu\text{A} - 0 \text{ A}) e^{-t/33 \text{ ns}}$$

or

$$i_L(t > 0) = 600 \mu\text{A} \cdot e^{-t/33 \text{ ns}}$$