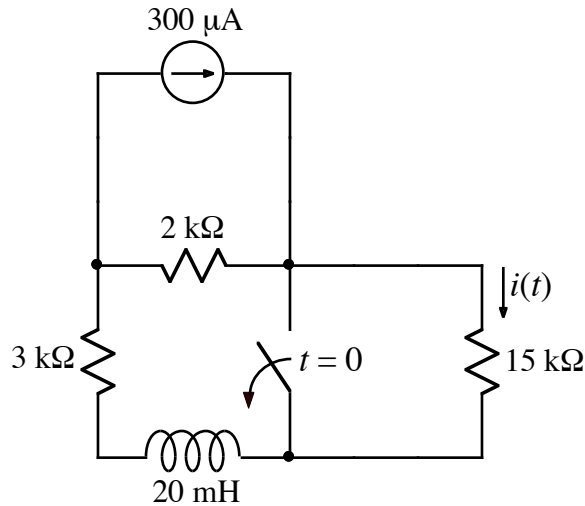


Ex:



After being closed for a long time, the switch opens at $t = 0$.

- Calculate the energy stored on the inductor as $t \rightarrow \infty$.
- Write a numerical expression for $i(t)$ for $t > 0$.

SOL'N: a) As t approaches infinity, the switch is open and the inductor acts like a wire. The $3 \text{ k}\Omega$ and $15 \text{ k}\Omega$ sum to act like an $18 \text{ k}\Omega$ resistor. This $18 \text{ k}\Omega$ resistor is in parallel with the $2 \text{ k}\Omega$ resistor, forming a current divider. The current in the inductor is the same as the current in the $3 \text{ k}\Omega$ and $15 \text{ k}\Omega$ resistors:

$$i_L(t \rightarrow \infty) = 300 \mu\text{A} \frac{2 \text{ k}\Omega}{2 \text{ k}\Omega + 18 \text{ k}\Omega} = 30 \mu\text{A}$$

The energy for an inductor is the current squared times half the inductance:

$$w_L(t \rightarrow \infty) = \frac{1}{2} L i_L^2(t \rightarrow \infty)$$

Using the final current we have the energy:

$$w_L(t \rightarrow \infty) = \frac{1}{2} 20 \text{ mH} (30 \mu\text{A})^2 = 9 \text{ pJ}$$

- We use the general form of solution for RL circuits:

$$i(t > 0) = i(t \rightarrow \infty) + [i(0^+) - i(t \rightarrow \infty)]e^{-t/(L/R_{Th})}$$

We find the initial condition for i by determining the inductor current at $t = 0^+$. With the switch closed for a long time, the $15 \text{ k}\Omega$ resistor on the right side is bypassed, and the inductor looks like a wire. The circuit becomes a current divider, with the $2 \text{ k}\Omega$ and $3 \text{ k}\Omega$ resistors in parallel. The current flowing through L is the same as the current flowing through the $3 \text{ k}\Omega$ resistor:

$$i_L(t = 0^-) = 300 \text{ }\mu\text{A} \frac{2 \text{ k}\Omega}{2 \text{ k}\Omega + 3 \text{ k}\Omega} = 120 \text{ }\mu\text{A}$$

Because the energy stored by the inductor cannot change instantly, the value of i_L at time $t = 0^+$ is the same as at time $t = 0^-$:

$$i_L(t = 0^+) = i_L(t = 0^-) = 120 \text{ }\mu\text{A}$$

Since the $15 \text{ k}\Omega$ resistor is in series with the inductor, it carries the same current as the inductor:

$$i(0^+) = i_L(t = 0^+) = 120 \text{ }\mu\text{A}$$

Finally, we find the value of R_{Th} for time $t > 0$. We remove the L and look into the terminals to find R_{Th} . Here, we may simply turn off the current source, leaving a resistance of $3 \text{ k}\Omega + 2 \text{ k}\Omega + 15 \text{ k}\Omega$:

$$R_{Th} = 20 \text{ k}\Omega$$

Our time constant is L/R_{Th} :

$$\tau = \frac{L}{R_{Th}} = \frac{20 \text{ mH}}{20 \text{ k}\Omega} = 1 \text{ }\mu\text{s}$$

Substituting values yields our final answer:

$$i(t > 0) = 30 \text{ }\mu\text{A} + [120 \text{ }\mu\text{A} - 30 \text{ }\mu\text{A}]e^{-t/1 \text{ }\mu\text{s}}$$

or

$$i(t > 0) = 30 \text{ }\mu\text{A} + 90 \text{ }\mu\text{A}e^{-t/1 \text{ }\mu\text{s}}$$