
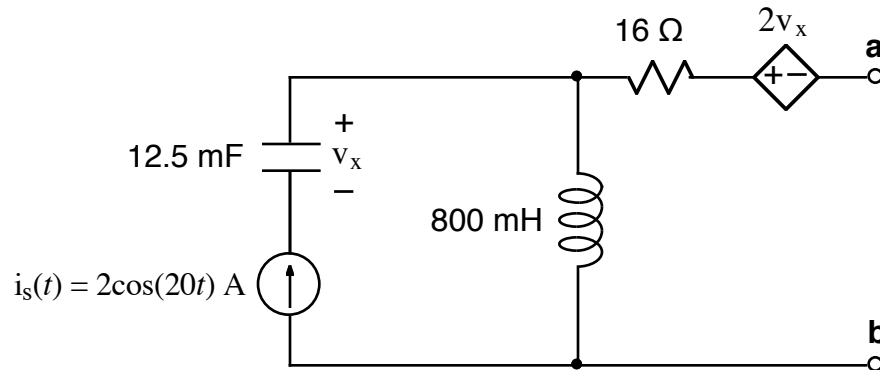


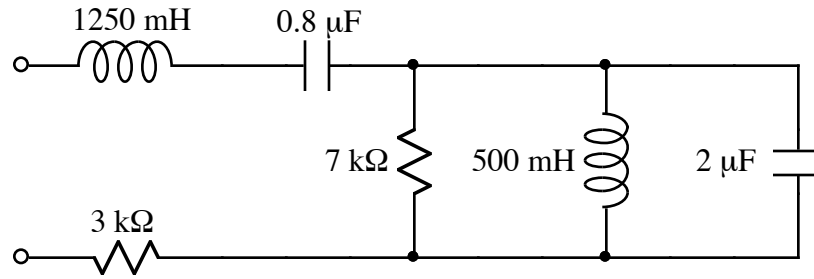1. Draw the frequency-domain circuit diagram (with numerical values for impedances and phasors [except the dependent source which will be labeled  $2V_x$ ]) for the following circuit:




2. Given  $\omega = 400$  rad/s, for each of the following impedances, determine which of the following the impedance is from: a capacitor, an inductor, or a resistor. Also, find the value of that capacitor, inductor, or resistor.
- a)  $1 \text{ k}\Omega$
  - b)  $-j50 \Omega$
  - c)  $j400 \Omega$
  - d)  $-j2 \text{ k}\Omega$
  - e)  $j8 \text{ k}\Omega$
3. Derive a symbolic expression for the impedance of an  $R$  in series with an  $L$  and  $C$  in parallel at frequency  $\omega$ . Express the answer as a ratio of polynomials with complex coefficients.


4. Find the total impedance of the circuitry shown below if  $\omega = 50\text{k rad/s}$ .



- 5.

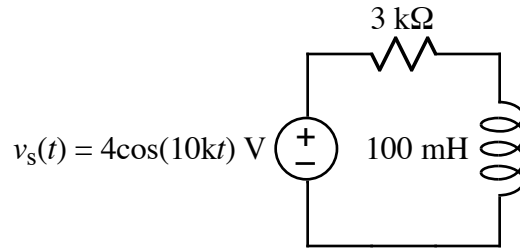

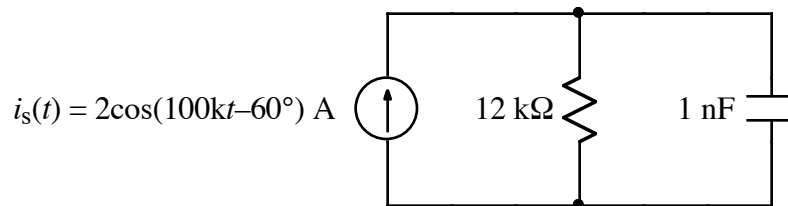- a) Find time-domain expressions for the waveforms of the voltages across the  $R$  and  $L$  in the above circuit.



- b) Find time-domain expressions for the waveforms of the currents through the  $R$  and  $C$  in the above circuit.