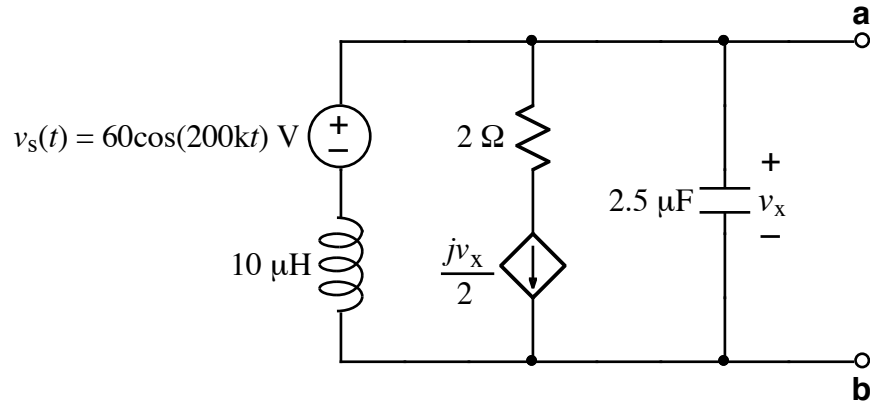


Ex:



- Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for $v_s(t)$, and show numerical impedance values for R , L , and C . Label the dependent source appropriately.
- Find the Thevenin equivalent (in the frequency domain) for the above circuit. Give the numerical phasor value for V_{Th} and the numerical impedance value of z_{Th} .


SOL'N: a) We calculate the impedances for the frequency-domain circuit:

$$V_s = 60\angle 0^\circ \text{ V}$$


$$z_L = j\omega L = j200k \cdot 10\mu \Omega = j2 \Omega$$

$$z_C = \frac{1}{j\omega C} = \frac{1}{j200k \cdot 2.5\mu} \Omega = -j2 \Omega$$

The frequency domain circuit:

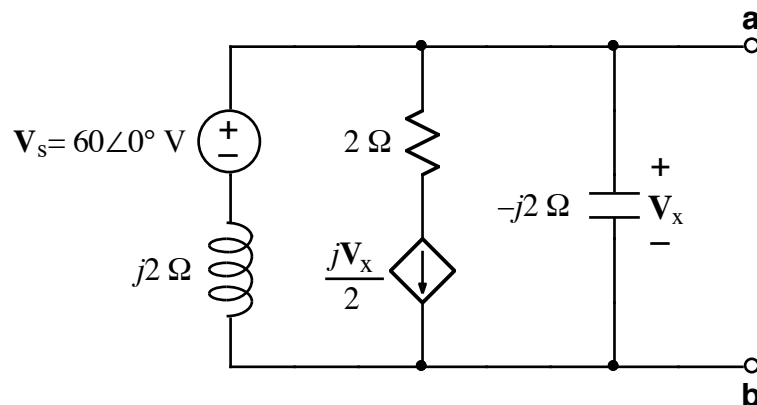

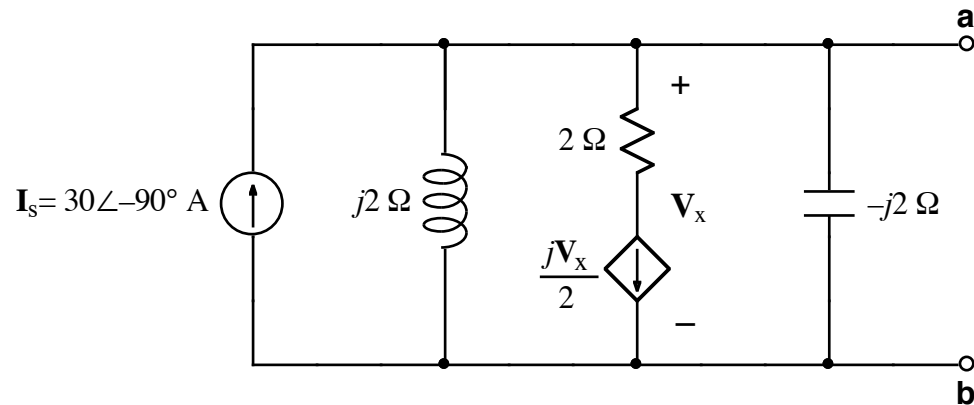- b) The Thevenin equivalent voltage is the voltage at **a** and **b** for the circuit with no load attached at **a** and **b**. We may perform a source transformation on the left side to obtain the following circuit:



In the above circuit, the inductance and capacitance in parallel are equivalent to an open circuit. With the inductor and capacitor gone, we see that current from \mathbf{I}_s flows through the dependent current source. Thus, the dependent current source must have the same current as \mathbf{I}_s :

$$\frac{j\mathbf{V}_x}{2} = \mathbf{I}_s$$


or

$$\mathbf{V}_x = \frac{2\mathbf{I}_s}{j} = \frac{2 \cdot 30\angle -90^\circ \text{ V}}{1\angle -90^\circ} = 60 \text{ V}$$

This voltage is the same as the Thevenin equivalent voltage:

$$\mathbf{V}_{\text{Th}} = \mathbf{V}_x = 60 \text{ V}$$

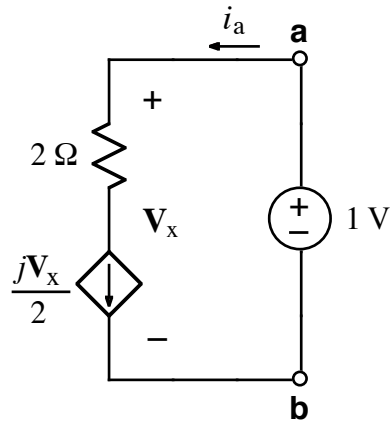To find the Thevenin impedance, we turn off the independent current (and remove the L and C that cancel out). Then we apply a voltage (1 V) to the **a** and **b** terminals:



We see that $V_x = 1 \text{ V}$ and the dependent current source carries the current i_a :

$$i_a = \frac{jV_x}{2} = j\frac{1}{2} \text{ A}$$

The Thevenin impedance is 1 V divided by the current, i_a :

$$z_{Th} = \frac{1 \text{ V}}{i_a} = \frac{1 \text{ V}}{j\frac{1}{2} \text{ A}} = -j2 \Omega$$

Thus, we have the following Thevenin equivalent circuit:

