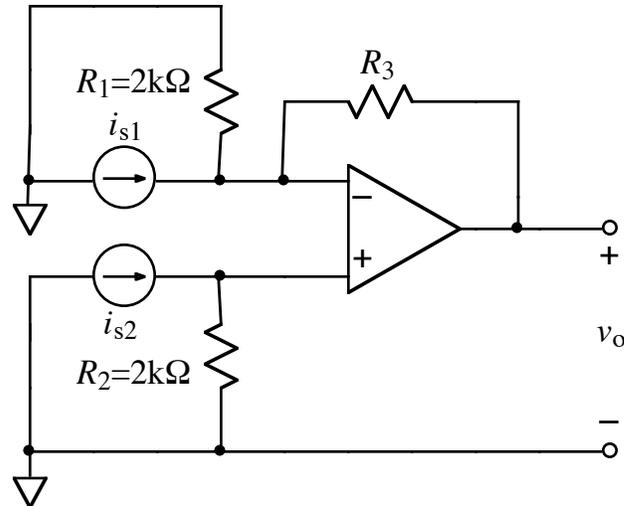


1.



Rail voltages =  $\pm 10$  V

The above circuit operates in linear mode. Derive a symbolic expression for  $v_o$ . The expression must contain not more than the parameters  $i_{s1}$ ,  $i_{s2}$ ,  $R_1$ ,  $R_2$ , and  $R_3$ .

2. a) If  $i_{s1} = 0 \mu\text{A}$ , find the value of  $R_3$  that will yield an output voltage of  $v_o = 1$  V when  $i_{s2} = 10 \mu\text{A}$ .
- b) Derive a symbolic expression for  $v_o$  in terms of common mode and differential input currents:

$$i_{\Sigma} \equiv \frac{i_{s1} + i_{s2}}{2} \quad \text{and} \quad i_{\Delta} \equiv \frac{i_{s1} - i_{s2}}{2}$$


The expression must contain not more than the parameters  $i_{\Sigma}$ ,  $i_{\Delta}$ ,  $R_1$ ,  $R_2$ , and  $R_3$ . Write the expression as  $i_{\Sigma}$  times a term plus  $i_{\Delta}$  times a term.

Hint: start by writing  $i_{s1}$  and  $i_{s2}$  in terms of  $i_{\Sigma}$  and  $i_{\Delta}$ :

$$i_{s1} \equiv i_{\Sigma} + i_{\Delta} \quad \text{and} \quad i_{s2} \equiv i_{\Sigma} - i_{\Delta}$$

3. If  $i_{\Delta} = 0$  and  $R_1 = R_2$ , write a formula for the current flowing from left to right in  $R_3$  as a function of not more (and possibly less) than the following terms:  $i_{\Sigma}$ ,  $R_1$ ,  $R_2$ , and  $R_3$ .

4.

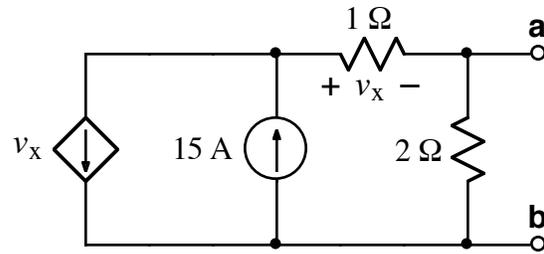

Find the Thevenin equivalent of the above circuit relative to terminals **a** and **b**.

- 5.
- a) If we attach  $R_L$  to terminals **a** and **b**, find the value of  $R_L$  that will absorb maximum power.
  - b) Calculate the value of that maximum power absorbed by  $R_L$ .