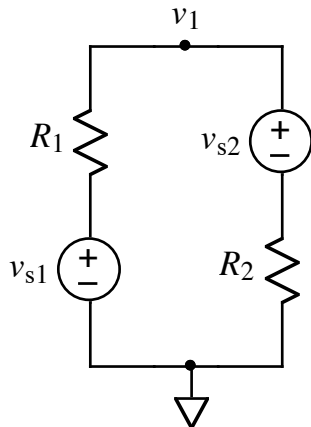


**Ex:**

Use the node-voltage method to find a formula for  $v_1$ . Write your answer as a sum of a voltage divider for  $v_{s1}$  and a voltage divider for  $v_{s2}$ .

**SOL'N:** We sum currents out of the  $v_1$  node:

$$\frac{v_1 - v_{s1}}{R_1} + \frac{v_1 - v_{s2}}{R_2} = 0 \text{ V}$$

or

$$v_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v_{s1}}{R_1} + \frac{v_{s2}}{R_2}$$

or

$$R_1 R_2 v_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = R_1 R_2 \left( \frac{v_{s1}}{R_1} + \frac{v_{s2}}{R_2} \right)$$

or

$$v_1 (R_1 + R_2) = v_{s1} R_2 + v_{s2} R_1$$

or

$$v_1 = \frac{v_{s1} R_2 + v_{s2} R_1}{R_1 + R_2}$$

or, when written as a sum of voltage dividers:

$$v_1 = v_{s1} \frac{R_2}{R_1 + R_2} + v_{s2} \frac{R_1}{R_1 + R_2}$$