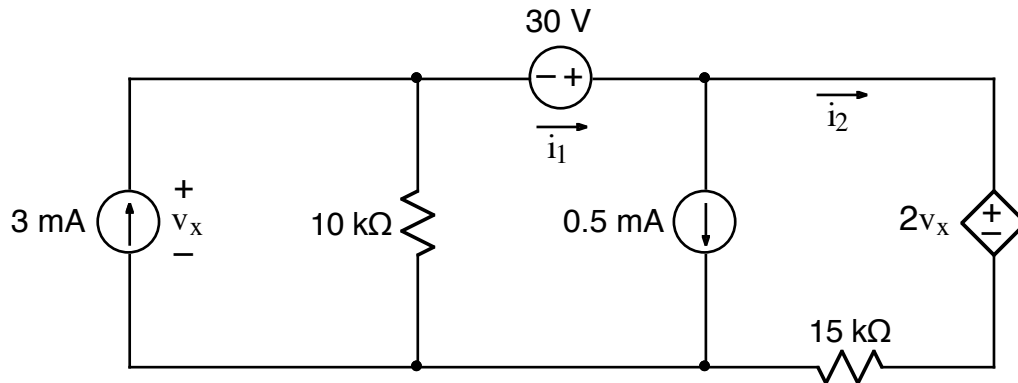


Ex:




- Use the mesh-current method to find  $i_1$  and  $i_2$ .
- Find the power dissipated by the dependent source.

sol'n: a) We follow a step-by-step procedure:

- We define mesh currents. If, however, we have any current sources on outside edges of the circuit, the mesh currents for those loops will be the same as the current source.

In this circuit, we have a current source on the left edge. Thus, the mesh current for the left loop is 3mA.

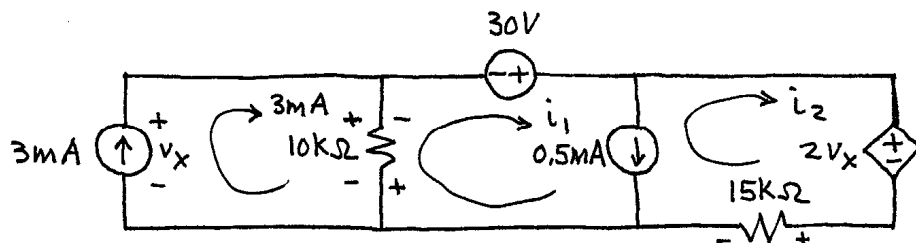Since  $i_1$  and  $i_2$ , as defined, are on the outside edge of the circuit, we may use them as our mesh currents.



- 2) We define the voltage from the dependent src,  $v_x$ , in terms of mesh currents. Here, we observe that  $v_x$  is across the  $10k\Omega$  resistor, too. For the  $10k\Omega$  resistor, we have

$$v_x = 3\text{mA} \cdot 10k\Omega - i_1 \cdot 10k\Omega$$

- 3) We look for loops with a current source in between, meaning we have a super mesh. This is the case for the  $i_1, i_2$  loops. For the  $i_1, i_2$  supermesh, we take a  $v$ -loop around the outside edge of the  $i_1$  and  $i_2$  loops, (bypassing the  $0.5\text{mA}$  src).

$$i_1, i_2 \text{ } v\text{-loop: } -i_1 \cdot 10k\Omega + 30V - \overbrace{2(3\text{mA} - i_1)}^{v_x} 10k\Omega + 3\text{mA} \cdot 10k\Omega$$

$$-i_2 \cdot 15k\Omega = 0V$$

Add a current eq'n for the  $0.5\text{mA}$  src between the loops:

$$i_1 - i_2 = 0.5\text{mA} = \frac{1}{2}\text{mA}$$

Note: we have  $-i_2$  for current measured opposite the arrow in the current src.

- 4) We solve our eq'ns for  $i_1$  and  $i_2$ .

We group  $i_1$  and  $i_2$  terms on the left and move constant to the right side.

$$i_1 \underbrace{(-10k\Omega + 2 \cdot 10k\Omega)}_{= 10k\Omega} + i_2(-15k\Omega) = -60V + 60V$$

$$i_1 - i_2 = \frac{1}{2} \text{ mA}$$

Solving the 2<sup>nd</sup> eq'n for  $i_1$ , we have

$$i_1 = i_2 + \frac{1}{2} \text{ mA}$$

Substituting into 1<sup>st</sup> eq'n, we have

$$(i_2 + \frac{1}{2} \text{ mA}) 10k\Omega + i_2(-15k\Omega) = 30V$$


$$\text{or } i_2(10k\Omega - 15k\Omega) = 30V - \frac{1}{2} \text{ mA} \cdot 10k\Omega$$

$$\text{or } -i_2(5k\Omega) = -5V$$

$$\text{or } i_2 = 1 \text{ mA}$$

$$\text{Then } i_1 = 1 \text{ mA} + \frac{1}{2} \text{ mA} = \frac{3}{2} \text{ mA}$$

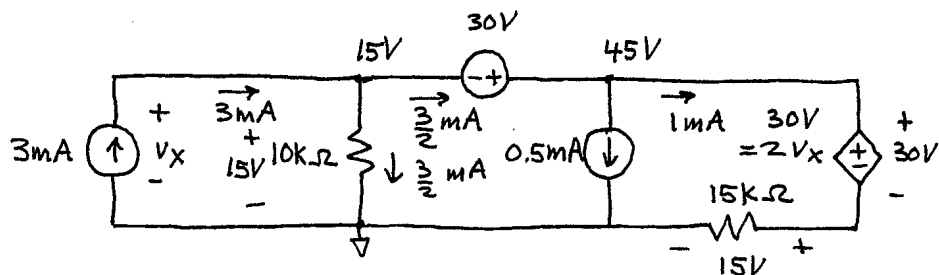Consistency check: calculate v-drops for  $i_1, i_2$  and verify v-loops.



$$V_x = \frac{3}{2} \text{ mA} \cdot 10k\Omega = 15V$$

All v-loops sum to 0V, and all current sums at nodes = 0A. ✓

---

b) We know  $v_x = (3\text{mA} - i_1) 10\text{k}\Omega$

$$= \frac{3}{2} \text{mA} \cdot 10\text{k}\Omega$$

$$v_x = 15\text{V}$$

The current for the dependent src is  $i_2$ .

$$i_2 = 1\text{mA}$$

Thus, power for the dependent src is

$$p = v \cdot i = 2v_x i_2 = 2(15\text{V}) \cdot 1\text{mA}$$

$$\text{or } p = 30 \text{ mW.}$$