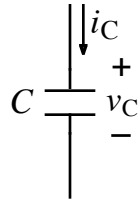
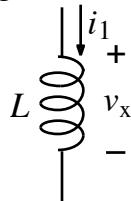


1. In (a)-(c), the voltage  $v_C(t)$  across a 500 nF capacitor is listed. Find the current,  $i_C(t)$ , flowing in the capacitor in each case as a function of time:



- a)  $v_C(t) = 5 \text{ V}$   
b)  $v_C(t) = 30t \text{ kV/s}$   
c)  $v_C(t) = 1 - e^{-t/10\mu\text{s}} \text{ V}$

2. In (a)-(c), the current  $i_L(t)$  flowing into a 2  $\mu\text{H}$  inductor is listed. Find the voltage,  $v_L(t)$ , across the inductor in each case as a function of time:



- a)  $i_L(t) = 3 \text{ mA}$   
b)  $i_L(t) = 10t \text{ MA/s}$   
c)  $i_L(t) = 8\cos(2\pi \cdot 10\text{k} \cdot t) \mu\text{A}$

3. The following equation describes the voltage,  $v_C$ , across a capacitor as a function of time. Find the time,  $t$ , at which  $v_C$  is equal to -4 V.

$$v_C(t) = -12 + 10(1 - e^{-t/2\text{ms}}) \text{ V}$$

4. The following equation describes the voltage,  $v_L$ , across an inductor as a function of time. Find an expression for the current,  $i_L(t)$ , through the inductor as a function of time. Assume that  $i_L(t = 0) = 0 \text{ A}$ .

$$v_L(t) = 10 - 4e^{-t/50\text{ms}} \text{ V}$$

5. Find the voltage,  $v_C$ , on the capacitor in the circuit below as a function of time if  $v_C(t = 0^+) = 6 \text{ V}$ .

