
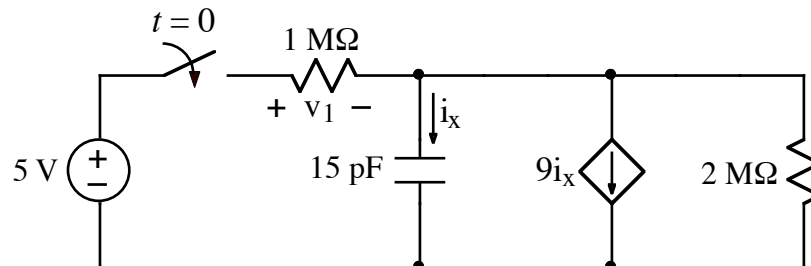


Ex:

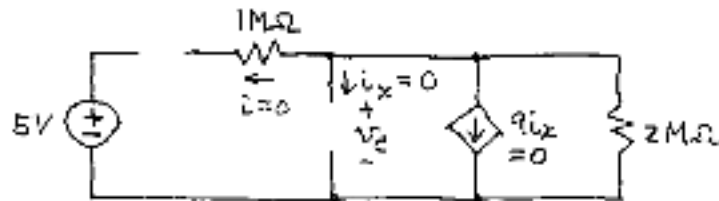

After being open for a long time, the switch closes at $t = 0$. Find $v_1(t)$ for $t > 0$.

sol'n: $t = 0^-$ model: (to find $v_c(0^-)$) $C = \text{open circuit}$



The total current flowing out of top node equals zero, and there is no current flowing in the $1\text{M}\Omega$, the C , and the dependent source. It follows that the current in the $2\text{M}\Omega$ is 0A . By Ohm's law, the voltage drop across the $2\text{M}\Omega$ is $0 \cdot 2\text{M}\Omega = 0\text{V}$. This is also the voltage across the C .


$$\therefore v_c(0^-) = 0\text{V}$$

and

$$v_c(0^+) = v_c(0^-) = 0\text{V}$$


We use this value of $v_c(t=0^+)$ as a voltage source in the $t=0^+$ model to find $v_1(0^+)$.

$t = 0^+$ model:

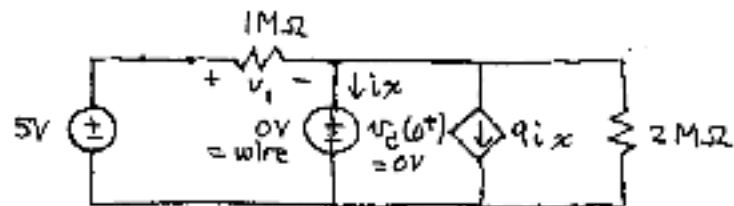

From a voltage loop on the left side, we have $v_1(0^+) = 5V$. Note: the components to the right of C are in parallel with the circuitry on the left and directly across the same voltage source, (namely $0V$).

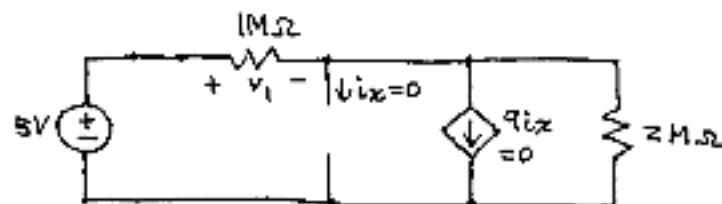
$t \rightarrow \infty$ model: (to find $v_1(t \rightarrow \infty)$) $C = \text{open circ}$



The dependent src is off and effectively disappears. This leaves a voltage divider:

$$v_1(t \rightarrow \infty) = 5V \cdot \frac{1M\Omega}{1M\Omega + 2M\Omega} = \frac{5}{3}V$$

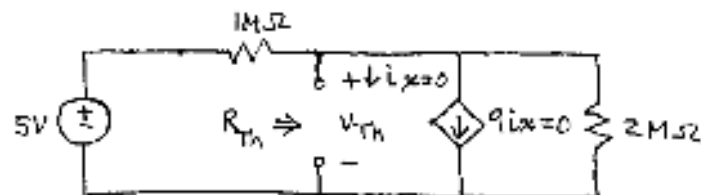
Finally, we have $\tau = R_{Th}C$ where R_{Th} is the Thevenin equivalent resistance seen looking into the terminals where C is connected.



Because there is a dependent source, we find R_{Th} from $R_{Th} = \frac{V_{Th}}{i_{sc}}$.

V_{Th} , as always, equals the voltage across the output terminals when nothing is connected across them. Since $i_x = 0$ and $g_i i_x = 0$, V_{Th} is given by a voltage divider formula:
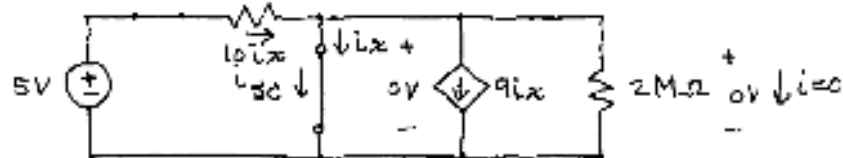
$$V_{Th} = \frac{5V \cdot 2M\Omega}{1M\Omega + 2M\Omega} = \frac{10V}{3}$$



If we short out the output terminals, we have 0V across the $2M\Omega$ resistor. Thus, there is no current in the $2M\Omega$ R.

A current summation for the top node reveals that the current in the $1M\Omega$ must be $10i_x$. From a v-loop on the left side, we also have 5V across the $1M\Omega$ R. Thus, the current in the $1M\Omega$ R is $5V/1M\Omega = 5\mu A$. Thus, we have

$$5\mu A = 10i_x \quad \text{or} \quad i_x = 0.5\mu A$$

From the schematic diagram, we see that

$$i_{sc} = i_x = 0.5 \mu A.$$

$$\therefore R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{10 \text{ V}}{\frac{0.5 \mu A}{3}} = \frac{20}{3} \text{ M}\Omega$$

$$\text{Thus, } \tau = R_{Th} C = \frac{20}{3} \text{ M}\Omega \cdot 15 \text{ pF} = 100 \mu s.$$

Using the general form of solution, we have

$$v_f(t) = v_f(t \rightarrow \infty) + [v_f(t=0^+) - v_f(t \rightarrow \infty)] e^{-t/\tau}$$

$$v_f(t) = \frac{5}{3} \text{ V} + \left[5 \text{ V} - \frac{5}{3} \text{ V} \right] e^{-t/100 \mu s}, \quad t > 0$$

$$\text{or } v_f(t) = \frac{5}{3} \text{ V} + \frac{10}{3} \text{ V} e^{-t/100 \mu s}, \quad t > 0$$

Note: A much simpler way to solve this problem is to observe ^{that} the dependent source acts like a capacitor that is 9 times C. Since the C and 9C are in parallel, we have an equivalent capacitance of $10C = 10 \cdot 15 \text{ pF} = 150 \text{ pF}$. The dependent source is now gone, and the sol'n is easier to find. The solution, of course is the same as above. $R_{Th} C$ is the same, but $R_{Th} = 1 \text{ M}\Omega \parallel 2 \text{ M}\Omega$ and $C = 150 \text{ pF}$. $v_f(0^+)$ and $v_f(t \rightarrow \infty)$ are the same as before.