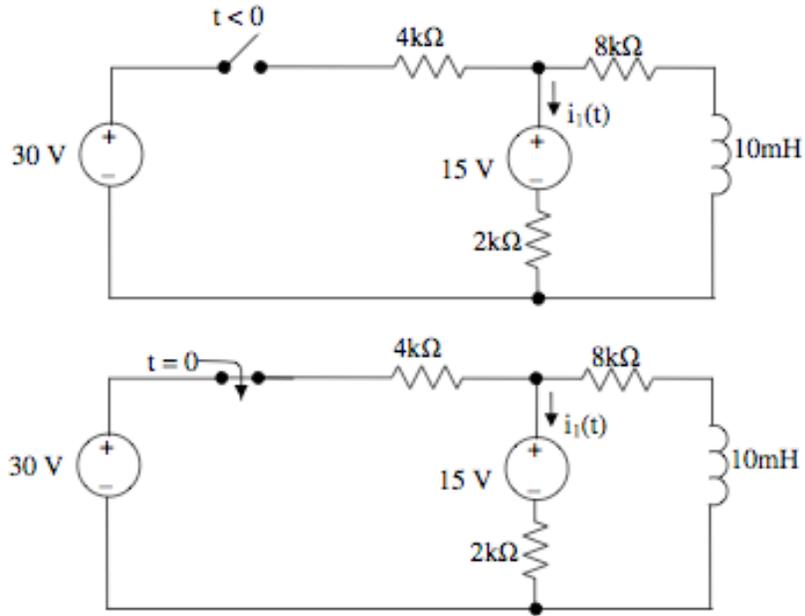




1.




After being open for a long time, the switch closes at  $t = 0$ .  
Calculate the energy stored on the inductor as  $t \rightarrow \infty$ .

2.


For the circuit in problem 1, write a numerical expression for  $i_1(t)$  for  $t > 0$ .

3.

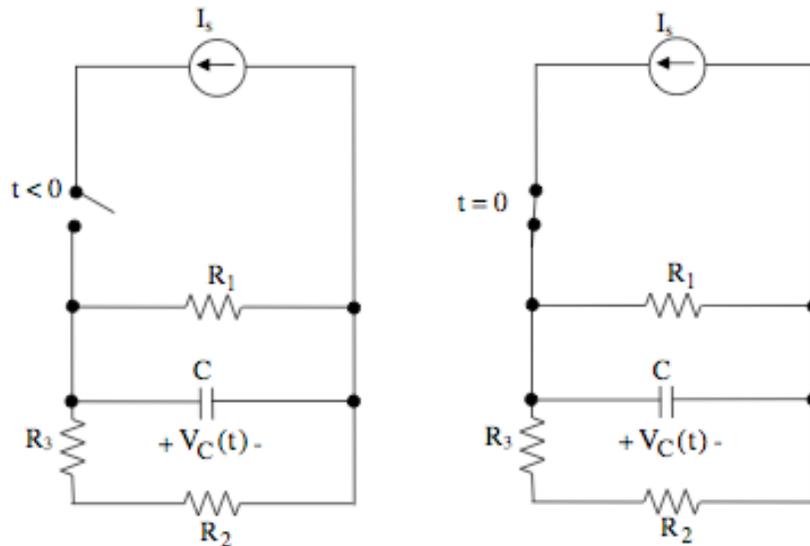


After being open for a long time, the switch closes at  $t = 0$ . Write an expression for  $v_C(t > 0)$  in terms of at most circuit quantities  $R_1$ ,  $R_2$ ,  $R_3$ ,  $i_s$ , and  $C$ .

4.

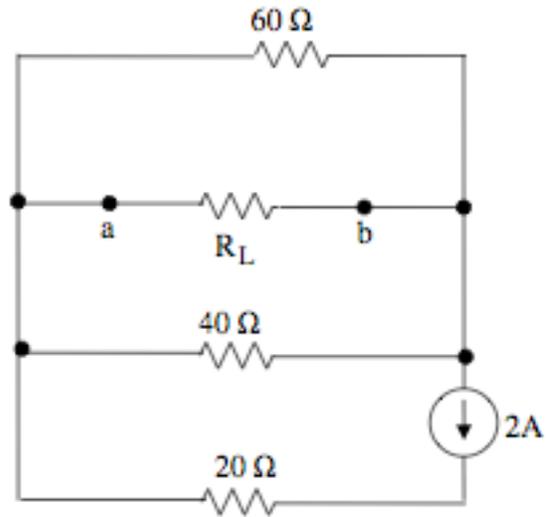

- a) Calculate the value of  $R_L$  that would absorb maximum power.
- b) Calculate that value of maximum power  $R_L$  could absorb.

5.

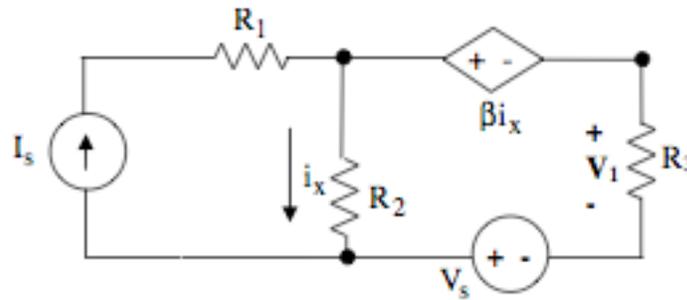

Using superposition, derive an expression for  $v_1$  that contains no circuit quantities other than  $i_s$ ,  $v_s$ ,  $R_1$ ,  $R_2$ ,  $R_3$ , and  $\beta$ , where  $\beta < 0$ .