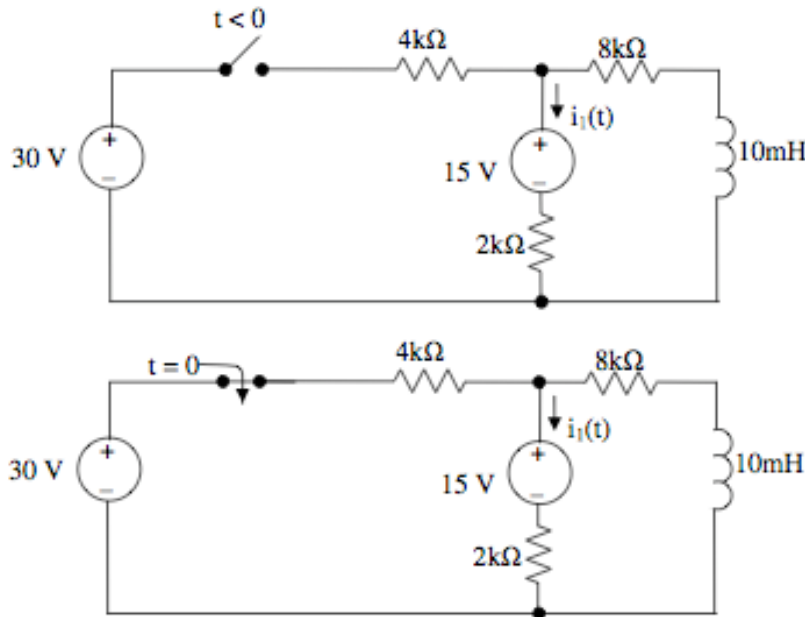


Ex:



After being open for a long time, the switch closes at $t = 0$.

- Calculate the energy stored on the inductor as $t \rightarrow \infty$.
- Write a numerical expression for $i_1(t)$ for $t > 0$.

SOL'N:


$(t=0^-)$ Inductor acts as a wire. Switch is open
 $V\text{-loop: } +2ki_1 + 15 + 8ki_1 = 0 \therefore i_1 = \frac{-15}{10k} = -1.5\text{mA}$

$(t=0^+)$ Inductor acts as I src. Switch closed.

node -V: $\frac{V_1 - 30}{4k} + \frac{V_1 - 15}{2k} + (1.5\text{mA}) = 0$
 $V_1 \left(\frac{1}{4k} + \frac{2}{2k} \right) = \frac{30}{4k} + \frac{15(2)}{2k(2)} - 1.5\text{mA}$
 $V_1 = \frac{4k \left(\frac{60}{4k} - 1.5\text{mA} \right)}{3} =$

$i_1 = \frac{(V_1 - 15)}{2k} = \frac{(18 - 15)}{2k} = \frac{3}{2k} = 1.5\text{mA}$
Initial value

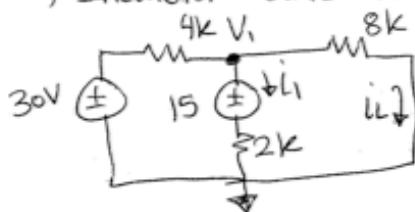($t \rightarrow \infty$) Inductor acts as a wire. switch closed.



using node-V:


$$\frac{(V_1 - 30)}{4k} + \frac{(V_1 - 15)}{2k} + \frac{V_1}{8k} = 0$$

$$V_1 \left(\frac{2(1)}{2(4k)} + \frac{4(1)}{4(2k)} + \frac{1}{8k} \right) = \frac{30}{4k} + \frac{15(2)}{2k(2)}$$

$$V_1 = \frac{60}{4k} \cdot \left(\frac{8k}{7} \right) = \frac{120}{7}$$

$$i_1 = \frac{(V_1 - 15)}{2k} = \frac{\left(\frac{120}{7} - 15 \right)}{2k} = \boxed{1.1mA} \quad \text{Final value}$$

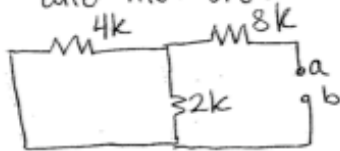τ : (Remove inductor and ind. src's) $\tau = \frac{L}{R_{eq}}$



$$R_{eq} = 8k + 4k(2k)$$

$$R_{eq} = 8k + \frac{4k(2k)}{6k} = \frac{48k}{6} + \frac{8k}{6}$$

$$R_{eq} = \frac{56k}{6}$$

$$\Rightarrow \tau = \frac{10m \cdot 6}{56k} \approx 1.1\mu$$

($t > 0$)

$$i_1(t) = 1.1mA + (1.5mA - 1.1mA)e^{-t/1.1\mu sec} \quad A$$

Energy at $t \rightarrow \infty$

$$i_2 = \frac{V_1}{8k} = \frac{120}{7(8k)} \approx 2.1mA$$

$$w_L = \frac{1}{2} L i_2^2 = \frac{1}{2} (10m)(2.1mA)^2 = \boxed{22.05nJ}$$