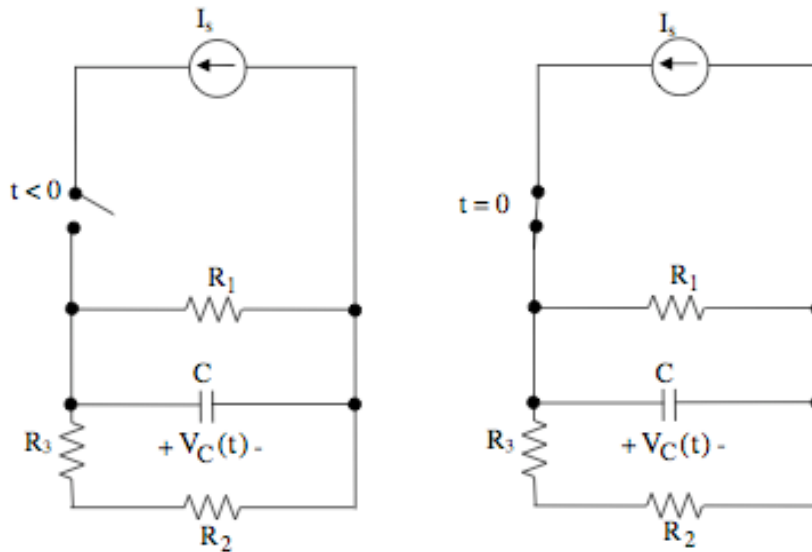


Ex:




After being open for a long time, the switch closes at $t = 0$. Write an expression for $v_C(t > 0)$ in terms of at most circuit quantities R_1, R_2, R_3, i_s , and C .

SOL'N:


$$R_1 \parallel (R_2 + R_3) = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3}$$

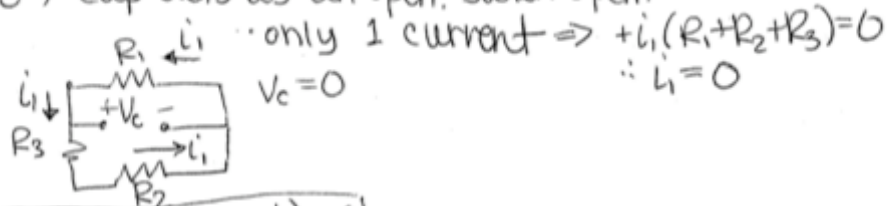($t = 0^-$) cap acts as an open, switch open.



$$V_C(t = 0^-) = V_C(t = 0^+) = 0$$

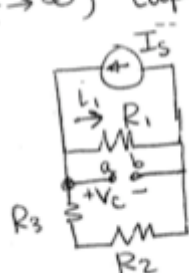($t \rightarrow \infty$) cap acts as an open, switch closed.



current divider:
 $i_1 = \frac{I_s (R_2 + R_3)}{R_1 + R_2 + R_3} \therefore V_C = i_1 R_1 = \frac{I_s R_1 (R_2 + R_3)}{R_1 + R_2 + R_3}$

$$t > 0 \quad \tau = R_{eq} \cdot C = R_1 \parallel (R_2 + R_3) \cdot C$$

$$V_C(t) = \frac{I_s R_1 (R_2 + R_3)}{R_1 + R_2 + R_3} - \frac{I_s R_1 (R_2 + R_3)}{R_1 + R_2 + R_3} e^{-t / [R_1 \parallel (R_2 + R_3) C]} \quad \checkmark$$