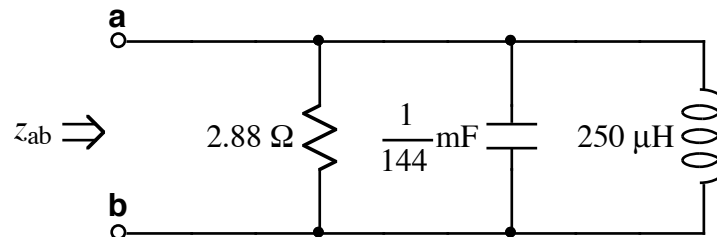


Ex:



Find a frequency, ω , that causes z_{ab} to have a phase angle of -45° , (i.e., imaginary part is the negative of the real part). Hint: use admittance, (the reciprocal of impedance).

sol'n: For single components in parallel, using admittance = $1/z$ is helpful.

$$\frac{1}{z_{ab}} = \frac{1}{z_R} + \frac{1}{z_C} + \frac{1}{z_L}$$

$$\begin{aligned} \text{Here, we have } z_C &= \frac{1}{j\omega C} = -\frac{j}{\omega C} \\ &= \frac{-j}{\omega \cdot \frac{1}{144\text{m}}} = -\frac{j}{\omega} \cdot 144\text{m} \end{aligned}$$

$$z_L = j\omega L = j\omega \cdot 250\mu$$

If $\angle z_{ab} = -45^\circ$, then $z_{ab} = k(1-j)$
where k is a positive real number.

$$\text{Then } \frac{1}{z_{ab}} = \frac{1}{k(1-j)} = \frac{1+j}{k(1-j)(1+j)} = \frac{1+j}{2k}$$

Thus, $\angle \frac{1}{z_{ab}} = 45^\circ$ and $\text{Re}\left[\frac{1}{z_{ab}}\right] = \text{Im}\left[\frac{1}{z_{ab}}\right]$.

We observe that the values of $\frac{1}{z_c}$ and $\frac{1}{z_L}$ are pure imaginary and constitute the entire imaginary part of $\frac{1}{z_{ab}}$:

$$\begin{aligned}\operatorname{Im}\left[\frac{1}{z_{ab}}\right] &= \operatorname{Im}\left[\frac{1}{z_c} + \frac{1}{z_L}\right] \\ &= \operatorname{Im}\left[j\omega C + \frac{1}{j\omega L}\right] \\ &= \operatorname{Im}\left[j\omega C - \frac{j}{\omega L}\right] \\ &= \omega C - \frac{1}{\omega L}.\end{aligned}$$

Note: $\operatorname{Im}[\]$ has a real value.
 $\operatorname{Im}[a+jb] = b$ rather than jb .

The real part of z_{ab} consists entirely of $\frac{1}{R}$:

$$\operatorname{Re}\left[\frac{1}{z_{ab}}\right] = \operatorname{Re}\left[\frac{1}{R}\right] = \frac{1}{R}$$

Now we solve $\operatorname{Re}\left[\frac{1}{z_{ab}}\right] = \operatorname{Im}\left[\frac{1}{z_{ab}}\right]$

or $\frac{1}{R} = \omega C - \frac{1}{\omega L}$.

$$\text{or } \frac{1}{RC} \omega = \omega^2 - \frac{1}{LC}$$

$$\text{or } \omega^2 - \frac{1}{RC} \omega - \frac{1}{LC} = 0$$

$$\text{or } \omega = \frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

Note: since $\omega > 0$, we use only $+$ sign.

$$\omega = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

Now we calculate values.

$$\frac{1}{2RC} = \frac{1}{2(2.88) \frac{1 \text{ m}}{144} \text{ s}} = \frac{1 \text{ k} \cdot 1 \text{ k}}{2(2.88 \text{ k}) \text{ s}}$$

$$\frac{1}{2RC} = \frac{1 \text{ M}}{40 \text{ s}} = 25 \text{ k/s}$$

$$\frac{1}{LC} = \frac{1}{250 \mu \cdot \frac{1 \text{ m}}{144} \text{ s}^2}$$

$$= \frac{144 \text{ G/s}^2}{250} \cdot \frac{4}{4}$$

$$= 4(144) \text{ M/s}^2$$

$$\frac{1}{LC} = (24 \text{ k/s})^2$$

Using values, we have the following:

$$\omega = 25 \text{ k/s} + \sqrt{(25 \text{ k/s})^2 + (24 \text{ k/s})^2}$$

$$\omega \doteq 25 \text{ k/s} + 34.7 \text{ k/s}$$

$$\omega \doteq 59.7 \text{ k/s}$$