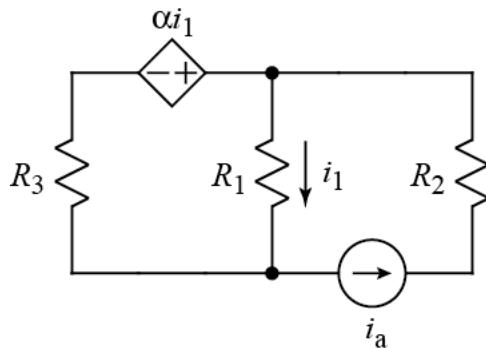





Ex:



Derive an expression for i_1 . The expression must contain no other parameters than i_a , R_1 , R_2 , R_3 , and α . **Note:** $\alpha < 0$. (Hint: It is not just a voltage or current divider.)

SOL'N:

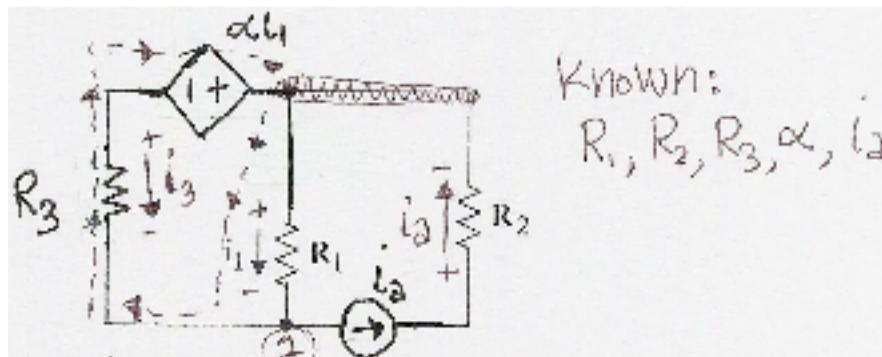

$$\text{V-loop: } +i_3 R_3 + \alpha i_1 - R_1 i_1 = 0$$

$$\textcircled{1} \quad i_3 R_3 + i_1 (\alpha - R_1) = 0$$

Current summation at ②

$$-i_3 - i_1 + i_2 = 0$$

$$\textcircled{3} \quad i_3 = i_2 - i_1$$

$$\text{plugging } i_3 \text{ into } \textcircled{1} \Rightarrow$$

$$i_2 R_3 - i_1 R_3 + i_1 (\alpha - R_1) = 0$$

$$i_1 (R_3 - \alpha + R_1) = i_2 R_3$$

$$\boxed{i_1 = \frac{i_2 R_3}{(R_1 + R_3 - \alpha)}}$$