
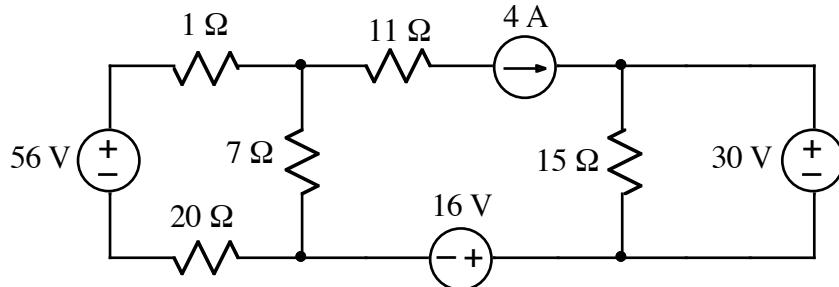


Ex:

Choose a reference node and use the node-voltage method to the remaining node voltages.

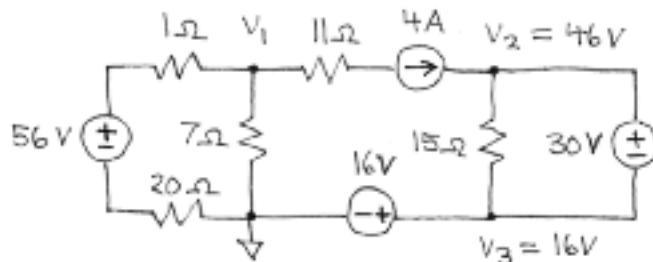SOL'N: Node voltages shift up or down, depending on which node is chosen as the reference node. The choice is arbitrary. Here, the reference node will be below the 7 Ω resistor.




We find that V_2 and V_3 are known values, owing to the 16V and 30V sources connected in series to the reference node, (with no series resistors).

We have only the V_1 node to solve for. The summation of currents out of the V_1 node yields the following eq'n:

$$\frac{V_1 - 56V}{1\Omega + 20\Omega} + \frac{V_1}{7\Omega} + 4A = 0A$$

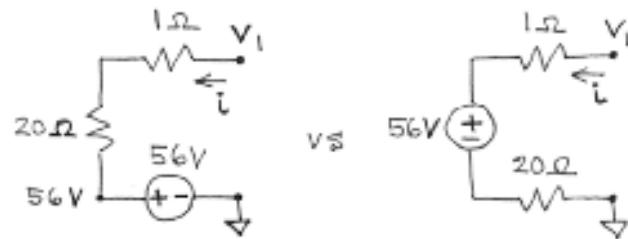Note: The first term of the current summation is found by sliding the 20Ω resistor thru the $56V$ source.



The current i is the same in both circuits:

$$i = \frac{V_1 - 56V}{1\Omega + 20\Omega}$$

Returning to the eq'n for V_1 , we group together the terms multiplying V_1 and move constants to the right side:

$$V_1 \left(\frac{1}{21\Omega} + \frac{1}{7\Omega} \right) = \frac{56V}{21\Omega} - 4A$$

Multiplying both sides by 21Ω yields the following:

$$V_1 (1+3) = 56V - 21\Omega (4A) = 56V - 84V$$

or

$$V_1 = -\frac{28V}{4} = -7V$$

Note: The currents flowing out of the V_1 node are $-3A$ to the left, $-1A$ down, and $4A$ to the right. The sum is zero. ✓