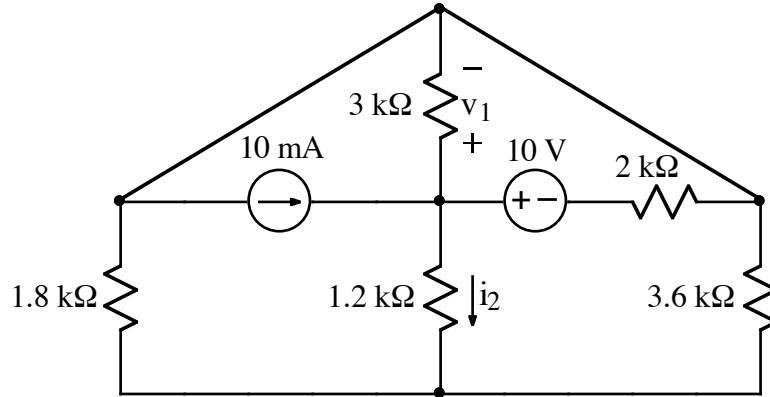


**Ex:**

- a) Use the node-voltage method to calculate  $v_1$  and  $i_2$ .  
 b) Calculate the power in the  $2\text{ k}\Omega$  resistor.

*sol'n:* Can put ref node where we like.

Putting ref at top is convenient for definition of  $v_1$ . We note that all 3 nodes on top are the ref node.

$$v_1 - \text{node eqn: } \frac{v_1 - 0V}{3k\Omega} - 10\text{ mA} + \left( \frac{v_1 - 10V}{2k\Omega} \right) - 0V + \frac{v_1 - v_2}{1.2k\Omega} = 0A$$

$$\text{or } v_1 \left( \frac{1}{3k\Omega} + \frac{1}{2k\Omega} + \frac{1}{1.2k\Omega} \right) + v_2 \left( -\frac{1}{1.2k\Omega} \right)$$

$$= 10\text{ mA} + \frac{10V}{2k\Omega}$$

$$v_2 - \text{node eqn: } \frac{v_2 - 0V}{1.8k\Omega} + \frac{v_2 - v_1}{1.2k\Omega} + \frac{v_2 - 0V}{3.6k\Omega} = 0A$$

$$\text{or } V_1 \left( \frac{-1}{1.2k\Omega} \right) + V_2 \left( \frac{1}{1.8k\Omega} + \frac{1}{1.2k\Omega} + \frac{1}{3.6k\Omega} \right) = cA$$

$$\text{consider } \frac{1}{3k\Omega} + \frac{1}{2k\Omega} + \frac{1}{1.2k\Omega} = \frac{1}{6k\Omega} (2+3+5) = \frac{10}{6k\Omega}$$

$$= \frac{5}{3k\Omega}$$

$$\text{and } \frac{1}{1.8k\Omega} + \frac{1}{1.2k\Omega} + \frac{1}{3.6k\Omega} = \frac{1}{7.2k\Omega} (4+6+2)$$

$$= \frac{12}{7.2k\Omega} = \frac{10}{6k\Omega} = \frac{5}{3} k\Omega$$

Our signs become:

$$V_1 \left( \frac{5}{3k\Omega} \right) + V_2 \left( -\frac{1}{1.2k\Omega} \right) = 15mA$$

$$V_1 \left( \frac{-1}{1.2k\Omega} \right) + V_2 \left( \frac{5}{3k\Omega} \right) = 0mA$$

Mult both sides by  $6k\Omega$ :

$$V_1 (10) + V_2 (-5) = 90V$$

$$V_1 (-5) + V_2 (10) = 0V \quad \text{or} \quad V_1 = 2V_2$$

$$2V_2 (10) + V_2 (-5) = 90V$$

$$15V_2 = 90V$$

$$V_2 = 6V \quad \text{and} \quad V_1 = 12V$$

b)  $P_{2k\Omega} = (V_1 - 10V)^2 / 2k\Omega = 2mW$