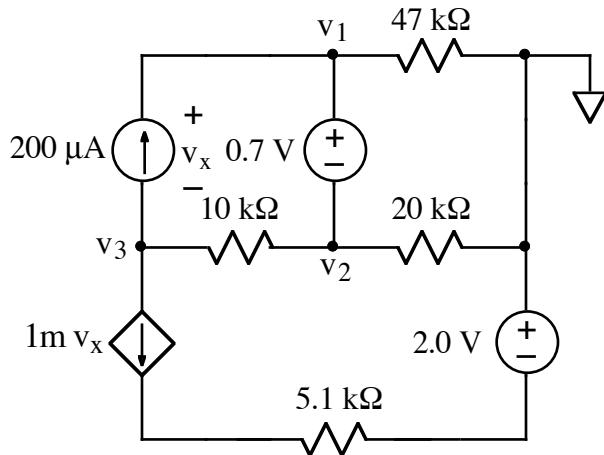


Ex:Use the node-voltage method to find v_1 , v_2 , and v_3 .

Sol'n: We have v_1 , v_2 supernode since v_3 is a node without resistor is between nodes. Thus, we sum all currents out of bubble, (arrows),

$$-200 \mu\text{A} + \frac{v_1 - 0V}{47\text{k}\Omega} + \frac{v_2 - v_3}{10\text{k}\Omega} + \frac{v_3 - 0V}{20\text{k}\Omega} = 0A$$

We add a v -drop eq'n:

$$v_2 + 0.7V = v_1$$

Then we finish with the current sum for node v_3 :

$$200 \mu\text{A} + \frac{v_3 - v_2}{10\text{k}\Omega} + \frac{1m \cdot (v_1 - v_3)}{5.1\text{k}\Omega} = 0A$$

↗ *v_x in terms of node v_1 's*
added to make units correct

Now we do the algebra: (1st & 3rd eqns first)

$$V_1 \cdot \frac{1}{47k\Omega} + V_2 \left(\frac{1}{10k\Omega} + \frac{1}{20k\Omega} \right) + V_3 \left(-\frac{1}{10k\Omega} \right) = 200 \mu A$$

$$V_1 \cdot 1m + V_2 \left(\frac{1}{10k\Omega} - 1m \right) + V_3 \left(\frac{1}{10k\Omega} \right) = -200 \mu A$$

Multiply both sides by $20k\Omega$ to clear most fractions:

$$V_1 \frac{20k\Omega}{47k\Omega} + V_2 \cdot 3 + V_3 (-2) = 4V$$

$$V_1 \cdot 20 + V_2 (-2) + V_3 (\cancel{2} - \cancel{2}) = -4V$$

Use v-drop eqn to substitute for V_1 :

$$(V_2 + 0.7V) \frac{20}{47} + V_2 (3) + V_3 (-2) = 4V$$

$$(V_2 + 0.7) \frac{20}{47} + V_2 (-2) + V_3 (-18) = -4V$$

 Now multiply 1st eqn by (-9) and sum eqns:

$$+ (-9)(V_2 + 0.7V) \frac{20}{47} + (-9)V_2 (3) + (-9)V_3 (-2) = (-9)4V$$

$$\Rightarrow \frac{(V_2 + 0.7V)(-9) \frac{20}{47} + 20}{47} + V_2 (-29) = -40V$$

$$\Rightarrow V_2 \left(\frac{(-9) \frac{20}{47} + 20 - 29}{47} \right) = -40V - 0.7 \left[(-9) \frac{20}{47} + 20 \right] V$$

$$\text{or } V_2 (-9) \left(\frac{20}{47} + 1 \right) = -40V - 0.7 \left[(-9) \left[\frac{20}{47} + 1 \right] + 29 \right] V$$

$$\text{or } V_2 (-9) \left[\frac{20}{47} + 1 \right] = -40V - 0.7(29)V - 0.7 \left[\frac{20}{47} + 1 \right] V$$

$$\text{or } V_2 = \frac{-40V - 0.7(29)V - 0.7V}{-9 \left(\frac{20}{47} + 1 \right)}$$

$$= \frac{-\frac{400}{10} - \frac{29}{10}V - 0.7V}{-9 \cdot \frac{67}{47}}$$

$$= \frac{-60.3}{(-9)10} \cdot \frac{47}{67} V - 0.7V$$

$$= -\frac{9}{-9} \cdot \frac{47}{10} V - 0.7V$$

$$= 4.7V - 0.7V$$

$$V_2 = 4.0 V$$

$$V_1 = V_2 + 0.7V = 4.7V$$

$$V_1 \left(\frac{20}{47} \right) + V_2 \left(+\frac{3}{5} \right) + V_3 (-2) = 4V$$

$$4.7 \left(\frac{20}{47} \right) + 4 \cdot \frac{3}{5} + V_3 (-2) = 4V$$

$$\text{or } V_3 = 5V$$