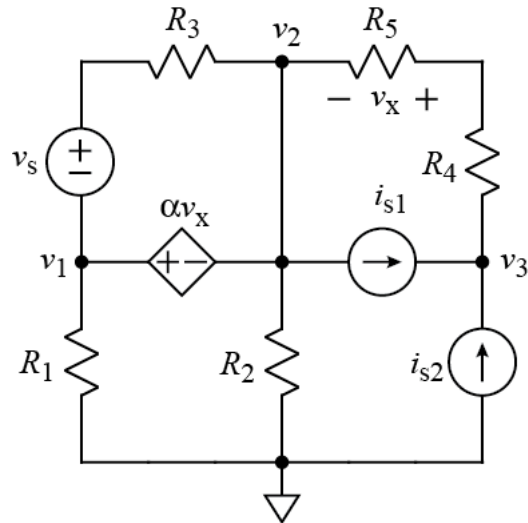


Ex:



For the circuit shown, start with three independent equations for the node-voltages, v_1 , v_2 , and v_3 . The quantity v_x must not appear in the equations. Only component and source names may appear in answer.

Make at least one consistency check (other than a units check) on your three equations. In other words, choose component values that make the values of v_1 , v_2 , and v_3 obvious, and verify that your answer to problem 1 gives these values. State the values of resistors and sources for your consistency check.

SOL'N: Many solutions are possible. One possible check is as follows:

$$R_2 = \infty, R_3 = \infty, i_{s1} = 0,$$

$$R_1 = 1\Omega, R_4 = 4\Omega, R_5 = 5\Omega,$$

$$v_s = 24\text{ V}, \alpha = 12, i_{s2} = 6\text{ A}$$

With these choices of values, we have open circuits for R_2 and R_3 , and current source i_{s2} in series with R_4 , R_5 , and R_1 . By Ohm's law, we get the following v-drops (with + on top of R_1 and + on bottom of R_4):

$$v_{R1} = 6\text{ V}, v_{R4} = 24\text{ V}, v_{R5} = 30\text{ V}$$

We also have the v-drop for the dependent source as follows:

$$\alpha v_x = 12(30)\text{ V} = 360\text{ V}$$

Following v-drops from the reference = 0V, up through R_1 , through the dependent source, through R_4 and R_5 , we find the node v's:

$$v_1 = v_{R1} = 6 \text{ V}$$

$$v_2 = v_1 - \alpha v_x = 6 \text{ V} - 360 \text{ V} = -354 \text{ V}$$

$$v_3 = v_2 + v_{R5} + v_{R4} = -354 \text{ V} + 30 \text{ V} + 24 \text{ V} = -300 \text{ V}$$

Now we plug the numbers into the equations from node-v analysis to see if we get equality:

$$v_1 - \alpha(v_3 - v_2) \frac{R_5}{R_4 + R_5} = v_2$$

$$\frac{v_1}{R_1} + \frac{v_1 + v_s - v_2}{R_3} + \frac{v_2}{R_2} + \frac{v_2 - v_3}{R_4 + R_5} = 0 \text{ V}$$

$$-i_{s1} - i_{s2} + \frac{v_3 - v_2}{R_4 + R_5} = 0 \text{ A}$$

or


$$6 \text{ V} - 12(-300 - -354) \frac{5}{4 + 5} = -354, \quad 6 - 12(54) \frac{5}{9} = 6 - 12(30) = -354 \quad \checkmark$$

$$\frac{6 \text{ V}}{1 \Omega} + \frac{6 \text{ V} + 24 \text{ V} - -354 \text{ V}}{\infty} + \frac{-354 \text{ V}}{\infty} + \frac{-354 \text{ V} - -300 \text{ V}}{4 \Omega + 5 \Omega} = 0 \text{ V}, \quad 6 \text{ A} - \frac{54 \text{ V}}{9 \Omega} = 0 \text{ V} \quad \checkmark$$

$$-0 \text{ A} - 6 \text{ A} + \frac{-300 - -354 \text{ V}}{4 \Omega + 5 \Omega} = 0 \text{ A}, \quad -6 \text{ A} + \frac{54 \text{ V}}{9 \Omega} = 0 \text{ A} \quad \checkmark$$

The equations hold true for this example. The node-v equations pass this consistency check.

(b) Using mesh currents:

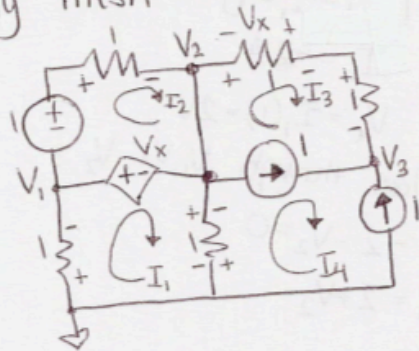

$$I_4 = -1$$

$$1 = I_4 - I_3$$

$$\therefore I_3 = I_4 + 1 = -2$$

$$V_x = -I_3(1) = +2$$

$$V_1 = -1(I_1)$$

$$V_2 = V_1 - V_x$$

$$V_3 = V_2 - I_3(2)$$

$$-1(I_1) - V_x - 1(I_1) + 1(I_4) = 0$$

$$I_1(2) = (-1) - 2 = -\frac{3}{2}$$

$$\therefore V_1 = +\frac{3}{2} \checkmark \text{ same as eq. set } (V_1 = \frac{6}{4} = \frac{3}{2})$$

$$V_2 = V_1 - V_x = \frac{3}{2} - \frac{4}{2} = -\frac{1}{2} \checkmark \text{ same as eq. set } (V_2 = -\frac{2}{4} = -\frac{1}{2})$$

$$\sum I \text{ at } V_3: -I_3 - 1 - 1 = 0 \Rightarrow I_3 = -2$$

$$V_3 = V_2 - I_3(2) = -\frac{1}{2} + \frac{8}{2} = \frac{7}{2} \checkmark \text{ same as eq. set } (V_3 = \frac{14}{4} = \frac{7}{2})$$

Alternative way: Create 1 pathway to ground \Rightarrow

$$R_1 = 1, \alpha = 0, R_3 = \infty, I_{s1} = I_{s2} = 0, R_2 = \infty, R_4 = R_5 = 1$$


$$\therefore \text{From eq. set: } ① (V_1 - V_2) = 0 \Rightarrow V_1 = V_2$$

$$② V_1 + 0 - 0 + 0 + 0 + \frac{(V_2 - V_3)}{2} = 0$$

$$\left(\frac{V_2 + V_2}{2}\right) = \frac{V_3}{2} \Rightarrow V_2 = \frac{V_3}{2} \cdot \frac{2}{3}$$

$$③ -0 - 0 - \frac{(V_2 - V_3)}{2} = 0 \Rightarrow V_2 = V_3$$
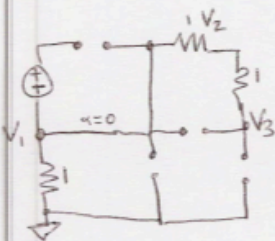
$$\therefore V_2 = \frac{V_2}{3} \Rightarrow V_2\left(\frac{3}{3} - \frac{1}{3}\right) = 0 \Rightarrow V_2 = 0 \text{ so } V_1 = V_3 = 0$$



Since no source
then $V_1 = V_2 = V_3$ because
no I flow (open wire)