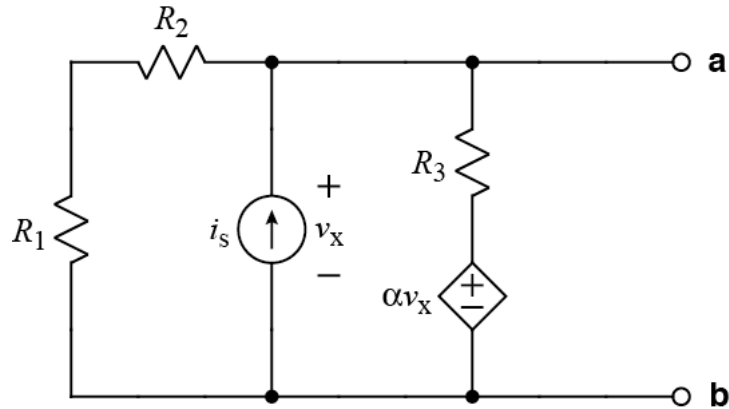


Ex:



Find the Thevenin equivalent circuit at terminals a-b. v_x must not appear in your solution. The expression must not contain more than circuit parameters α , R_1 , R_2 , R_3 , and i_s . **Note:** $0 < \alpha < 1$.

SOL'N:

① Find V_{th} : (Top node is V_{th})

$$+\frac{V_{th}}{R_1+R_2} - I_s + \frac{V_{th} - \alpha V_x}{R_3}$$

$$V_x = V_{th}$$

$$\therefore V_{th} \left(\frac{1}{R_1+R_2} + \frac{1}{R_3} - \frac{\alpha}{R_3} \right) = I_s$$

$$V_{th} = \frac{I_s R_3 (R_1+R_2)}{R_3 + (R_1+R_2)(1-\alpha)}$$

② Find R_{th} :
method using I_{sc}

$V_x = 0$
 $I_{sc} = I_s$

$$\therefore R_{th} = \frac{V_{th}}{I_{sc}} = \frac{R_3 (R_1+R_2)}{R_3 + (R_1+R_2)(1-\alpha)}$$