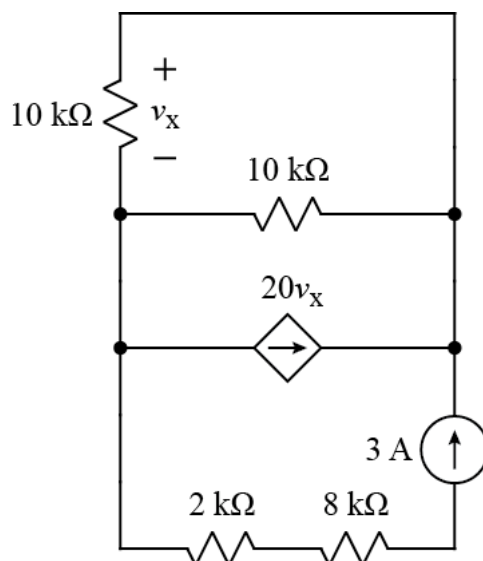


Ex:



Calculate the power dissipated by the dependent current source, (labeled  $20v_x$ ).

SOL'N:

using node-voltage:

$$+3 + 20V_x + \frac{V_1}{10k} + \frac{V_1}{10k} = 0$$

$$V_1 = V_x$$

$$\therefore V_1 (20 + \frac{1}{10k} + \frac{1}{10k}) = -3$$

$$V_1 = \frac{-3(10k)}{20(10k) + 2} \cong -150mV$$

$$\text{power} = (20V_x) V_x = 20(150m)^2 = \boxed{450mW}$$

positive means absorbing power