
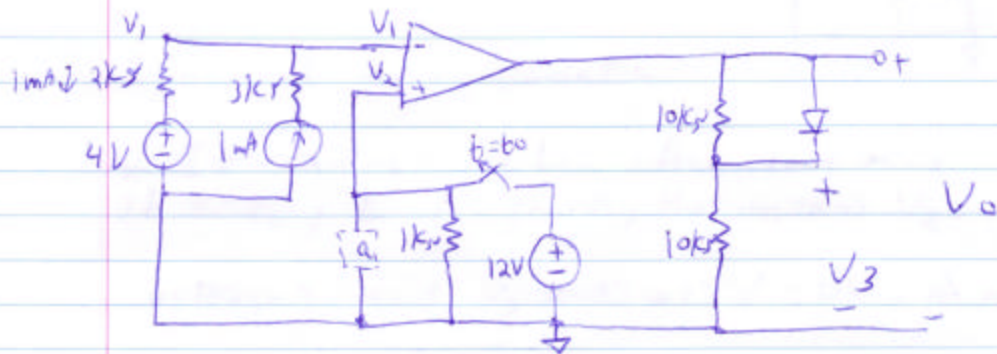


## Homework #10 Solutions

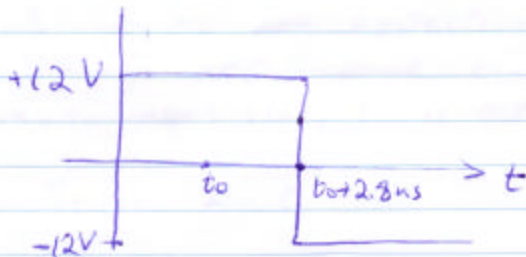

Rail voltages =  $\pm 12$



a) Choose either an R, C, or L to go in box  $\alpha$  to produce the  $V_o(t)$  shown above.


For  $V_o$  to be  $+12V$   $V_2$  should be more than  $V_1$ ;  $V_2 > V_1$ . When  $V_2$  drops below  $V_1$ ,  $V_o$  will switch from  $+12V$  to  $-12V$ .

First we need  $V_1$

note that no current goes into the opamp

so the 1mA current goes into the  $2k\Omega$  and  $3k\Omega$  resistors so

$$V_1 = +4V + 1mA \times 2k\Omega = 6V$$

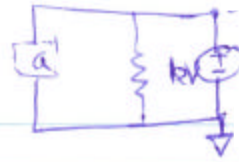

To Find the component:-

\* It can not be L after long time  
 At  $t = t_0^-$ , L is short, that means  $V_2 = 0V = +12V??$

• A node

cannot have ~~two~~ two voltages. It is not L

\* Since we are expecting the voltage at  $V_2$  to change ~~over~~ over time and not instantaneously, it is not a R

\* It is a C

$$V_C(t_0^-) = +12$$

$$V_C(t_0^+) = +12V \quad (\text{initial value})$$

$$V_C(t_0 \rightarrow \infty) = 0V \quad (\text{final value})$$

$$\tau = RC = 1\mu s$$

$$V_C(t) = V_f + (V_i - V_f) e^{-t/\tau}$$

$$= 12 e^{-t/\tau}$$

$$= +12 e^{-t/\tau}$$

if we take  $t_0 = 0 s$   $\frac{2.8 \mu s}{\tau}$

$$V(2.8 \mu s) = +12$$

At  $2.8 \mu s$   $V_2 = V_1 = 6$  (Vo switches to -12)

$$\Rightarrow +12e^{-\frac{2.8 \text{ ms}}{\tau}} = 6$$


$$\Rightarrow e^{-\frac{2.8 \text{ ms}}{\tau}} = \frac{6}{12}$$

$$-\frac{2.8 \text{ ms}}{\tau} = \ln \frac{1}{2}$$


$$\tau = \frac{-2.8 \text{ ms}}{-0.693} = 4.04 \text{ ms}$$

$$C = \frac{4.04 \text{ ms}}{1 \text{ k}\Omega} = 4.04 \mu\text{F}$$

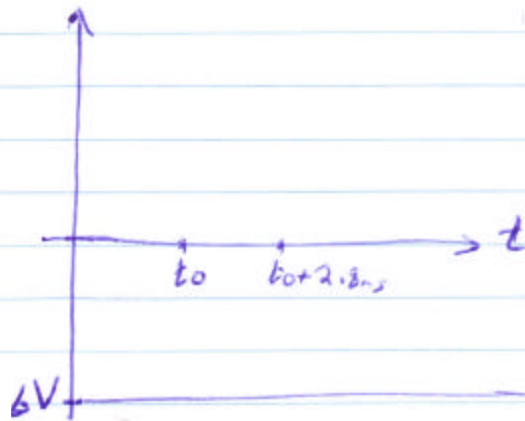b)  $V_o(t)$  is not going to change over time



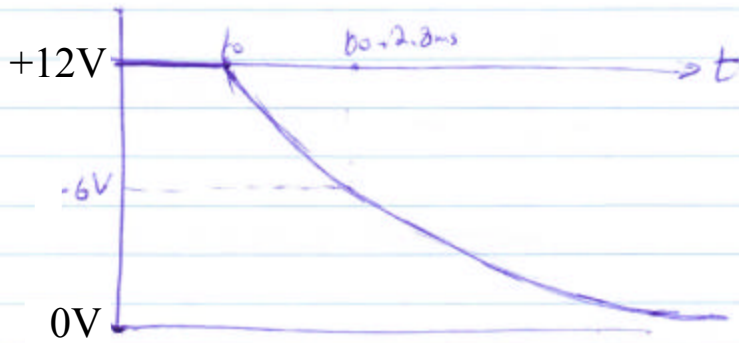2 a)  $v_2(t)$  is going to discharge exponentially from 0 to -12V




b)  $v_3(t)$   
 when  $V_0 = 12\text{V}$ , the diode is forward biased and  $V_3 = V_0 = 12\text{V}$

when  $V_0 = -12\text{V}$ , the diode is reverse biased

and  $V_3 = \dots = -6\text{V}$

drop across 1k $\Omega$

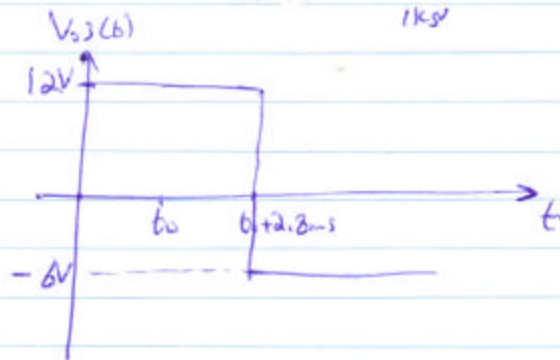

3.  $I_x = 0$

$I_1 = 20 \exp^{(45)} / (j6k - j2k) = 20 \exp^{(45)} / j4k = 5 \exp^{(45-90)}$

$I_1 = 5 \exp(-45) \text{A}$

$i_1(t) = 5 \text{m} \cos(52t - 45) \text{A}$