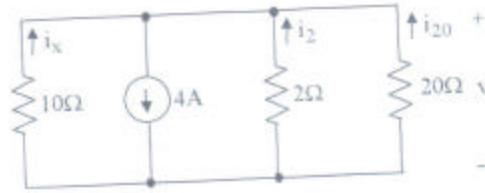


1.



- (a) Calculate  $i_x$ ,  $i_2$ , and  $v$ .  
 (b) Find the power dissipated for every component including the current source.

First we name all voltages and currents. Make sure you indicate the direction of each current and + and - ends of each voltage.



- We equate all voltages in parallel

$$v_x = v_2 = v$$

using Ohm's Law

$$v_x = 10\Omega \cdot i_x$$

$$v = 20\Omega \cdot i_{20}$$

$$v_2 = 2\Omega \cdot i_2$$

$$\text{since } v_x = v \Rightarrow i_{20} = \frac{10\Omega \cdot i_x}{20\Omega} = \frac{1}{2} i_x \rightarrow \textcircled{1}$$

$$\text{since } v_2 = v \Rightarrow i_2 = \frac{10\Omega \cdot i_x}{2} = 5i_x \rightarrow \textcircled{2}$$

using Currents sum at the upper left node

$$4A - i_x - i_2 - i_{20} = 0 \quad \left( \begin{array}{l} \text{if current is} \\ \text{going in the node} \\ \text{it's } (-), \text{ out} \\ \text{of the node is } (+) \end{array} \right)$$

substituting for  $i_2$  and  $i_{20}$  from (1) and (2), we get

$$4A - i_x - 5i_x - \frac{1}{2}i_x = 0$$

$$4A = \frac{13}{2} i_x$$

$$i_x = \frac{8}{13} A$$

From eq. (1)

$$i_2 = 5i_x = 5 \times \frac{8}{13} A = \frac{40}{13} A$$

$$V = 10V \cdot -i_x = 10V \cdot -\frac{8}{13} A = -\frac{80}{13} V$$

(b) Power Dissipation

$$P_{(10V)} = -i_x V_x = \frac{8}{13} \times \frac{-80}{13} = \frac{640}{169} W$$

(The negative sign is because  $i_x$  goes from - to +)


$$P_{(20V)} = -i_{20} V = -\frac{1}{2} i_x V = -\frac{8}{2 \times 13} \times \frac{-80}{13} = \frac{320}{169} W$$

$$P_{(25)} = -i_2 v = -\frac{40}{13} \times \frac{-80}{13} = \frac{3200}{169} \text{ W}$$

$$P_{(4A)} = v \times 4A = \frac{-80}{13} \times 4 = \frac{-320}{13} \text{ W}$$


The power is negative which means  
it is a source. It is generating (or supplying) power.

2

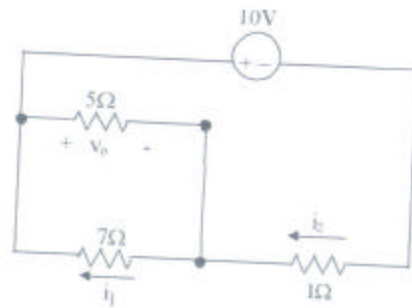Calculate  $i_1$ ,  $i_2$ , and  $v_0$ .

3.

First we name all voltages and currents

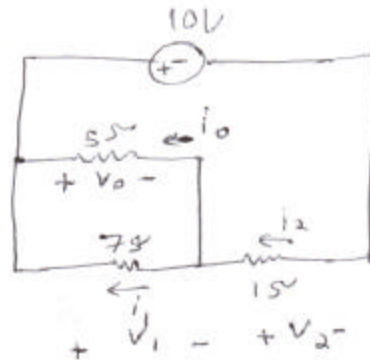

Voltage Loops:-

- inner loop:-  $V_0 - V_1 = 0$ 

$$V_0 = V_1$$

we can also notice that the resistors are in parallel and the voltages across are equal.

using Ohm's Law:-  $5\Omega \cdot i_0 = -7\Omega \cdot i_1 \Rightarrow i_0 = \frac{7}{5} i_1$  --- (1)

- outer loop:-  $10V - V_1 - V_2 = 0$ Substituting for  $V_1$  and  $V_2$  using Ohm's Law

$$10V = V_1 + V_2$$

$$= -7\Omega \cdot i_1 - 15\Omega \cdot i_2 \quad \text{(2)}$$

(The negative sign is because  $i$  goes from - to +)

- Current Sum

summing the current at the center bottom node:-

$$i_2 - i_1 - i_0 = 0$$

$$i_2 = i_0 + i_1$$

using ①

$$i_2 = \frac{7}{5} i_1 + i_1 = \frac{12}{5} i_1$$

substituting for  $i_2$  in ②

$$\begin{aligned} 10 \text{ V} &= -7 \text{ S} \cdot i_1 - 15 \text{ V} \cdot i_2 \\ &= -7 \text{ S} \cdot i_1 - 1 \text{ S} \cdot \frac{12}{5} i_1 \end{aligned}$$


$$10 = \frac{-35 - 12}{5} i_1$$

$$i_1 = \frac{-50}{47} \text{ A}$$

$$i_2 = \frac{12}{5} i_1 = \frac{12}{5} \times \frac{-50}{47} \text{ A} = \frac{-120}{47} \text{ A}$$


$$V_0 = V_1 = -7 \text{ S} \cdot i_1 = -7 \times \frac{-50}{47} = \frac{350}{47} \text{ V}$$

3.

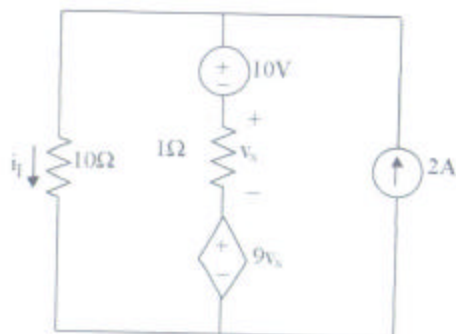

Find  $v_x$ ,  $i_1$ , and the power dissipated by the dependent source.

- Name all voltages and currents

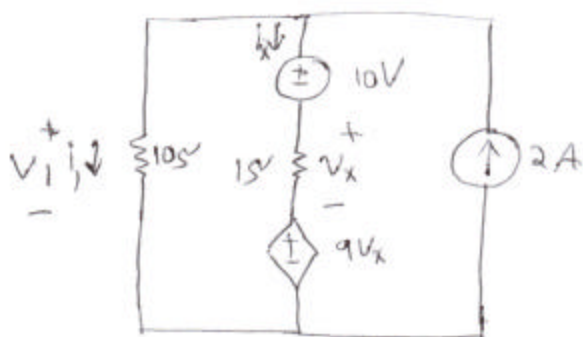

- Voltage Loops:

The left loop:  $10V - v_1 + 9V_x + V_x = 0$   
 $10V - v_1 + 10V_x = 0$

using Ohm's Law:

$$10V = v_1 - 10V_x$$

$$10V = 10\Omega \cdot i_1 + 10 \cdot 1\Omega \cdot i_x \rightarrow \textcircled{1}$$

- Currents, Same

$$2A - i_x - i_1 = 0$$

$$2A = i_x + i_1$$

$$i_1 = 2A - i_x \rightarrow \textcircled{2}$$

Substituting for  $i_1$  in (1)

$$10V = 10S \cdot (2A - i_x) - 10 \cdot 1S \cdot i_x$$

$$10V = 20AS - 10S \cdot i_x - 10S \cdot i_x$$

$$10V = 20AS - 20S i_x$$

$$20 i_x = 20 - 10$$

$$i_x = \frac{10}{20} = \frac{1}{2} A$$

$$V_x = i_x \cdot 1S = \frac{1}{2} V$$

$$i_1 = 2A - i_x = 2 - \frac{1}{2} = \frac{3}{2} A$$

- Power Dissipation by the dependent source

$$P = IV = i_x (9V_x) = \frac{1}{2} \times 9 \times \frac{1}{2} = \frac{9}{4} W$$