


UNIVERSITY OF UTAH  
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1270


HOMEWORK #2

Spring 2008

1. Calculate  $V_1$ .

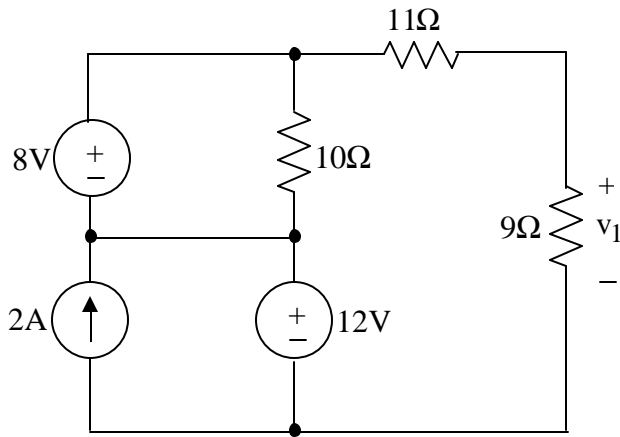


2. Calculate  $i_1$ .

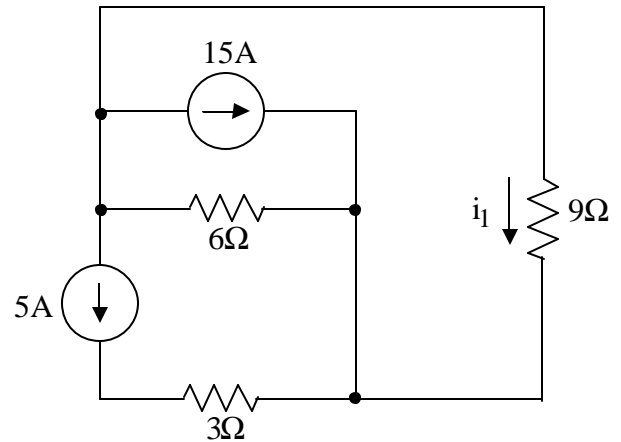


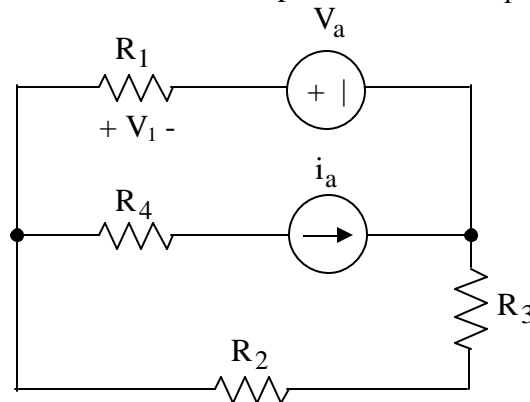3. Derive an expression for  $V_1$ . The expression must contain no other parameters than  $R_1, R_2, R_3, i_a$ , and  $V_a$ .

(Hint: It is NOT just a voltage divider.)




4.

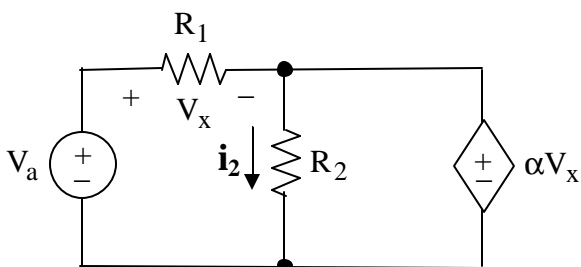

a) Derive the expression for  $i_2$  containing not more than circuit parameters  $\alpha, R_1, R_2$ , and  $V_a$ .

b) State the symbolic expression for power in the resistor,  $R_2$ . Use only  $\alpha, R_1, R_2$ , and  $V_a$  in the expression.

5.

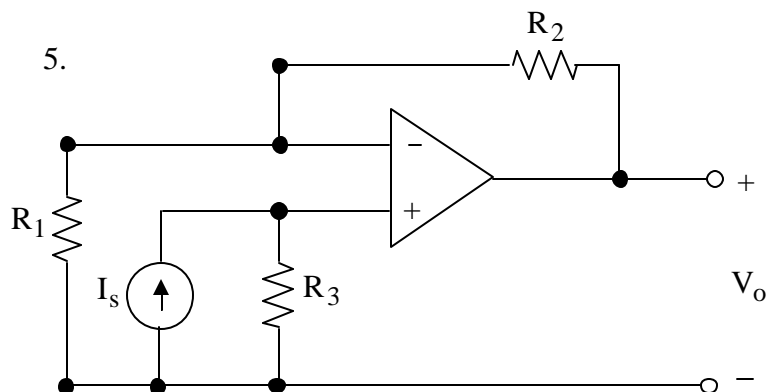

The op-amp operates in the linear mode. Using an appropriate model of the op-amp, derive an expression for  $V_o$  in terms of not more than  $I_s, R_1, R_2$ , and  $R_3$ .