


UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1270

HOMEWORK #6

Spring 2008

1.

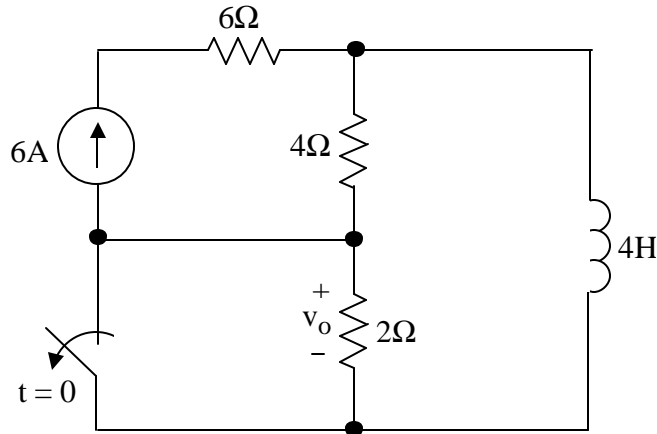


After being closed for a long time, the switch opens at $t = 0$.

Calculate the energy stored on the inductor as $t \rightarrow \infty$.

2. Use the circuit in 1 above to write a numerical expression for $v_o(t)$ for $t > 0$.


3.

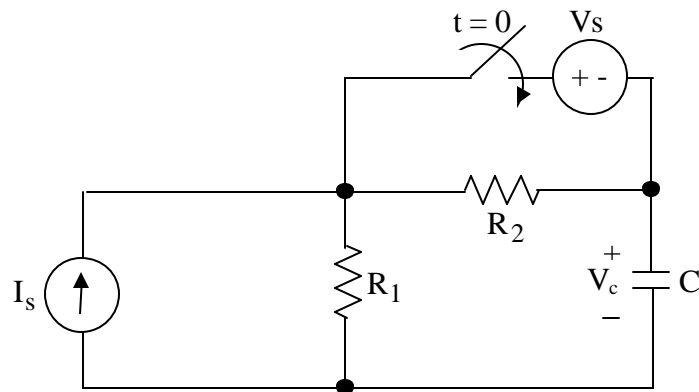

After being open for a long time, the switch closes at $t = 0$.


- a) Write an expression for $V_c(t = 0^+)$
- b) Write an expression for $V_c(t > 0)$ using not more than R_1 , R_2 , V_s , I_s , and C .

4.

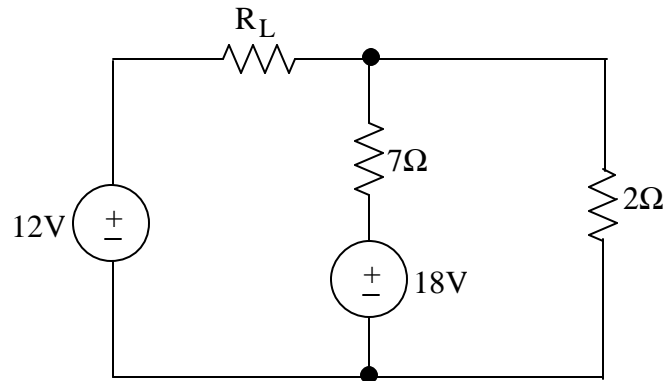

- a) Calculate the value of R_L that would absorb maximum power.
- b) Calculate that value of maximum power R_L could absorb.

5.

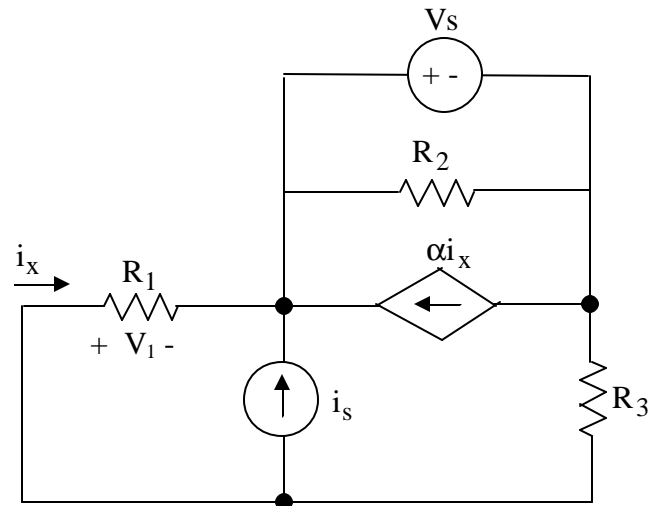

Using superposition, derive an expression for V_1 that contains no circuit quantities other than i_s , V_s , R_1 , R_2 , R_3 , and α , where $\alpha > 0$.