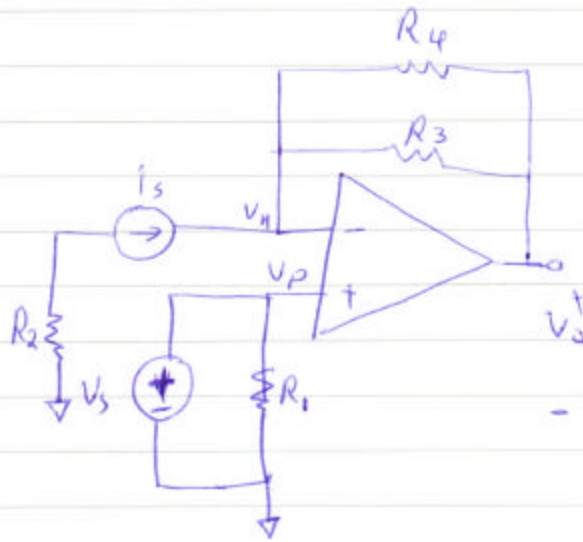


1)



Derive symbolic expression for  $V_o$

in linear mode  $V_n = V_p$

$$V_p = V_s$$

since no current goes into the op-amp,

$i_s$  passes through to  $R_3 \parallel R_4$

$$V_o = V_n - i_s (R_3 \parallel R_4)$$

$$\Rightarrow V_o = V_s - i_s (R_3 \parallel R_4)$$

2) a) if  $i_s = 0$   
 $V_n = V_p = V_s = 1$



since no current is flowing from  $V_n$  to  $V_o$   
 $V_o = V_n = 1V$

any value of  $R_1$  would not change the value at  $V_p$  or  $V_n$  or  $V_o$  because the voltage across  $R_1$  will always be equal to  $V_s$  as  $V_s$  is in parallel to  $R_1$ .

b) when  $V_s = 0$ , we can use the expression we derived before

$$V_o = V_s - i_s (R_3 \parallel R_4)$$

$$-1 = 0 - i_s (10K \parallel 10K)$$


$$\Rightarrow -1 = 0 - 5k i_s$$

$$\Rightarrow i_s = \frac{1}{5k} = 0.2 \text{ mA}$$

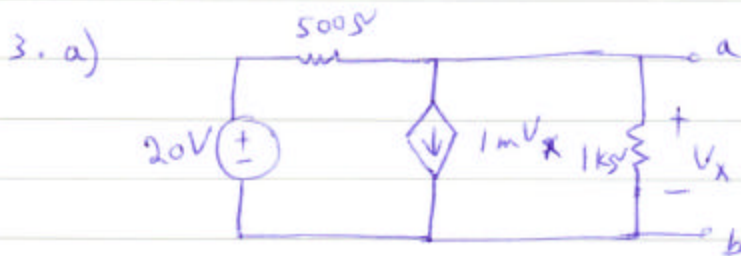c)  $R_{in} = V_s / i_1 = R_1$

$$\Rightarrow R_{in} = R_1$$

whatever the value we choose for  $R_1$  is our input resistance



we can replace the dependant source with an equivalent resistance

$$R = \frac{V}{I} = \frac{V_x}{1mV_x} = 1k\Omega$$


The circuit becomes:



$$\begin{aligned} V_{th} = V_x &= 20V \times \frac{1k\Omega // 1k\Omega}{1k\Omega // 1k\Omega + 500} \\ &= 20 \times \frac{500}{500 + 500} = 10V \end{aligned}$$

$$\begin{aligned} R_{th} &= (1k\Omega // 1k\Omega) // 500\Omega \\ &= 500\Omega // 500\Omega \\ &= 250\Omega \end{aligned}$$

a) other solutions

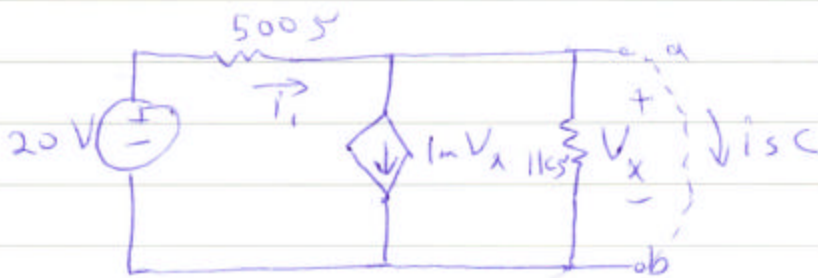

sum loop Voltages

$$20V - 500i_1 - V_x = 0 \quad \text{--- (1)}$$

node currents

$$i_1 = 1mV_x + \frac{V_x}{1k\Omega}$$

$$\Rightarrow i_1 = 1mV_x + 1mV_x = 2mV_x$$

substituting into (1)

$$20 - 500 \times 2mV_x - V_x = 0$$

$$\Rightarrow 20 - 2V_x = 0$$

$$\Rightarrow V_x = 10V$$

$$V_{th} = V_x = 10V$$

$$i_{sc} = \frac{20V}{500\Omega} = 40mA$$

$$R_{th} = \frac{V_{th}}{i_{sc}} = \frac{10}{40mA} = 250\Omega$$

$$\begin{aligned} \text{b) } R_L \text{ that would absorb maximum power} &= R_{th} \\ &= 250 \Omega \end{aligned}$$

$$\begin{aligned} \text{c) The maximum power} &= \frac{V_L^2}{4R_L} = \frac{10^2}{4 \times 250} = \frac{100}{1000} \\ &= 0.1 \text{ W} \end{aligned}$$