


UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1270

HOMEWORK #1 Solution

Summer 2007


1.

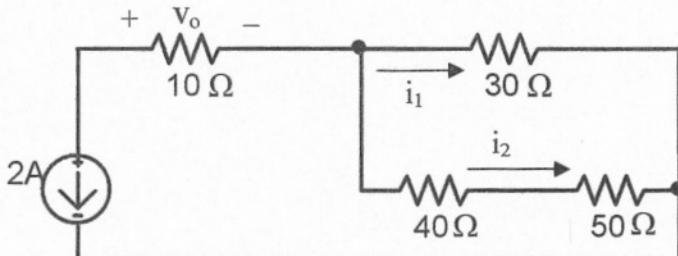

(a) Calculate i_1 , i_2 , and V_o .

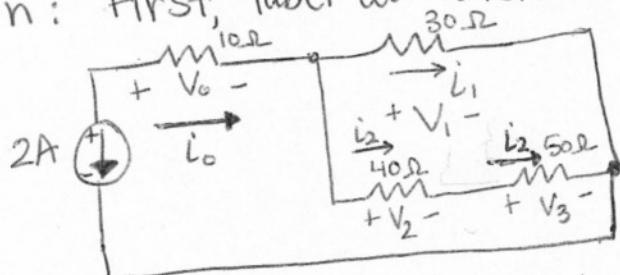(b) Find the power dissipated for every component including the current source.

Sol'n: Step 1: First, label all resistors to have current and voltage



Step 2: Next write eq. for wanted unknowns:

- Ohm's law $\Rightarrow \textcircled{1} V_o = i_0(10)$

- $\textcircled{2} V_1 = i_1(30)$

- $\textcircled{3} V_2 = i_2(40)$

- $\textcircled{4} V_3 = i_2(50)$

- V_{loop} equation \Rightarrow (remember to avoid taking a V_{loop} with the current source in it)

$$\textcircled{5} +V_3 +V_2 -V_1 = 0$$

- I sum equation $\Rightarrow \textcircled{6} -i_0 +i_1 +i_2 = 0$

- Since only one current can flow in a branch \Rightarrow

$$i_0 = -2A$$

$$\therefore V_o = -2(10) = \boxed{-20V}$$

#1 (cont.)

• Need to solve for i_1 and i_2 . Knowing i_0 , eq. ⑥ is

$$⑦ i_1 + i_2 = -2A$$

→ Need another eq. with just i_1 and i_2 in it \Rightarrow

• Use ⑤ with ②, ③ and ④ in it:

$$⑧ i_2(50) + i_2(40) - i_1(30) = 0$$

• We now have 2 eq. and 2 unknowns \rightarrow
 \downarrow \downarrow
 ⑦ and ⑧ i_1, i_2

$$i_1 = (-2 - i_2)$$

$$i_2(90) - 30(-2 - i_2) = 0$$



$$i_2(90) + 60 + 30i_2 = 0$$

$$i_2(120) = -60$$

$$\therefore i_2 = -\frac{60}{120} = -\frac{1}{2} A$$

$$i_1 = (-2 - i_2) = -2 - \frac{1}{2} = -2\frac{1}{2} A$$

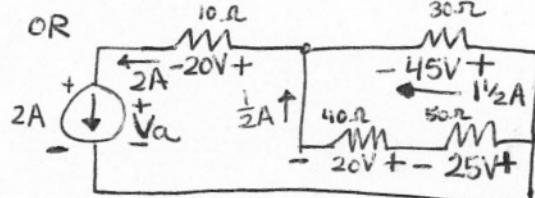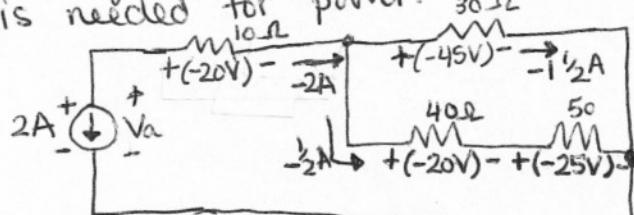From eq. ②, ③, and ④ we know all v's across R's. The voltage across the
 2A is needed for power:




$$+V_a + 20 + 45 = 0$$

$$V_a = -65V$$


	absorbed	delivered
2A src.		$-(65)(2) = -130W$
10 ohm	$+20(2) = 40W$	
30 ohm	$45(1\frac{1}{2}) = 67.5W$	
40 ohm	$(20)(1.5) = 30W$	
50 ohm	$25(1.5) = 37.5W$	
Total	$+130W$	$-130W$

delivered = absorbed

2.

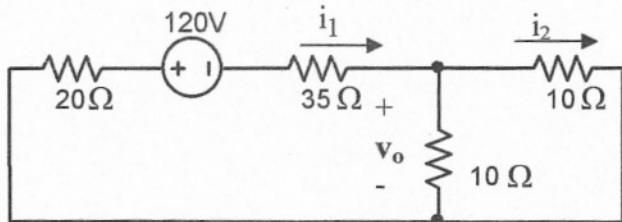Calculate i_1 , i_2 , and v_o .

- ① Label all R's with an I and V

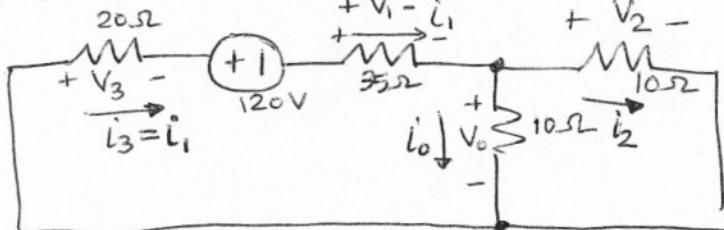

Note that only 1 current can be in a branch \Rightarrow
 $i_1 = i_3$

- ② Ohm's Law:

$$V_3 = i_1 (20)$$

$$V_1 = i_1 (35)$$

$$V_0 = i_0 (10)$$

$$V_2 = i_2 (10)$$

- ③ V loops \Rightarrow

$$+V_0 - V_2 = 0 \Rightarrow V_0 = V_2$$

$$+V_0 + V_1 + V_3 + 120 = 0$$

- ④ Current Sum \Rightarrow

$$-i_1 + i_0 + i_2 = 0$$

Now we need to get eq. with the same variables.
 \rightarrow Replacing V_2 with $V_0 \Rightarrow$ from ohm's laws:

$$V_0 = i_0 (10) \text{ and } V_0 = i_2 (10)$$

$$\therefore i_0 (10) = i_2 (10) \text{ so } i_0 = i_2 \quad \text{⑤}$$

\rightarrow Replacing V_0, V_1, V_3 to be in terms of i_0 and i_1 gives another eq.

$$i_0 (10) + i_1 (35) + i_1 (20) + 120 = 0$$

$$i_0 (10) + i_1 (55) + 120 = 0 \quad \text{⑥}$$

Using ④, ⑤, and ⑥ { put ⑤ into ④ and solve for i_1 }

$$-i_1 + 2i_0 = 0 \Rightarrow i_1 = 2i_0 \quad \{ \text{now put this eq. into ④} \}$$

$-2i_0 + 2i_0 = 0$ (See what happens when you put into the wrong eq. \rightarrow No sol.) \rightarrow put into ⑥

#2 (Cont.)

$$i_1 = 2i_0 \quad i_0 = i_2$$

(6) $i_0(10) + 2i_0(55) + 120 = 0$

$$120(i_0) = -120/120$$

$$i_0 = -1 \text{ A}$$


$$i_0 = i_2 = -1 \text{ A}$$

$$i_1 = 2i_0 = -2 \text{ A}$$

$$V_0 = i_0(10) = -10 \text{ V}$$

$$2\hat{i}_3 + 10m = \hat{i}_x$$

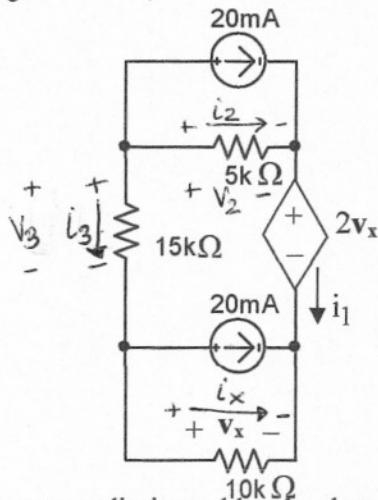3. ① Label all R's with a current and a voltage.



Find v_x , i_1 , and the power dissipated by the dependent source.

2. a. Write Ohm's Law eq:

$$\textcircled{1} \quad V_x = i_x(10k)$$

$$\textcircled{2} \quad V_3 = i_3(15k)$$

$$\textcircled{3} \quad V_2 = (5k) i_2$$

b. V loop eq's: (avoid taking loop through I src's)

$$\textcircled{4} \quad +V_3 - V_2 - 2V_x + V_x = 0$$

c. I summation:

$$\textcircled{5} \quad i_3 + i_2 + 20m = 0$$

$$\textcircled{6} \quad -i_3 + 20m + i_x = 0$$

Eqs. ⑥ and ⑤ contain 3 unknown's. Using these 2 and rewriting ④ in terms of i_2 , i_3 , and i_x gives 3rd eq:

$$\textcircled{7} \quad i_3(15k) - i_2(5k) - 2i_x(10k) + i_x(10k) = 0$$

$$i_3(15k) - i_x(10k) = i_2(5k)$$

Plug this into ⑤:

$$i_3 + [i_3(3) - i_x(2)] + 20m = 0$$

$$4i_3 + 20m = 2i_x$$

$$2i_3 + 10m = i_x$$

#3 (cont.)

⑨ $2i_3 + 10m = i_x \Rightarrow$ plug into ⑥

- $i_3 + 20m + 2i_3 + 10m = 0$

$i_3 + 30m = 0$

$i_3 = -30m A \Rightarrow$ plug back into ⑨

$2(-30m) + 10m = i_x$

$\therefore i_x = -50m A \Rightarrow$ use to find V_x ①

$V_x = i_x (10k) = -50m(10k) = -500 V$

To find $i_1 \Rightarrow$ use current summation

- $i_1 - 20m - i_x = 0$

$i_1 = -20m - (-50m) = +30mA$

power for dependent source \Rightarrow

$P = i_1 (2V_x)$

power = $-(30m)(1,000)$

power = $-30 W$

