


UNIVERSITY OF UTAH  
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1270

HOMEWORK #3

Summer 2007

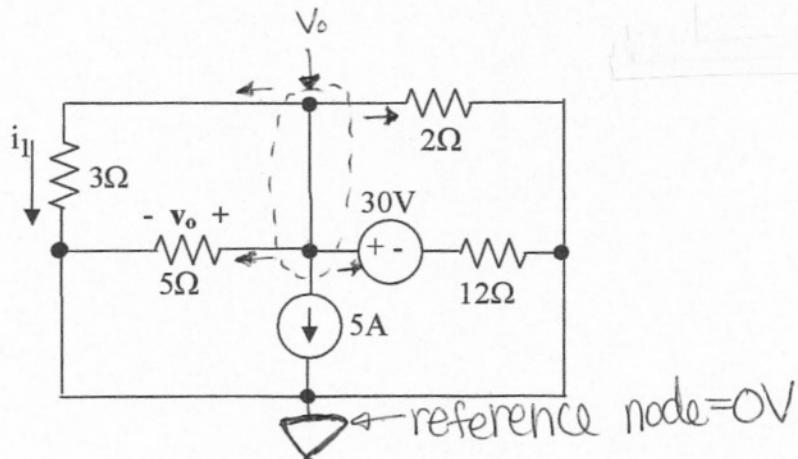1. Use node-voltage method to find  $i_1$  and  $v_o$ .



1. Assign reference node. (Typically to node with most branches connected to it)
2. Assign node voltage to nodes where 3 or more wires are connected.
3. Write current summation eq. for unknown node:


$$\frac{v_o}{3} + \frac{v_o}{5} + 5 + \frac{v_o - 30}{12} + \frac{v_o}{2} = 0$$

$$v_o \left( \frac{1}{3} + \frac{1}{5} + \frac{1}{12} + \frac{1}{2} \right) = \frac{30}{12} - 5$$

$$\therefore v_o = \frac{-150}{67} \quad \Rightarrow \quad i_1 = \frac{v_o}{3} = \frac{150}{67(3)} = \boxed{\frac{50}{67} A}$$

Note: The terms in above eq. are of the form: Voltage of the node we are at with (+) sign, subtract voltage at neighboring node. We divide V-drop by the total R between nodes to find current.

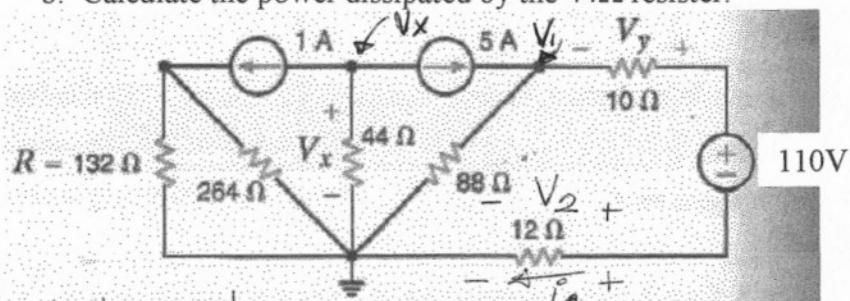2. a. Use the node-voltage method to find  $V_x$  and  $V_y$ .  
 b. Calculate the power dissipated by the  $44\Omega$  resistor.



a. Node-V at  $V_x$  node: ; Node-V at  $V_1$  node:

$$1 + \frac{V_x}{44} + 5 = 0$$

$$\frac{V_x}{44} = -6$$

$$V_x = \boxed{-264V}$$

$$-5 + \frac{V_1}{88} + \frac{V_1 - 110}{(10+2)} = 0$$

$$V_1 \left( \frac{1}{88} + \frac{1}{22} \right) = +5 + \left( \frac{110}{22} \right)$$

$$V_1 = 176V$$

$$+V_1 + V_y - 110 - i_2 (12) = 0 \quad \text{where } i_2 = \frac{(V_1 - 110)}{22}$$


$$+V_1 + V_y - 110 - \frac{(V_1 - 110)}{22} 12 = 0$$

$$V_y = 110 - V_1 + \frac{(V_1 - 110)}{22} 12$$

$$V_y = \boxed{-30V}$$

$$\text{b. power} = V_x \cdot i_{44} = V_x \cdot \frac{V_x}{44} = \frac{V_x^2}{44} = \boxed{+1,584W}$$

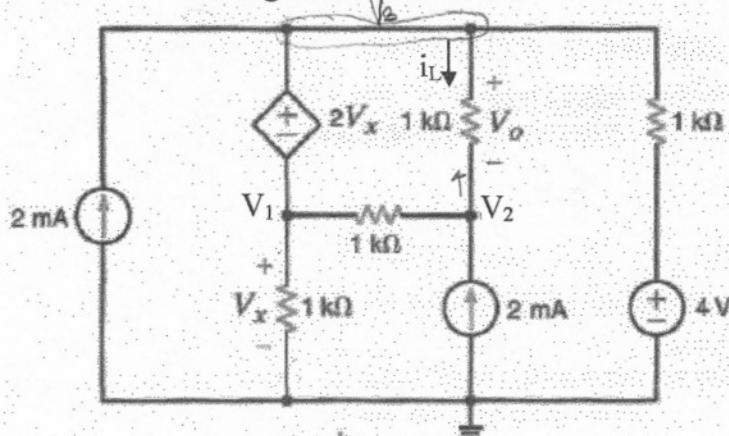3. Use the node voltage to find  $V_1$  and  $V_2$ . Then find  $i_L$ .



$$\begin{aligned} (\text{super node}) \Rightarrow V_3 - V_1 &= 2V_x \\ V_1 &= V_x \end{aligned}$$

$$\therefore V_3 - V_x = 2V_x$$

$$-2m + \frac{V_x}{1k} + \frac{(V_x - V_2)}{1k} + \frac{V_3 - V_2}{1k} + \frac{(V_3 - 4)}{1k} = 0$$

$$\textcircled{1} -2m + \frac{2V_x}{1k} - \frac{V_2}{1k} + \frac{3V_x}{1k} - \frac{V_2}{1k} + \frac{3V_x}{1k} + \frac{-4}{1k} = 0$$

$$\textcircled{2} \frac{(V_2 - V_1)}{1k} - 2m - \frac{V_2}{1k} = 0$$

Combine \textcircled{1} and \textcircled{2}

$$8V_x - 2V_2 = 0$$


$$-4V_x + 2V_2 = 0$$

$$\therefore V_x = 2V \Rightarrow V_1 = V_x = \boxed{2V}$$

$$V_2 = \boxed{5V}$$

$$i_L = \frac{V_2}{1k} = \boxed{1mA}$$

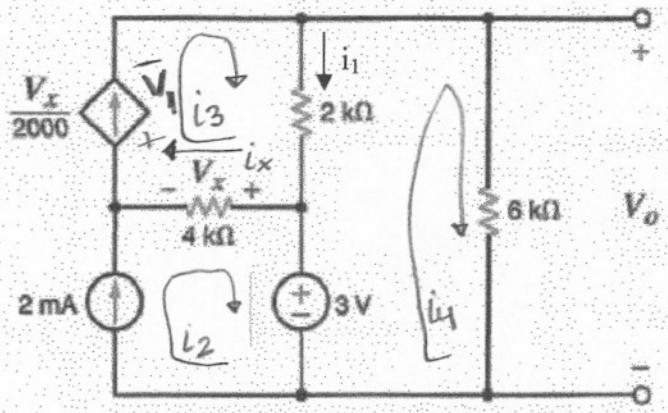4. a. Use the mesh-current method to find  $i_1$ .  
 b. Find the power dissipated by the dependent current source.



- Label currents in each square
  - Identify squares with currents in the outside branch and set equal to mesh current:
- ①  $i_3 = \frac{V_x}{2000}$  { Need to rewrite dependent variable  
 in terms of mesh currents  $\Rightarrow$   
 $i_2 = 2\text{mA}$       ②  $V_x = 4K(i_x) = 4K(i_3 - i_2)$  }

- Take Voltage loop  $\Rightarrow$

$$+3 + i_1(2K) - i_4(6K) = 0$$

$$\text{where } i_1 = (i_3 - i_4)$$

$$\therefore +3 + i_3(2K) - i_4(2K) - i_4(6K) = 0$$

$$\textcircled{3} \quad 3 + i_3(2K) - i_4(8K) = 0$$

$$\Rightarrow \text{plug } \textcircled{2} \text{ into } \textcircled{1}: 2K i_3 = 4K i_3 - 4K i_2 \\ 4K i_2 = 2K i_3$$

$$2i_2 = i_3 \Rightarrow i_3 = 2(2\text{mA}) = 4\text{mA}$$

Using  $i_3 = 4\text{mA}$  into ③:

$$+3 + 4m(2\text{k}) - i_4(8\text{k}) = 0$$

$$\therefore i_4(8\text{k}) = 3 + 8 = 11$$

$$i_4 = \frac{11}{8\text{k}} \text{ A}$$

want  $i_1 = (i_3 - i_4) = 4\text{m} - \frac{11}{8\text{k}}\text{A} = \frac{32}{8\text{k}} - \frac{11}{8\text{k}} = \boxed{\frac{21}{8\text{k}} \text{ A}}$

b. Need voltage across current,  $V_i$ .

Taking a V loop  $\Rightarrow$

$$+3 - V_i - i_4(6\text{k}) = 0$$

$$V_i = 3 - \frac{11}{8\text{k}}(6\text{k}) = 3 - 8.25 = \underline{\underline{-5.25\text{V}}}$$

$$\text{power} = V_i * i_3 = -(5.25)(4\text{m}) = \boxed{-21\text{mW}}$$

producing or  
generating  
power