


UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1270

HOMEWORK #4

Summer 2007


1.

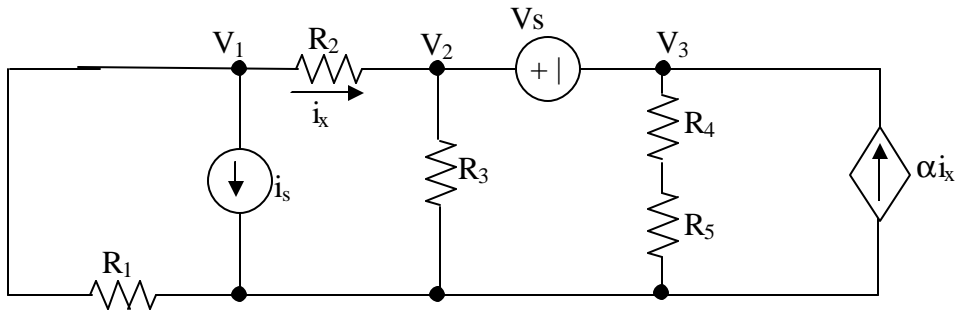

For the circuit shown, write three independent equations for the node voltages V_1 , V_2 , and V_3 . The quantity i_x must not appear in the equations.


2. Make a consistency check on your equations for Problem 1 by settings resistors and sources to values for which the values of V_1 , V_2 , and V_3 are obvious. State the values of resistors, sources, and for your consistency check, and show that your equations for Problem 1 are satisfied for these values. (In other words, plug in the values into your equations for Problem 1 and show that the left side and the right side of each equation are equal.)

3.

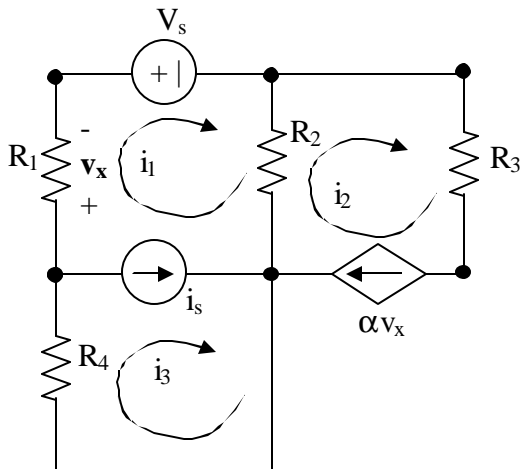


For the circuit shown, write three independent equations for the three mesh currents i_1 , i_2 , and i_3 . The quantity v_x must not appear in the equations.

4.

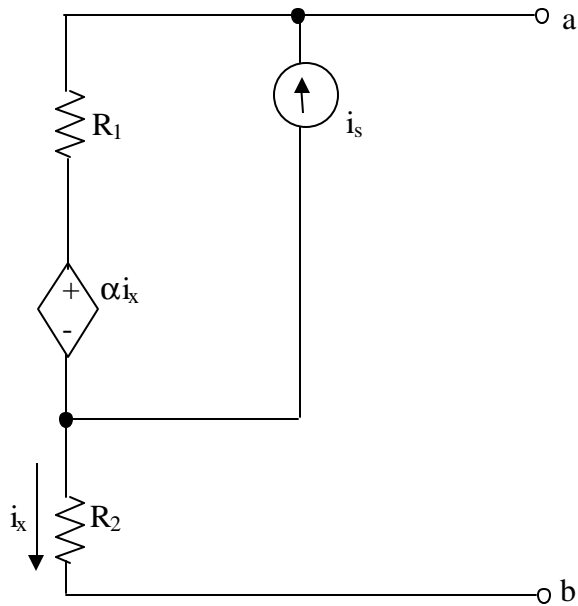

Find the Thevenin equivalent circuit at terminals a-b. i_x must not appear in your solution.
Note: $0 < \alpha < 1$.

5.

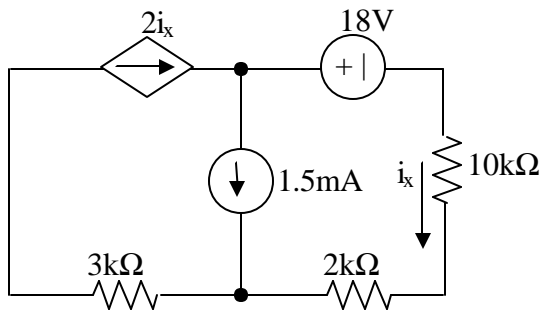

Calculate the power consumed (ie dissipated) by the 18V source. **Note:** If a source supplies power, the power it consumes is negative.