


UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1270

HOMWORK #4 Solution

Summer 2007

1.

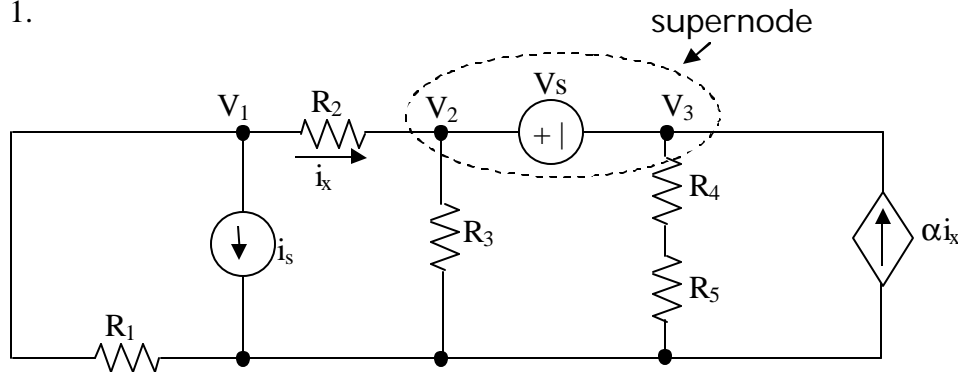

For the circuit shown, write three independent equations for the node voltages V_1 , V_2 , and V_3 . The quantity i_x must not appear in the equations.

First, we write i_x in terms of node v 's:

$$i_x = \frac{V_1 - V_2}{R_2}$$

Second, we check whether node v_1 is part of a supernode, (i.e., is connected to another node by only a voltage source). v_1 is not part of a supernode, so we write a current-summation eq'n for it:

$$\frac{V_1}{R_1} + i_s + \frac{V_1 - V_2}{R_2} = 0A \quad (1)$$

Third, we observe that v_2 and v_3 form a supernode. Thus, we write a eq'n for the summation of all currents out of the bubble shown on the circuit diagram:

$$\frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + \frac{V_3}{R_4 + R_5} - \alpha \left(\frac{V_1 - V_2}{R_2} \right) = 0A \quad (2)$$

Fourth, we add a voltage eq'n for nodes V_1 and V_2 .


$$V_2 - V_3 = V_s \quad \text{or} \quad V_2 = V_3 + V_s \quad (3)$$

2. Make a consistency check on your equations for Problem 1 by settings resistors and sources to values for which the values of V_1 , V_2 , and V_3 are obvious. State the values of resistors, sources, and for your consistency check, and show that your equations for Problem 1 are satisfied for these values. (In other words, plug in the values into your equations for Problem 1 and show that the left side and the right side of each equation are equal.)

There are many possible consistency checks: one example is shown here.

$$\begin{aligned} \text{Let } V_5 &= 0V, \quad i_5 = 6A, \quad \alpha = 5 \\ R_1 &= \infty \Omega \text{ (open)}, \quad R_2 = 2\Omega, \quad R_3 = 3\Omega \\ R_4 &= 4\Omega, \quad R_5 = \infty \Omega \text{ (open)} \end{aligned}$$

Our circuit becomes the following:

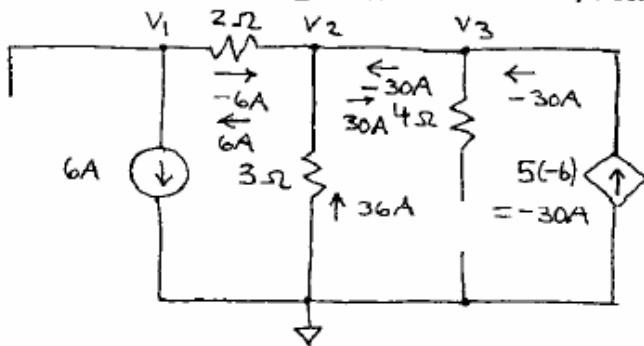

We have $i_x = -i_5 = -6A$. Thus $\alpha i_x = -30A$.

From a current summation at node V_1 , we conclude that 36A flows up thru the 3Ω resistor.

$$\therefore V_2 = -36A \cdot 3\Omega = -108V$$

Since the V_2 and V_3 nodes are connected by a 0V source (a wire) we have

$$V_2 = V_3 = -108V.$$

For V_1 , we have

$$V_1 = V_2 - 6A \cdot 2\Omega = V_2 - 12V = -120V.$$

Now we check to see if eq'ns (1), (2), and (3) from earlier hold when we substitute values from the consistency check:

$$(1) \frac{-120V}{\infty \Omega} + 6A + \frac{-120V - (-108V)}{2 \Omega}$$

$$= 6A - \frac{12V}{2 \Omega} = 0V \quad \checkmark \text{ (consistent)}$$

$$(2) \frac{-108V - (-120V)}{2 \Omega} + \frac{-108V}{3 \Omega} + \frac{-108V}{4 \Omega + \infty \Omega} - 5 \left(\frac{-120V - (-108V)}{2 \Omega} \right)$$


$$= \frac{12V}{2 \Omega} - \frac{108V}{3 \Omega} - 0A - 5 \left(\frac{-12V}{2 \Omega} \right)$$

$$= 6A - 36A + 30A = 0A \quad \checkmark \text{ (consistent)}$$

$$(3) \quad -108V - (-108V) = 0V = V_d \quad \checkmark \text{ (consistent)}$$

All three eq'ns are satisfied by values from the consistency check, giving us confidence that our node-voltage eq'ns are correct.

3.

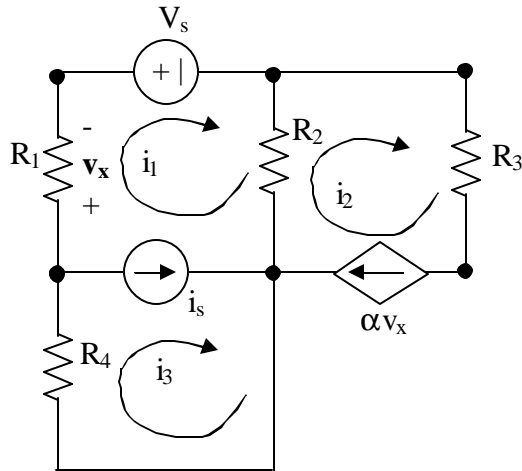

For the circuit shown, write three independent equations for the three mesh currents i_1 , i_2 , and i_3 . The quantity v_x must not appear in the equations.

sol'n: First, we write v_x in terms of mesh currents:

$$v_x = i_1 R_1$$

Note: current in R_1 is i_1 since R_1 is on the outside edge of the circuit.

Second, we observe that i_5 is between the i_1 and i_3 loops, meaning that the i_1 and i_3 loops form a supermesh. Thus, we write a v-loop eqn for the outside path around the i_1 and i_3 loops:

$$-i_1 R_1 + v_s - i_1 R_2 + i_2 R_2 - i_3 R_3 = 0V \quad (1)$$

Third, we write a current summation eqn for the source, i_5 , between the i_1, i_3 loops:


$$i_5 = i_3 - i_2 \quad (2)$$

Note: i_3 has a + sign because it flows in the same direction as i_5 , whereas i_2 has a - sign because it flows in the opposite direction from i_5 .

Fourth, we observe that the i_2 loop has a current source that is on the outside edge of the circuit. The loop current, i_2 , must equal the current flowing in the current source:

$$i_2 = \alpha (i_1 R_1) \quad (3)$$


4.

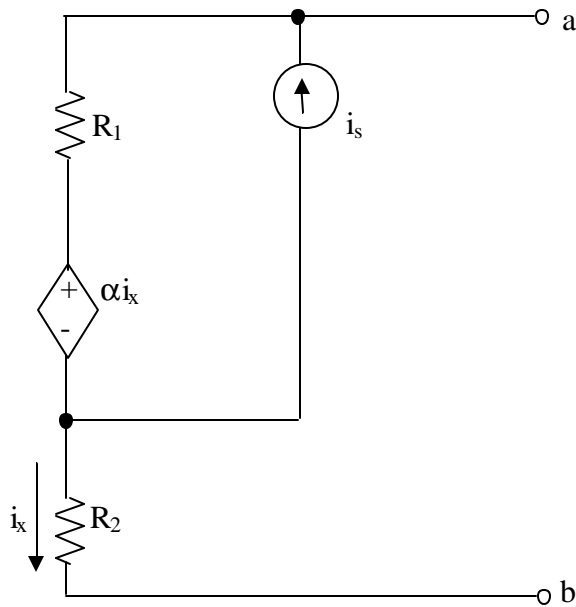

Find the Thevenin equivalent circuit at terminals a-b. i_x must not appear in your solution.
Note: $0 < \alpha < 1$.

$$V_{Th} = V_{a,b} \text{ open circuit} \quad (\text{always true})$$

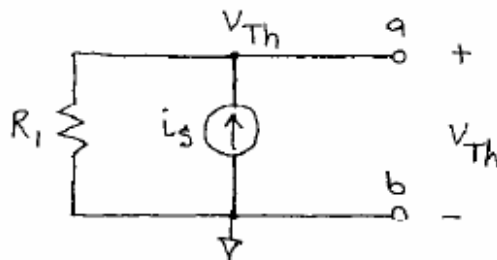
If we have an open circuit, $i_x = 0$ and there is no voltage drop across R_2 and $\alpha i_x = 0$ acts like a wire. An equivalent circuit model for finding V_{Th} is shown below.



We see by inspection that V_{Th} is across R_1 and $V_{Th} = i_s R_1$ by Ohm's law.

$$V_{Th} = i_s R_1$$

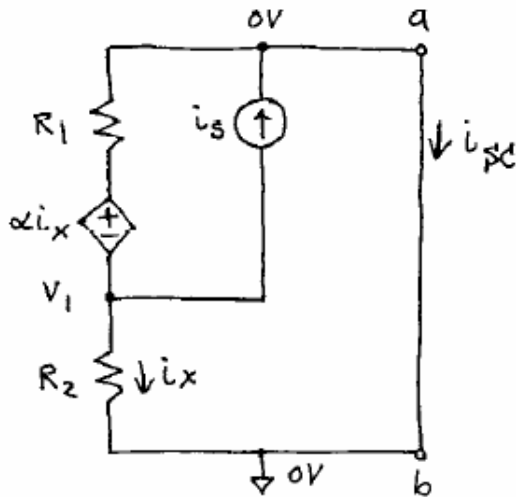To find R_{Th} , we short the a, b terminals and measure the short-circuit current, i_{sc} .



One way to solve the circuit is to use the node-voltage method, as is done here.

First, we define i_x in terms of node-voltage:

$$i_x = \frac{V_1}{R_2}$$

Second, we write a current summation eq'n for node V_1 :

$$\frac{V_1 + \alpha \frac{V_1}{R_2}}{R_1} + i_s + \frac{V_1}{R_2} = 0A$$

or

$$v_1 \left(\frac{1}{R_1} + \frac{\alpha}{R_1 R_2} + \frac{1}{R_2} \right) = -i_s$$

$$\text{or } v_1 = -i_s \cdot R_1 \parallel \frac{R_1 R_2}{\alpha} \parallel R_2$$

Third, we observe that $i_{sc} = -i_x = -\frac{v_1}{R_2}$:

$$i_{sc} = i_s \cdot \left(R_1 \parallel \frac{R_1 R_2}{\alpha} \parallel R_2 \right) \cdot \frac{1}{R_2}$$

Fourth, we use $R_{Th} = \frac{v_{Th}}{i_{sc}}$:


$$R_{Th} = \frac{v_{Th}}{i_{sc}} = \frac{i_s R_1}{i_s \cdot R_1 \parallel \frac{R_1 R_2}{\alpha} \parallel R_2 \cdot \frac{1}{R_2}}$$

$$R_{Th} = \frac{R_1 R_2}{R_1 \parallel \frac{R_1 R_2}{\alpha} \parallel R_2}$$


$$\text{or } R_{Th} = R_1 R_2 \left(\frac{1}{R_1} + \frac{\alpha}{R_1 R_2} + \frac{1}{R_2} \right) = R_2 + \alpha + R_1$$

Thevenin equivalent:

$$R_{Th} = R_1 + R_2 + \alpha$$

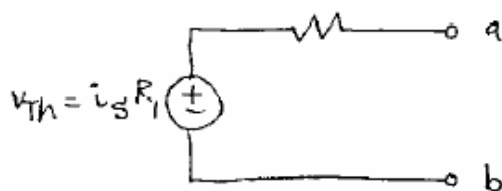

5.

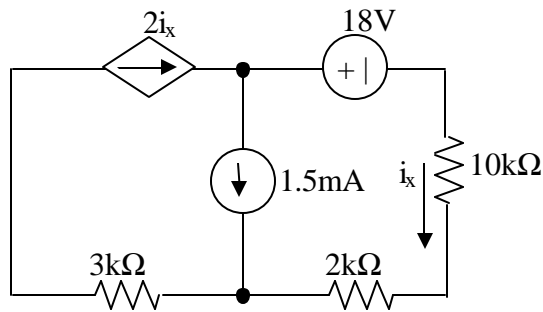

Calculate the power consumed (ie dissipated) by the 18V source. **Note:** If a source supplies power, the power it consumes is negative.

We may solve this circuit in a variety of ways, but a simple way is to write a current summation eq'n for the v_1 node:

$$-2i_x + 1.5\text{mA} + i_x = 0A \quad (1)$$

Note: We normally avoid using i_x . To do so here, we would use the following eq'n for i_x :

$$i_x = \frac{v_1 + 18V}{10k\Omega + 2k\Omega}$$

This leads to a correct solution but requires more writing.

From eq'n (1), we have

$$i_x = 1.5\text{mA}$$

Our pwr is $p = i_x \cdot 18V = 1.5\text{mA} \cdot 18V = 27\text{mW}$