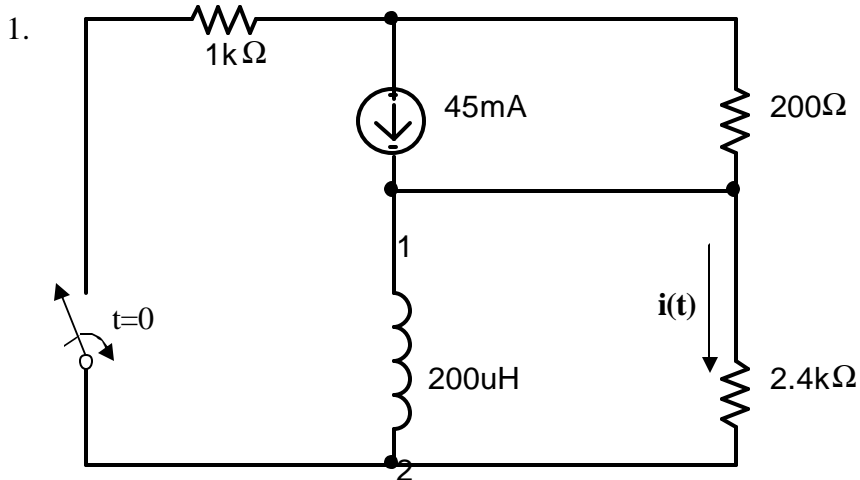


UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1270

HOMework #6


Summer 2007



After being open for a long time, the switch closes at $t=0$.


- a) Calculate the energy stored on the inductor as $t \rightarrow \infty$.
- b) Write a numerical expression for $i(t)$ for $t > 0$.

2.

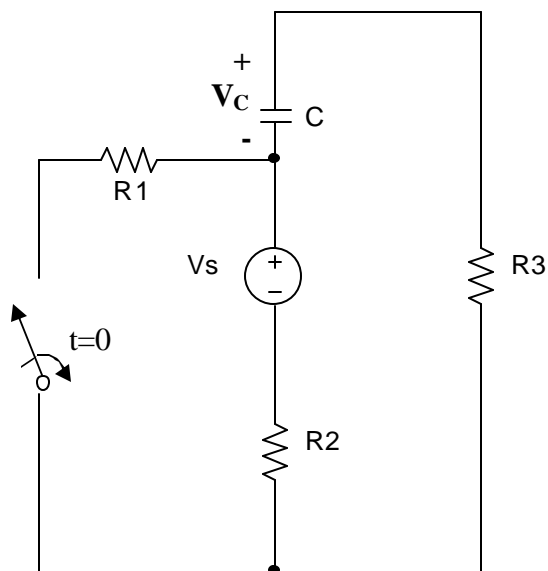


After being open for a long time, the switch becomes closed at $t=0$.

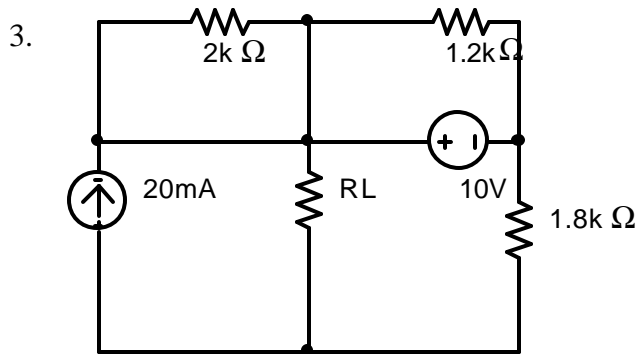- a) Write an expression for $V_c(t=0^+)$.
- b) Write an expression for $V_c(t > 0)$ in terms of $R1$, $R2$, $R3$, V_s , and C .



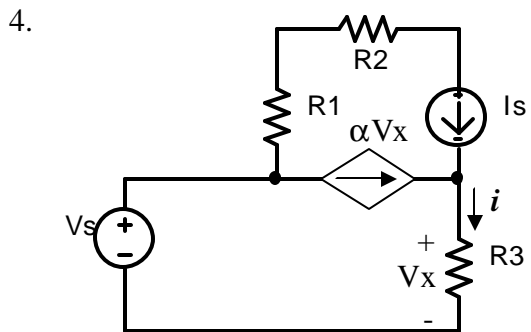- Calculate the value of R_L that would absorb maximum power.
- Calculate that value of maximum power R_L could absorb.



Using superposition, derive an expression for i that contains no circuit quantities other than I_s , V_s , R_1 , R_2 , R_3 , and α , where $\alpha > 0$.