

UNIVERSITY OF UTAH  
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1270

HOMEWORK #8

Summer 2007

1. Give numerical answers to each of the following questions:

a) Rationalize  $\frac{-80 - j60}{28 - j96}$ . Express your answer in rectangular form.


b) Find the polar form of  $(1 + j)^* \left( \sqrt{1 + \frac{\sqrt{3}}{2}} - j\sqrt{1 - \frac{\sqrt{3}}{2}} \right)^*$ . (Note: the asterisk means "conjugate".)

c) Find the following phasor:  $P|3\sin(25kt - 120^\circ)|$ .

d) Find the magnitude of  $\frac{(1 - j7)e^{-j10^\circ}}{1 - e^{j90^\circ}}$ .

e) Find the imaginary part of  $\frac{1 + j\sqrt{3}}{e^{-j30^\circ}}$ .

2.

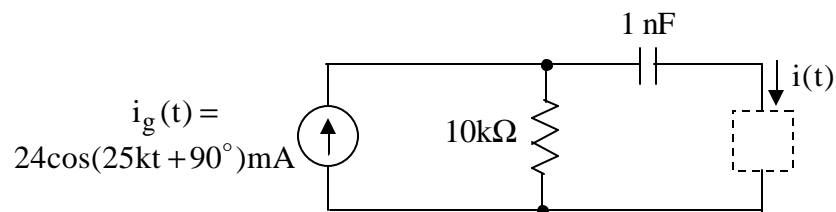


a) Choose an R, an L, or a C to be placed in the dashed-line box to make

$$i(t) = I_0 \cos(25kt + 135^\circ)$$

where  $I_0$  is a positive, (i.e., nonzero), real constant. State the value of the component you choose. Hint: Use a Thevenin equivalent.

3. With your component from problem 2 in the circuit, calculate the resulting value of  $I_0$ .

4.

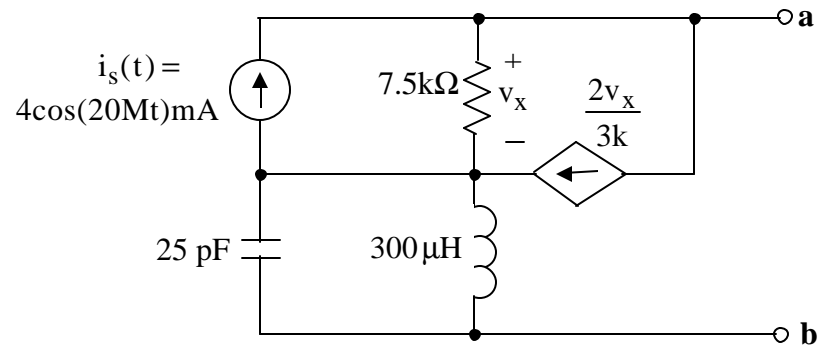

- Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for  $i_s(t)$ , and show numerical impedance values for R, L, and C. Label the dependent source appropriately.
- Find the Thevenin equivalent (in the frequency domain) for the above circuit. Give the numerical phasor value for  $\mathbf{V}_{\text{Th}}$  and the numerical impedance value of  $\mathbf{z}_{\text{Th}}$ .