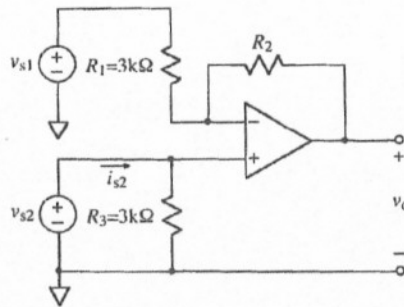



1.

Rail voltages =  $\pm 9$  V

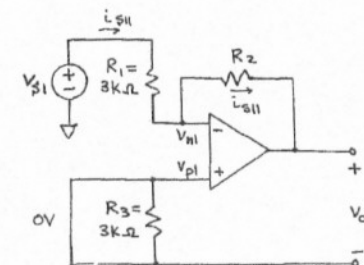- a) The above circuit operates in linear mode. Derive a symbolic expression for  $v_o$ . The expression must contain not more than the parameters  $v_{s1}$ ,  $v_{s2}$ ,  $R_1$ ,  $R_2$ , and  $R_3$ .
- b) If  $v_{s2} = 0$  V, find the value of  $R_2$  that will yield an output voltage of  $v_o = -1$  V when  $v_{s1} = 10$  mV.
- c) Derive a symbolic expression for  $v_o$  in terms of common mode and differential input voltages:
- $$v_{\Sigma} = \frac{v_{s1} + v_{s2}}{2} \quad \text{and} \quad v_{\Delta} = \frac{v_{s1} - v_{s2}}{2}$$
- The expression must contain not more than the parameters  $v_{\Sigma}$ ,  $v_{\Delta}$ ,  $R_1$ ,  $R_2$ , and  $R_3$ . Write the expression as  $v_{\Sigma}$  times a gain term plus  $v_{\Delta}$  times a gain term. Hint: write  $v_{s1}$  and  $v_{s2}$  in terms of  $v_{\Sigma}$  and  $v_{\Delta}$ .
- d) Using the value of  $R_2$  from part (b), if necessary, calculate the input resistance.  $R_{in} = v_{s2}/i_{s2}$ , seen by the  $v_{s2}$  source.

sol'n: a) Using superposition, we turn on one  $v$ -source at a time.

case I:  $v_{s1}$  on,  $v_{s2}$  off (= wire)



$R_3$  is bypassed by a wire and may be ignored. The circuit is then seen to be a simple negative-gain amplifier:


$$v_{p1} = 0V \quad v_{n1} = v_{p1} = 0V$$

$$i_{s1} = \frac{v_{s1} - 0V}{R_1} \quad \text{on left side}$$

$$i_{s1} = \frac{0V - v_o}{R_2} \quad \text{on right side}$$

$$\therefore -\frac{v_o}{R_2} = \frac{v_{s1}}{R_1} \quad \text{or} \quad v_o = -v_{s1} \frac{R_2}{R_1}$$

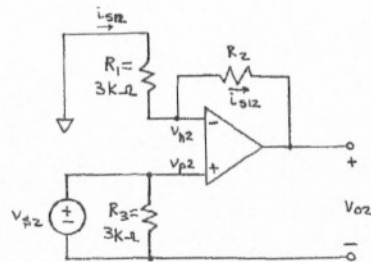case II:  $V_{s1}$  off (=wire),  $V_{s2}$  on



Since  $R_3$  is across  $V$ -source  $V_{s2}$ , we may ignore it. The circuit is then seen to be a simple positive-gain amplifier:

$$V_{p2} = V_{s2} \quad V_{n2} = V_{p2} = V_{s2}$$

$$i_{s12} = \frac{0 - V_{n2}}{R_1} = -\frac{V_{s2}}{R_1}$$

$$i_{s12} = \frac{V_{n2} - V_{o2}}{R_2} = \frac{V_{s2} - V_{o2}}{R_2}$$

$$\therefore \frac{V_{s2} - V_{o2}}{R_2} = -\frac{V_{s2}}{R_1}$$

$$V_{o2} = V_{s2} \left( 1 + \frac{R_2}{R_1} \right)$$

Summing results gives  $V_o = V_{o1} + V_{o2} = -V_{s1} \frac{R_2}{R_1} + V_{s2} \left( 1 + \frac{R_2}{R_1} \right)$ .

b) Using  $V_{s2} = 0V$  and  $V_{s1} = 10mV$  in the formula from (a), we have

$$V_o = -1V = -10mV \frac{R_2}{3k\Omega} + 0 \cdot \left( 1 + \frac{R_2}{3k\Omega} \right)$$

$$\text{or } R_2 = \frac{-1V}{-10mV} \cdot 3k\Omega = 300k\Omega$$

c) We have  $V_{s1} = V_{s2} + V_{\Delta}$  and  $V_{s2} = V_{s2} - V_{\Delta}$ .

Substituting these into the formula for  $V_o$  from (a) yields the following:

$$V_o = -(V_{s2} + V_{\Delta}) \frac{R_2}{R_1} + (V_{s2} - V_{\Delta}) \left( 1 + \frac{R_2}{R_1} \right)$$



$$V_o = V_{s2} \left( 1 + \frac{R_2}{R_1} - \frac{R_2}{R_1} \right) - V_{\Delta} \left( \frac{R_2}{R_1} + 1 + \frac{R_2}{R_1} \right)$$

$$V_o = V_{s2} - V_{\Delta} \left( 1 + 2 \frac{R_2}{R_1} \right)$$

d)  $R_{in} = \frac{V_{s2}}{i_{s2}} = \frac{V_{s2}}{V_{s2}/R_3}$  (no current flows into op-amp, so  $i_{s2} = V_{s2}/R_3$ )

$$R_{in} = R_3$$

2.

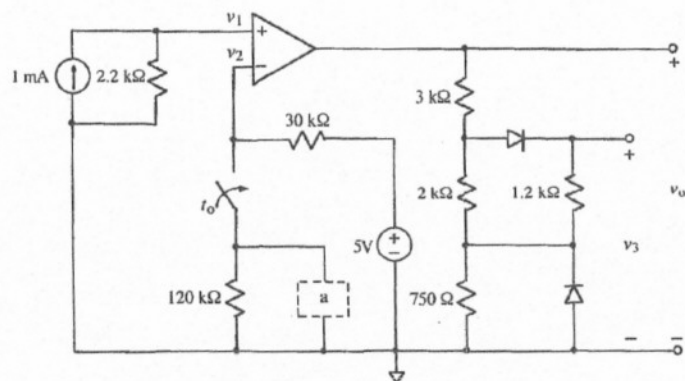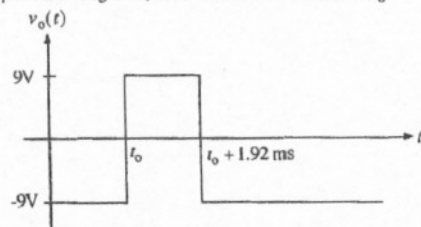Rail voltages =  $\pm 9$  VAfter being open for a long time, the switch closes at time  $t = t_0$ .

- Choose either an L or a C to go in box a to produce the  $v_o(t)$  shown above. Specify what component goes in the box and its value.
- Sketch  $v_1(t)$ , showing numerical values appropriately.
- Sketch  $v_2(t)$ , showing numerical values appropriately.
- Sketch  $v_3(t)$ . Show numerical values for  $t < t_0$ , for  $t_0 < t < t_0 + 1.92$  ms, and for  $t > t_0 + 1.92$  ms. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.


sol'n: a) The op-amp acts as a comparator since there is no feedback. It measures the voltage drop across the inputs with the polarity as indicated by the + and - signs. If the voltage is positive, the output is  $+V_{rail}$ . If the voltage is negative, the output is  $-V_{rail}$ .

To produce the waveform shown in the problem, we must have  $v_2 > v_1$  for  $t < t_0$  and  $t > t_0 + 1.92$  ms, and we must have  $v_2 < v_1$  for  $t_0 < t < t_0 + 1.92$  ms.

$v_1$  is constant. The value of  $v_1$  is


$$v_1 = 1 \text{ mA} \cdot 2.2 \text{ k}\Omega = 2.2 \text{ V}.$$

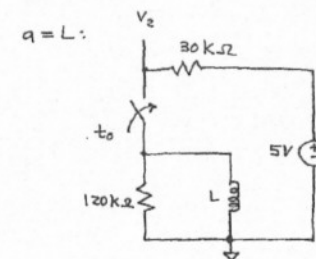For  $v_2$ , we consider the behavior with  $a = L$  and  $a = C$  in turn. (Assume  $t_0 = 0$ .)



At  $t = 0^-$ ,  $L = \text{wire}$  and  $i_L(0^-) = 0$  A,  $v_2 = 5$  V.

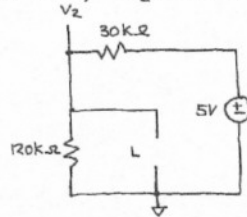At  $t=0^+$ ,  $i_L(0^+) = i_L(0^-) = 0A = \text{open}$ .



We have V-divider, with

$$V_2(0^+) = 5V \cdot \frac{120k}{120k + 30k} = 4V.$$

For  $t \rightarrow \infty$ ,  $L = \text{wire}$  and  $V_2(t \rightarrow \infty) = 0V$ .


Using the general form of solution, we write an expression for  $V_2(t > 0)$ :

$$V_2(t > 0) = V_2(t \rightarrow \infty) + [V_2(0^+) - V_2(t \rightarrow \infty)] e^{-t/L/R_{TH}}$$

$$V_2(t > 0) = 0V + [4V - 0V] e^{-t/L/R_{TH}}$$


$$V_2(t > 0) = 4V e^{-t/L/R_{TH}}$$

$$V_2(t < 0) = 5V \text{ from earlier}$$

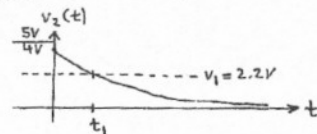


The time constant,  $L/R_{TH}$ , is unknown, but the shape of the curve is exponential.

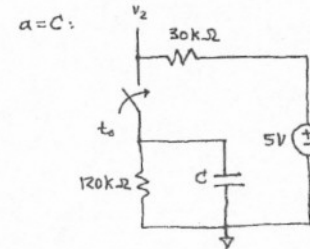We see that  $V_2 > V_1$  for  $t < 0$  and  $t < t_1$ , and  $V_2 < V_1$  for  $t > t_1$ . Thus, this is not a viable waveform for  $V_2$  to achieve the desired output pulse. Rather than proceeding with this solution, we consider the case of  $a = C$ .



At  $t=0^-$ ,  $C = \text{open}$  and  $V_C(0^-) = 0V$ ,  $V_2 = 5V$ .

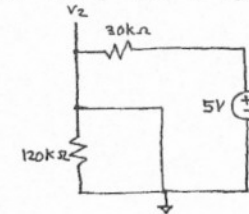At  $t=0^+$ ,  $V_C(0^+) = V_C(0^-) = 0V = \text{wire}$ .



We have  $V_2$  shorted to reference.  
 $\therefore V_2(0^+) = 0V$

For  $t \rightarrow \infty$ ,  $C = \text{open}$  and we have V-dividers:

$$V_2(t \rightarrow \infty) = 5V \cdot \frac{120k\Omega}{120k\Omega + 30k\Omega} = 4V$$


Using the general form of solution, we write an expression for  $V_2(t > 0)$ :

$$V_2(t > 0) = V_2(t \rightarrow \infty) + [V_2(0^+) - V_2(t \rightarrow \infty)] e^{-t/R_{Th}C}$$

$$V_2(t > 0) = 4V + [0V - 4V] e^{-t/R_{Th}C}$$

$$V_2(t > 0) = 4V - 4V e^{-t/R_{Th}C}$$


$$V_2(t < 0) = 5V \text{ from earlier}$$

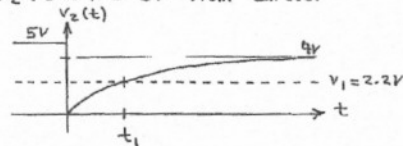

The time constant,  $R_{Th}C$ , is unknown at this point, but the curve is exponential.

We see that  $V_2 > V_1$  for  $t < 0$  and  $t > t_1$ , and  $V_2 < V_1$  for  $0 < t < t_1$ . Thus, this is a viable waveform for  $V_2$  to achieve the desired output pulse.

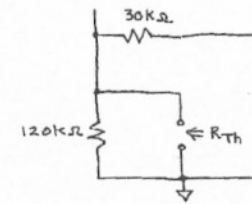We choose  $C$  to make  $t_1 = 1.92 \text{ ms}$  for proper pulse width. To find  $R_{Th}$ , we remove  $C$  and look into the terminals where  $C$  was connected—and turn off 5V src.



$$R_{Th} = 30k\Omega \parallel 120k\Omega$$

$$= 30k\Omega \cdot \frac{1}{1 + 4}$$

$$= 30k\Omega \cdot \frac{4}{5}$$

$$R_{Th} = 24k\Omega$$

For  $t_1 = 1.92 \text{ ms}$ , we want  $V_2(t_1) = V_1$ .

$$V_1 = 2.2V = V_2(t_1 = 1.92 \text{ ms}) = 4V - 4V e^{-t_1/R_{Th}C}$$

$$\text{or } 2.2V - 4V = -4V e^{-t_1/R_{Th}C}$$

$$\text{or } 1.8V = 4V e^{-t_1/R_{Th}C}$$

$$\text{or } \frac{1.8V}{4V} = e^{-t_1/R_{Th}C}$$

$$\text{or } \ln \frac{1.8V}{4V} = -t_1/R_{Th}C$$


$$\text{or } R_{Th}C = -t_1 / \ln \left( \frac{1.8}{4} \right) = \frac{-1.92 \text{ ms}}{\ln(1.8/4)}$$

$$\text{or } R_{Th}C = 2.4 \text{ ms} = \text{time const, } \tau$$


$$\text{or } C = \frac{2.4 \text{ ms}}{R_{Th}} = \frac{2.4 \text{ ms}}{24 \text{ k}\Omega}$$

$$\text{or } C = 0.1 \mu\text{F}$$

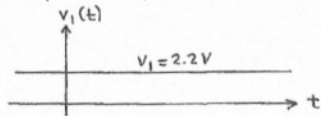
b) From part (a), we have  $V_1 = 2.2 \text{ V}$  always.



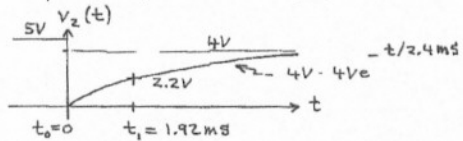c) From part (a), we have  $V_2(t)$  as follows:



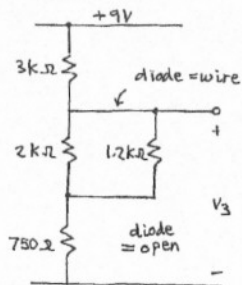d) When  $V_0$  is high, the top diode will conduct and the bottom diode will be off.



We have a v-divider:

$$V_3 = +9 \text{ V} \cdot \frac{750 \Omega + 1.2 \text{ k}\Omega \parallel 2 \text{ k}\Omega}{750 \Omega + 1.2 \text{ k}\Omega \parallel 2 \text{ k}\Omega + 3 \text{ k}\Omega}$$

$$\begin{aligned} \text{Note: } 1.2 \text{ k}\Omega \parallel 2 \text{ k}\Omega &= 0.2 \cdot 6 \parallel 10 \text{ k}\Omega \\ &= 0.4 \cdot 3 \parallel 5 \text{ k}\Omega = 0.4 \cdot \frac{15}{8} \text{ k}\Omega \\ &= \frac{6}{8} \text{ k}\Omega = 750 \Omega \end{aligned}$$


$$\therefore V_3 = 9 \text{ V} \cdot \frac{750 + 750}{750 + 750 + 3 \text{ k}} \frac{\Omega}{\Omega}$$

$$= 9 \text{ V} \cdot \frac{1.5 \text{ k}}{4.5 \text{ k}}$$

$$V_3 = 3 \text{ V} \quad \text{when } V_0 = +9 \text{ V}$$


When  $V_0 = -9 \text{ V}$ , the top diode will be off and the bottom diode will be on. Thus, the bottom diode will act like a wire shorting  $V_3$  to ref.
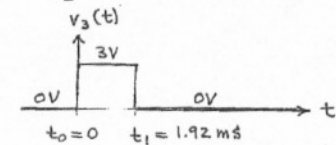
$$V_3 = 0 \text{ V} \quad \text{when } V_0 = -9 \text{ V}$$






3.

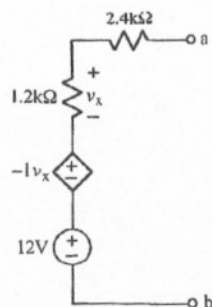

- Find the Thevenin equivalent of the above circuit relative to terminals a and b.
- If we attach  $R_L$  to terminals a and b, find the value of  $R_L$  that will absorb maximum power.
- Calculate the value of that maximum power absorbed by  $R_L$ .

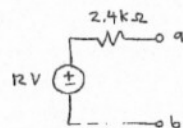Sol'n: a) The dependent source and  $1.2k\Omega$  resistor together produce a voltage drop of  $-v_x + v_x = 0V$ . Thus, they act like a wire and may be replaced by a wire:



This simplified circuit is the Thevenin equivalent.

$$V_{Th} = 12V$$

$$R_{Th} = 2.4k\Omega$$

$$b) \quad R_L = R_{Th} \text{ for max power transfer}$$

$$R_L = 2.4k\Omega$$


$$c) \quad P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(12V)^2}{4(2.4k\Omega)}$$

$$= \frac{12}{4} \cdot \frac{12}{2.4k} \text{ W}$$

$$= 3.5 \text{ mW}$$

$$P_{max} = 15 \text{ mW}$$


4.

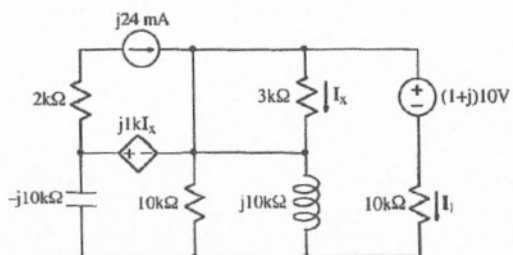Rail voltages =  $\pm 9$  V

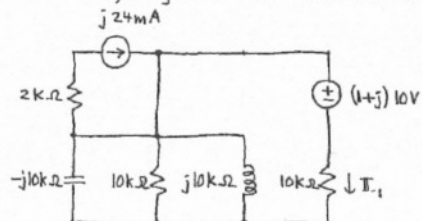- a) A frequency-domain circuit is shown above. Write the value of phasor current  $I_1$  in rectangular form.
- b) Given  $\omega = 20$  k rad/s, write a numerical time-domain expression for  $i_1(t)$ , the inverse phasor of  $I_1$ .

sol'n: a) First, we observe that  $I_x = 0$  since the  $3$  k $\Omega$  resistor is shorted out by wires.


Thus, the dependent source = 0V, and we may ignore the  $3$  k $\Omega$  resistor.



Second, we observe that the  $-j10$  k $\Omega$  and  $j10$  k $\Omega$  in parallel act like an open circuit:

$$\begin{aligned} -j10 \text{ k}\Omega \parallel j10 \text{ k}\Omega &= j10 \text{ k}\Omega \cdot (-1/j10) \Omega \\ &= j10 \text{ k}\Omega \cdot (-1/0) \Omega \\ &= \infty \Omega = \text{open} \end{aligned}$$

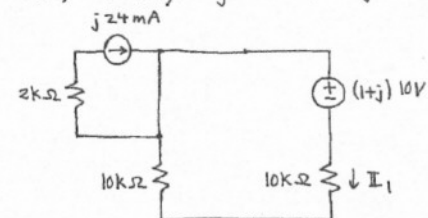Thus, we may ignore the  $-j10$  k $\Omega$  and  $j10$  k $\Omega$ :




Third, we observe that the  $2$  k $\Omega$  is in series with a current source and may be ignored.

Fourth, we observe that the current source is shorted by a wire that isolates it from the loop on the right. Thus, we may ignore the current source.

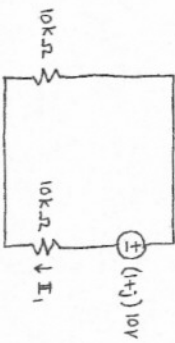The circuit now consists of a voltage source and two resistors.





$$I_1 = \frac{(1+j) 10V}{10k\Omega + 10k\Omega}$$

$$I_1 = \frac{1+j}{2} \text{ mA} = \frac{1}{2} \text{ mA} + j\frac{1}{2} \text{ mA}$$

b)  $I_1$  in rectangular form  $i_1(t)$  is a sum of a pure  $\cos()$  and a pure  $\sin()$ :

$$i_1(t) = \frac{1}{2} \text{ mA} \cos(20kt) - \frac{1}{2} \text{ mA} \sin(20kt)$$

$$\text{Note: } P' [j] = -\sin(\omega t)$$

In polar form,  $I_1 = \frac{1}{2} \sqrt{2} \angle 45^\circ \text{ mA}$

$$i_1(t) = \frac{\sqrt{2}}{2} \text{ mA} \cos(20kt + 45^\circ)$$