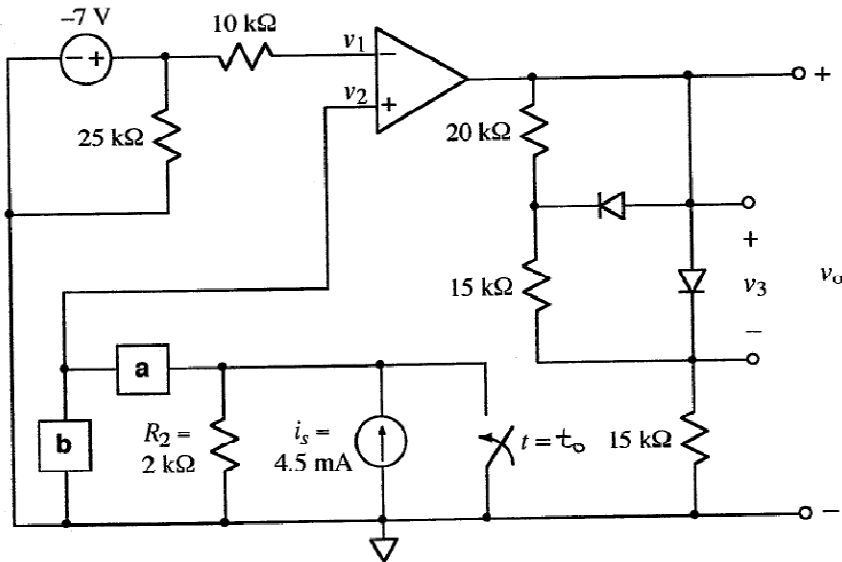
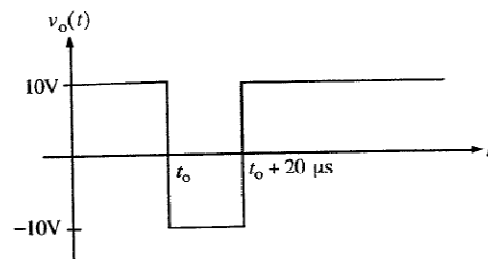


1.

Rail voltages =  $\pm 10$  VAfter being open for a long time, the switch closes at time  $t = t_0$ .


Choose either an  $R$  or  $C$  to go in box **a** and either an  $R$  or  $L$  to go in box **b** to produce the  $v_0(t)$  shown above. Use an  $R$  value of  $3 \text{ k}\Omega$ . Also, note that  $v_0$  stays high forever after  $t_0 + 20 \mu\text{s}$ . Specify which element goes in each box and its value.

2. Sketch  $v_1(t)$ , showing numerical values appropriately.3. a) Sketch  $v_2(t)$ , showing numerical values appropriately.

b)

Sketch  $v_3(t)$ . Show numerical values for  $t < t_0$ , for  $t_0 < t < t_0 + 20 \mu\text{s}$ , and for  $t > t_0 + 20 \mu\text{s}$ . Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

4.

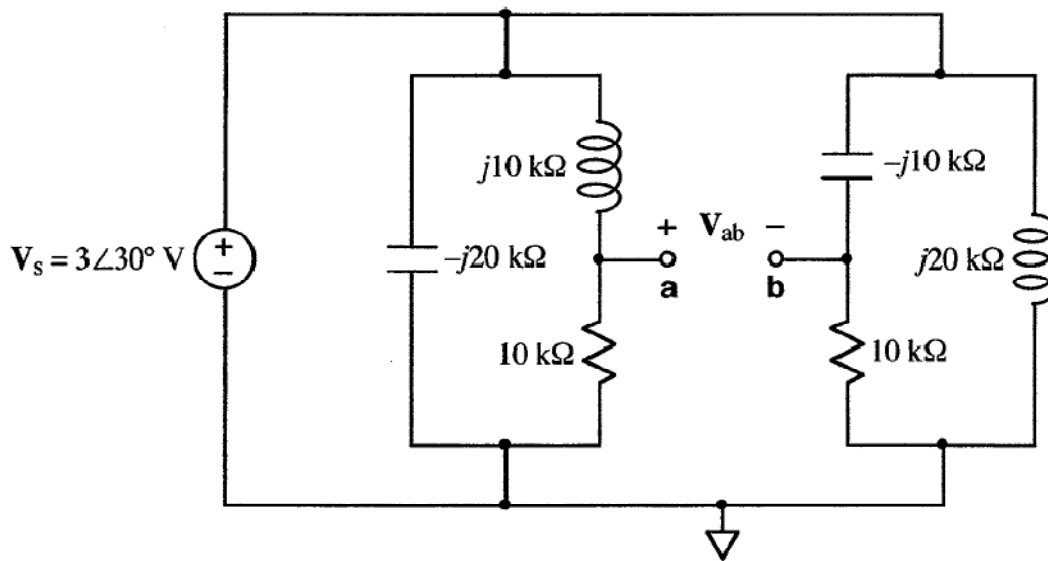

A frequency-domain circuit is shown above. Write the value of phasor voltage  $V_{ab}$  in polar form.

5.

Given  $\omega = 500\text{k rad/s}$ , write a numerical time-domain expression for  $v_{ab}(t)$ , the inverse phasor of  $V_{ab}$ .