
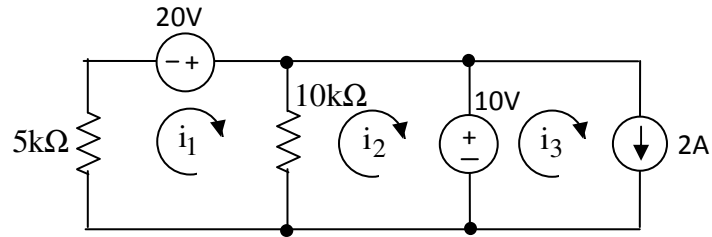


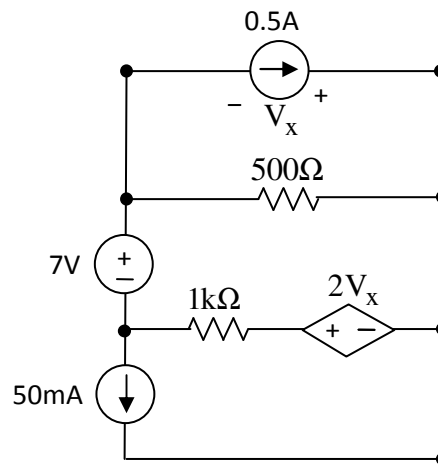
1. Use the mesh-current method to find  $i_1$  and  $i_2$ , and  $i_3$ .




2. a. Use the mesh-current method to find  $V_x$ ,  $V_x$  must not be in equation.  
 b. Find power dissipated by the dependent source.



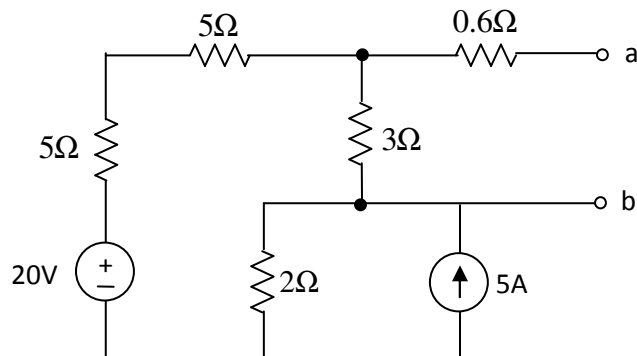
3. Find the Thevenin equivalent circuit at terminals a-b.



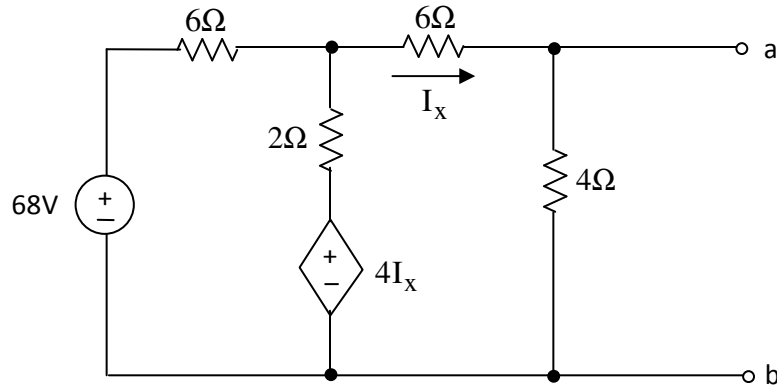
4. Find the Thevenin equivalent circuit at terminals a-b.



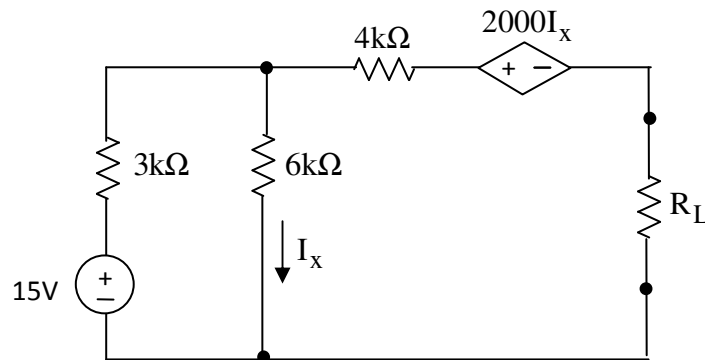5. Determine the power in the dependent source if  $R_L = 2\text{k}\Omega$




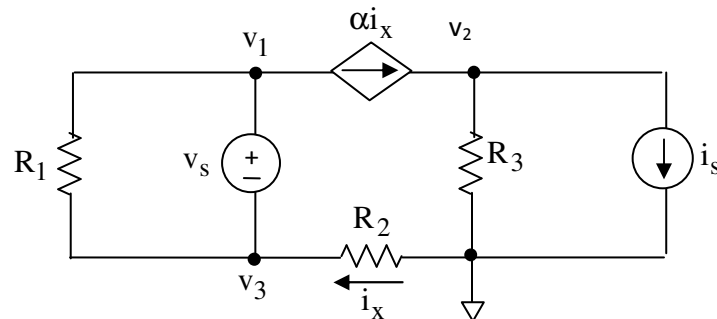6. For the circuit shown, write three independent equations for the node voltages  $v_1$ ,  $v_2$ , and  $v_3$ . The quantity  $i_x$  must not appear in the equations.




7. Make a consistency check on your equations for Problem 1 by setting resistors and sources to values for which the values of  $v_1$ ,  $v_2$ , and  $v_3$  are obvious. State the values of resistors, sources, and node voltages for your consistency check, and show that your equations for Problem 1 are satisfied for these values. (In other words, plug the values into your equations for Problem 1 and show that the left side and the right side of each equations are equal.)

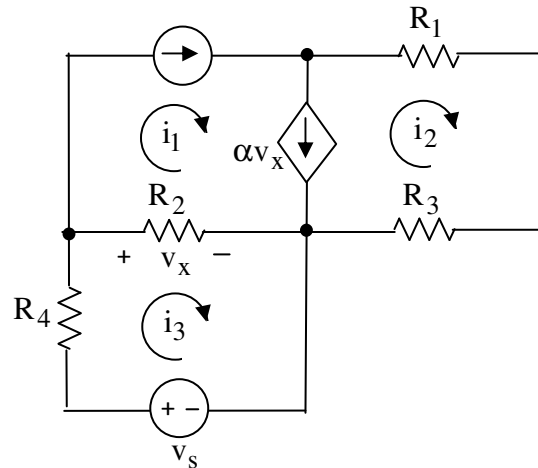8. For the circuit shown, write three independent equations for the three mesh currents,  $i_1$ ,  $i_2$ , and  $i_3$ . The quantity  $v_x$  must not appear in the equations.



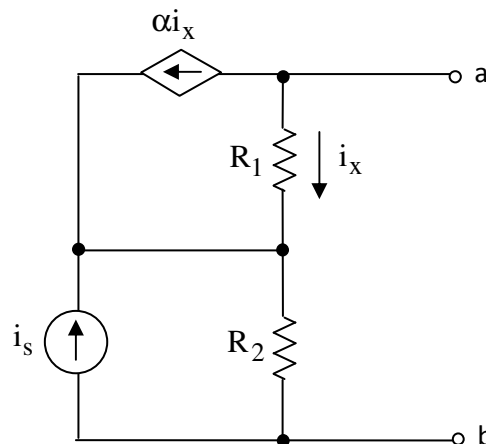9. Find the Thevenin equivalent circuit at terminals a and b. The quantity  $i_x$  must not appear in your solution. Note:  $\alpha > 0$ .



10. Calculate the power consumed (i.e. dissipated) by the  $i_x/2$  dependent source. Note: If a source supplies power, the power it consumes is negative.

