


UNIVERSITY OF UTAH  
ELECTRICAL & COMPUTER ENGINEERING DEPARTMENT

ECE 1270

**HOMEWORK #5**


Summer 2009

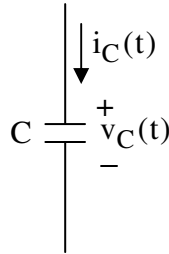1. In a-c, the voltage  $v_C(t)$  across a 10nF capacitor is listed. Find the current,  $i_C(t)$ , flowing in the capacitor in each case as a function of time:



- (a)  $v_C(t) = 6V$
- (b)  $v_C(t) = 42t \text{ kV/sec}$
- (c)  $v_C(t) = 1 - e^{-t/2\mu\text{sec}} V$

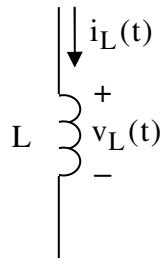2. In a-c, the current  $i_L(t)$  flowing into a  $6\mu\text{H}$  inductor is listed. Find the voltage,  $v_L(t)$ , across the inductor in each case as a function of time.



- (a)  $i_L(t) = 9\text{mA}$
- (b)  $i_L(t) = 15t\mu\text{A / sec}$
- (c)  $i_L(t) = 8\cos(2\pi \times 5 \times t)\text{A}$


3. The following equation describes the voltage,  $v_C$ , across a capacitor as a function of time. Find the time,  $t$ , at which  $v_C$  is equal to  $-6V$ . Plot  $v_C(t)$ . You may use Matlab.

$$v_C(t) = -12 + 12\left(1 - e^{-t/10\mu\text{s}}\right) V$$


4. The following equation describes the voltage,  $v_L$ , across an inductor as a function of time. Find an expression for the current,  $i_L(t)$ , through the inductor as a function of time. Assume that  $i_L(t = 0) = 0A$ . Plot  $i_L(t)$ . You may use Matlab.

$$v_L(t) = 6 - 2e^{-t/50\text{ms}} \text{V}$$

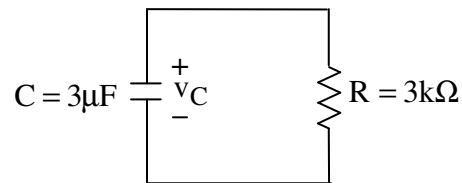
5. Find the voltage,  $v_C$ , on the capacitor in the circuit below as a function of time if the initial condition is,  $v_C(t = 0^+) = 3V$ .



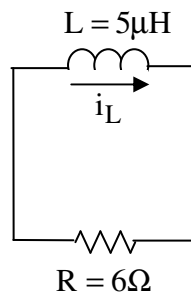
6. Find the current,  $i_L$ , through the inductor in the circuit below for  $t > 0$  if the initial condition is  $i_L(t = 0) = 3\text{mA}$ .



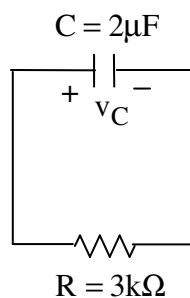7. Find the voltage,  $v_C$ , across the capacitor in the circuit below for  $t > 0$  if  $v_C(t = 0) = 15V$ .




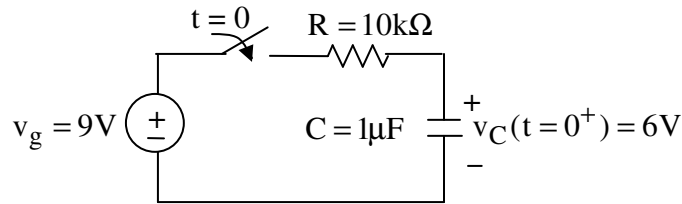8. After being open for a long time, the switch closes at  $t = 0$ .




- (a) Find an expression for  $v_C(t)$  for  $t \geq 0$ .
- (b) Find the energy stored in the capacitor at time  $t = 10$  ms.

9.

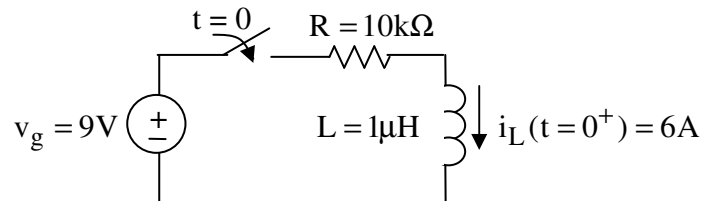

- (a) Find an expression for  $i_L(t)$  for  $t \geq 0$ . Note: Assume the initial current in the L is created by circuitry not shown in the diagram.
- (b) Find the energy stored in the inductor at time  $t = 10$  ms.

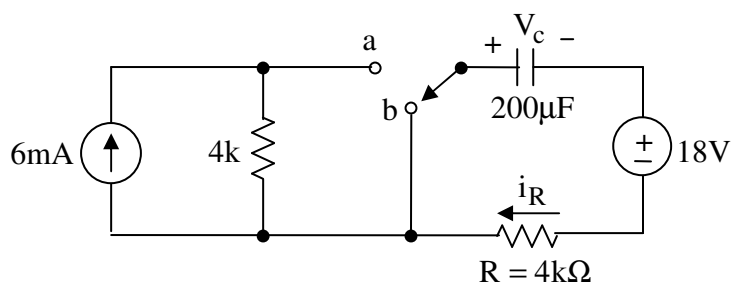10. The switch has been in a position a for a long time. It switched to position b at  $t = 0$ .



- (a) Find an expression for  $V_c(t)$  for  $t > 0$ .
- (b) Find the current,  $i_R$ , in R as a function of time.


UNIVERSITY OF UTAH  
ELECTRICAL & COMPUTER ENGINEERING DEPARTMENT

ECE 1270

**HOMEWORK #5**


Summer 2009

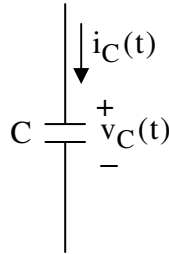1. In a-c, the voltage  $v_C(t)$  across a 10nF capacitor is listed. Find the current,  $i_C(t)$ , flowing in the capacitor in each case as a function of time:



- (a)  $v_C(t) = 6V$
- (b)  $v_C(t) = 42t \text{ kV/sec}$
- (c)  $v_C(t) = 1 - e^{-t/2\mu\text{sec}} V$

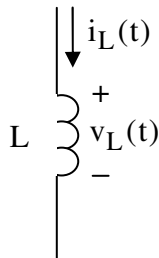2. In a-c, the current  $i_L(t)$  flowing into a 6 $\mu$ H inductor is listed. Find the voltage,  $v_L(t)$ , across the inductor in each case as a function of time.



- (a)  $i_L(t) = 9\text{mA}$
- (b)  $i_L(t) = 15t\mu\text{A} / \text{sec}$
- (c)  $i_L(t) = 8\cos(2\pi \times 5 \times t)\text{A}$


3. The following equation describes the voltage,  $v_C$ , across a capacitor as a function of time. Find the time,  $t$ , at which  $v_C$  is equal to -6V. Plot  $v_C(t)$ . You may use Matlab.

$$v_C(t) = -12 + 12\left(1 - e^{-t/10\mu\text{s}}\right) V$$


4. The following equation describes the voltage,  $v_L$ , across an inductor as a function of time. Find an expression for the current,  $i_L(t)$ , through the inductor as a function of time. Assume that  $i_L(t = 0) = 0A$ . Plot  $i_L(t)$ . You may use Matlab.

$$v_L(t) = 6 - 2e^{-t/50\text{ms}} \text{V}$$

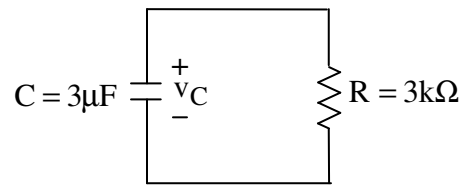
5. Find the voltage,  $v_C$ , on the capacitor in the circuit below as a function of time if the initial condition is,  $v_C(t = 0^+) = 3V$ .



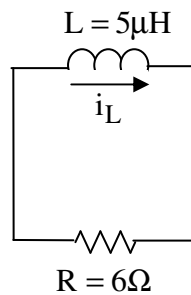
6. Find the current,  $i_L$ , through the inductor in the circuit below for  $t > 0$  if the initial condition is  $i_L(t = 0) = 3\text{mA}$ .



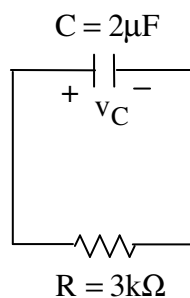7. Find the voltage,  $v_C$ , across the capacitor in the circuit below for  $t > 0$  if  $v_C(t = 0) = 15V$ .




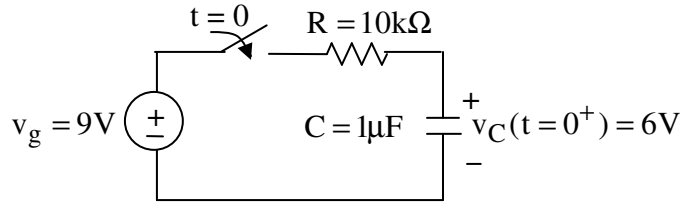8. After being open for a long time, the switch closes at  $t = 0$ .




- (a) Find an expression for  $v_C(t)$  for  $t \geq 0$ .
- (b) Find the energy stored in the capacitor at time  $t = 10$  ms.

9.

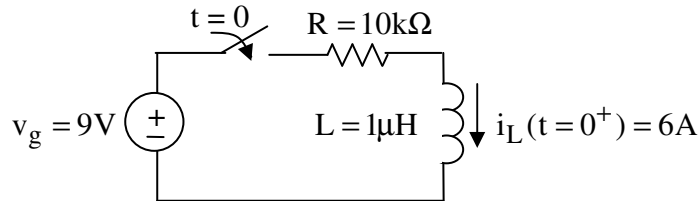

- (a) Find an expression for  $i_L(t)$  for  $t \geq 0$ . Note: Assume the initial current in the L is created by circuitry not shown in the diagram.
- (b) Find the energy stored in the inductor at time  $t = 10$  ms.

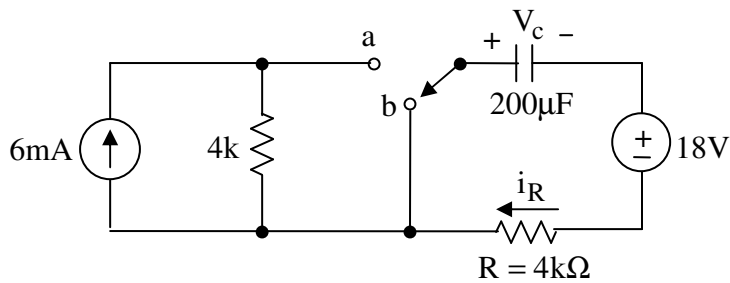10. The switch has been in a position a for a long time. It switched to position b at  $t = 0$ .



- (a) Find an expression for  $V_c(t)$  for  $t > 0$ .
- (b) Find the current,  $i_R$ , in R as a function of time.