


UNIVERSITY OF UTAH  
ELECTRICAL & COMPUTER ENGINEERING DEPARTMENT

ECE 1270


**HOMEWORK #6**

Summer 2009

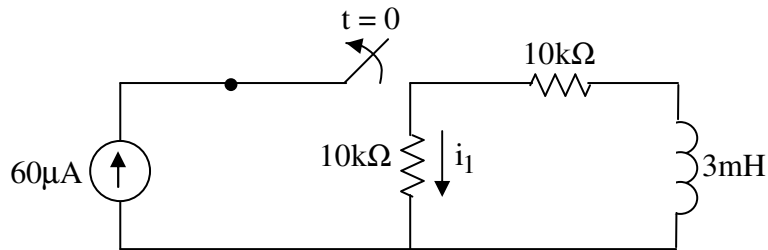
1. After being closed a long time, the switch opens at  $t = 0$ . Find  $i_1(t)$  for  $t > 0$ .



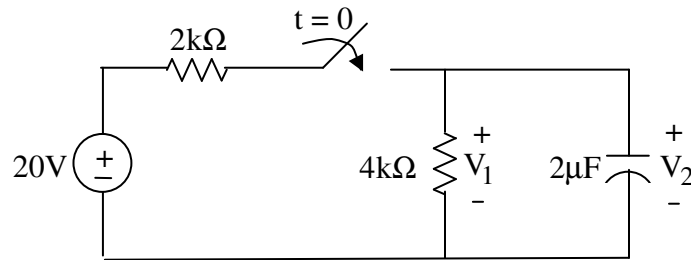
2. After being open for a long time, the switch closes at  $t = 0$ . Find  $V_1(t)$  for  $t > 0$ .



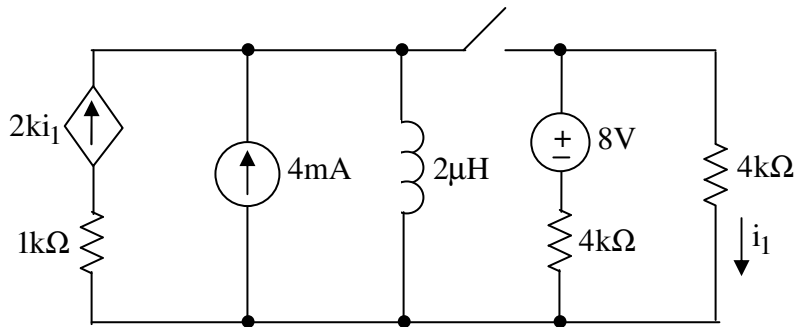
3. After being open for a long time, the switch closes at  $t = 0$ . Find  $i_1(t)$  for  $t > 0$ .



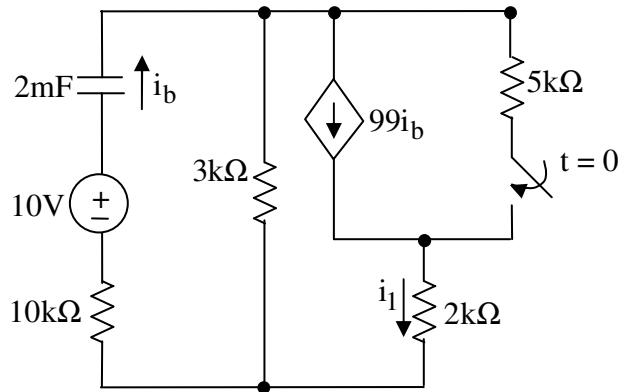
4. After being open for a long time, the switch closes at  $t = 0$ . Find  $i_1(t)$  for  $t > 0$ .



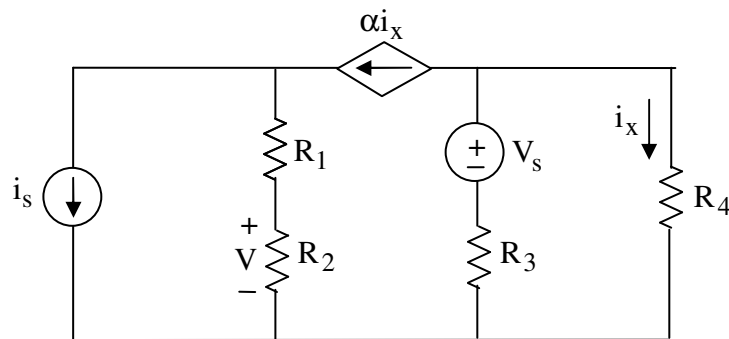
5. Using superposition, derive an expression for  $V$  that contains no circuit quantities other than  $i_s$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ ,  $\alpha$ , or  $V_s$ .



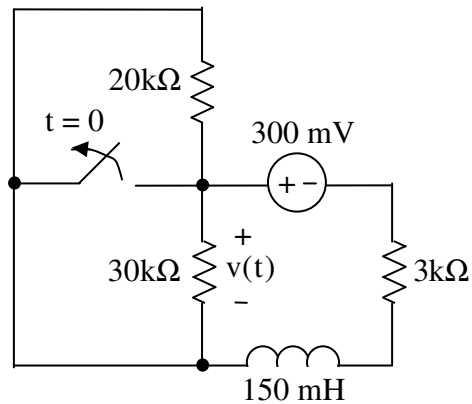6. After being closed for a long time, the switch opens at  $t=0$ .  
 a) Calculate the energy stored on the inductor as  $t \rightarrow \infty$ .  
 b) Write a numerical expression for  $v(t)$  for  $t > 0$ .




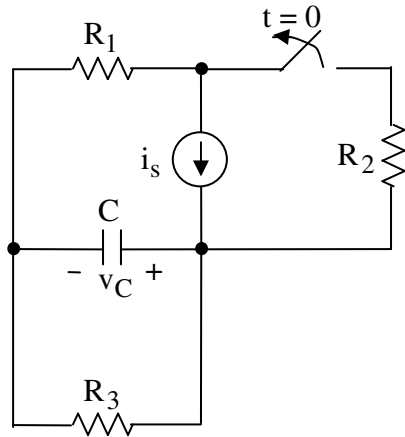7. After being open for a long time, the switch closes at  $t=0$ .
- Write an expression for  $v_c(t=0^+)$ .
  - Write an expression for  $v_c(t>0)$  in terms of  $i_s$ ,  $R_1$ ,  $R_2$ ,  $R_3$ , and  $C$ .



Use the circuit below for both problem 8 and 9.

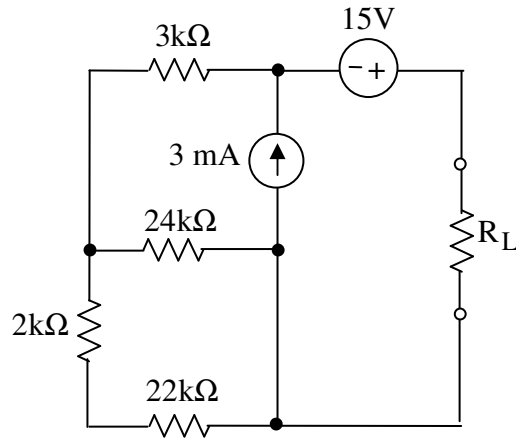- Calculate the value of  $R_L$  that would absorb maximum power.
- Calculate that value of maximum power  $R_L$  could absorb.



10. Using superposition, derive an expression for  $i$  that contains no circuit quantities other than  $i_s$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ ,  $\alpha$ , or  $V_s$ .

