



1. Plot each of the following complex numbers as vector in the complex plane:
 - a. $(3-3j)$
 - b. $e^{j\pi/4}$
 - c. $\frac{1+j}{2} - \frac{1-j}{4}$
 - d. $\frac{1}{j^3}$
 - e. $\frac{1-j}{-1+j}$

2. Give numerical answers to each of the following questions:
 - a. Rationalize $\frac{-80-j60}{28-j96}$. Express your answer in rectangular form.
 - b. Find the polar form of $(1+j)^* \left(\sqrt{1+\frac{\sqrt{3}}{2}} - j\sqrt{1-\frac{\sqrt{3}}{2}} \right)^*$ (Note: The asterisk means conjugate.)
 - c. Find the following phasor: $P[3\sin(25kt-120^\circ)]$.
 - d. Find the magnitude of $\frac{(1-j7)2e^{-j10^\circ}}{1-e^{j90^\circ}}$.
 - e. Find the imaginary part of $\frac{1+j\sqrt{3}}{e^{-j30^\circ}}$.


3.
 - a. Write phasors (as both $Ae^{j\phi}$ and $A\angle\phi$) for each of the following signals:
 - i. $v(t)=9\cos(2kt+30^\circ)V$
 - ii. $i(t)=2\sin(\omega t+10^\circ)mA$
 - iii. $v(t)=\cos(5t+30^\circ)V+5\sin(5t-30^\circ)V$

 - b. Given $w=3krad/sec$, write inverse phasors for each of the following signals:
 - i. $\mathbf{I}=34e^{j20^\circ} A$
 - ii. $\mathbf{V}=-j^3 V$
 - iii. $\mathbf{I}=3e^{+\pi-j20^\circ} A$

4.

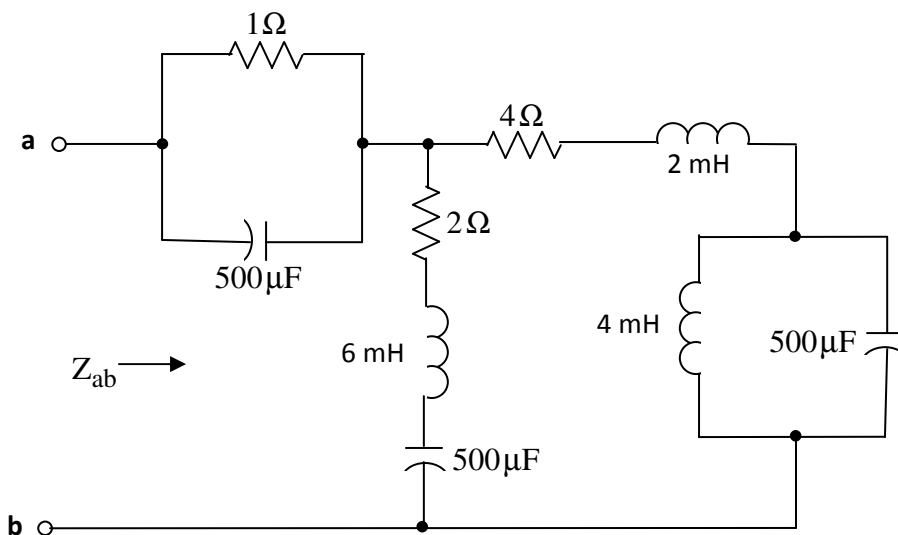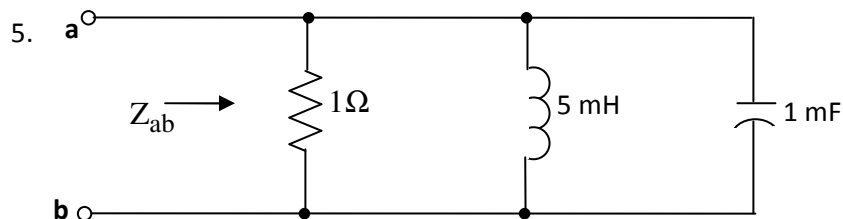Given $\omega = 1\text{k rad/sec}$, find Z_{ab} .Given $\omega = 447 \text{ rad/sec}$, find Z_{ab} .


6.

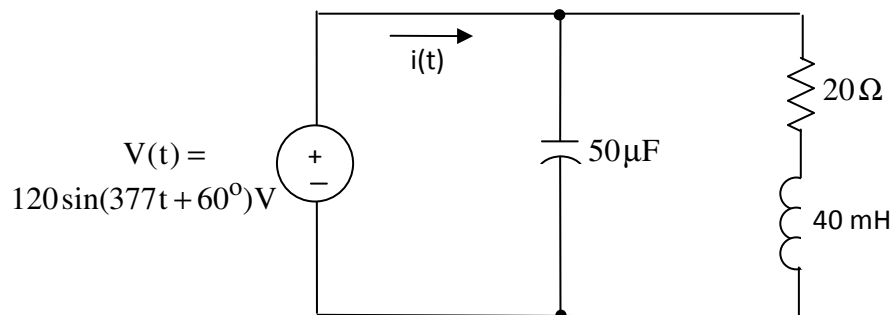

- Find the phasor value for $V(t)$.
- Draw the frequency-domain circuit diagram, including the phasor value for $V(t)$ and the impedance values for components.

7. Find the phasor value for $i(t)$ from the circuit in Problem 6.


8.

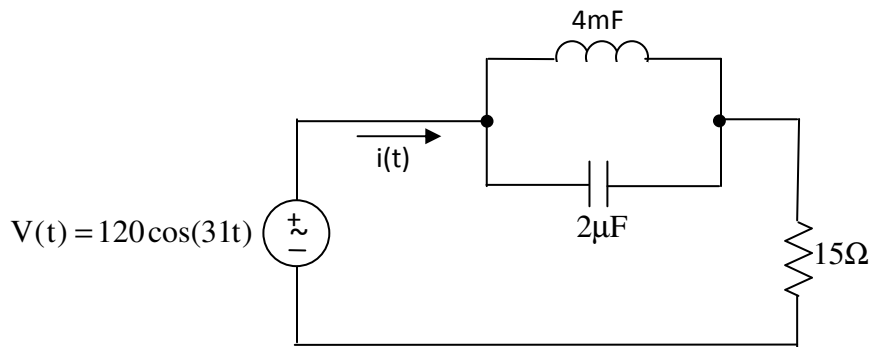

- Find the phasor value for $V(t)$.
- Draw the frequency-domain circuit diagram, including the phasor value for $V(t)$ and the impedance values for components.

9. Find the phasor value for $i(t)$ for the circuit in Problem 8.

10.

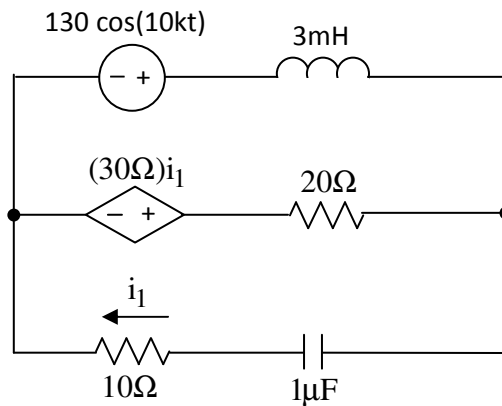Find $i_1(t)$.