
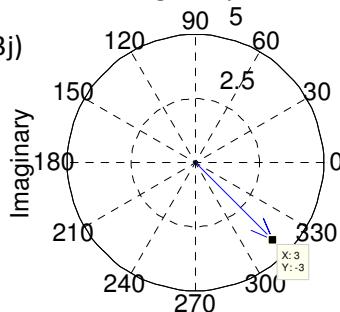


1. Plot each of the following complex numbers as vector in the complex plane:


a.  $(3-3j)$

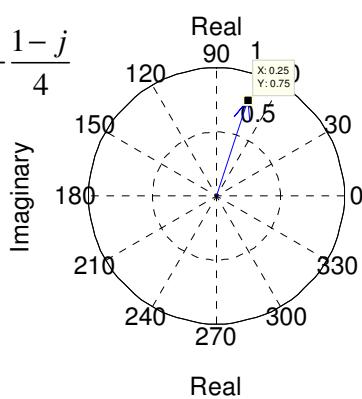


c.  $\frac{1+j}{2} - \frac{1-j}{4}$




e.  $\frac{1-j}{-1+j}$

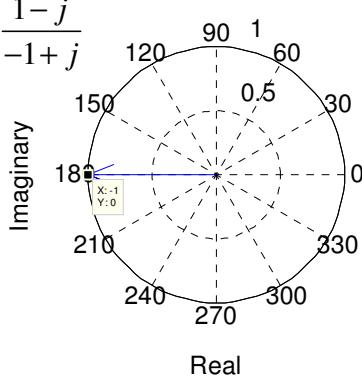

b.  $e^{j\pi/4}$

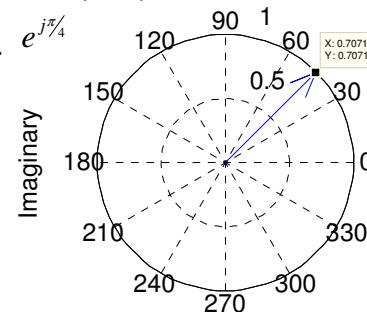

d.  $\frac{1}{j^3}$

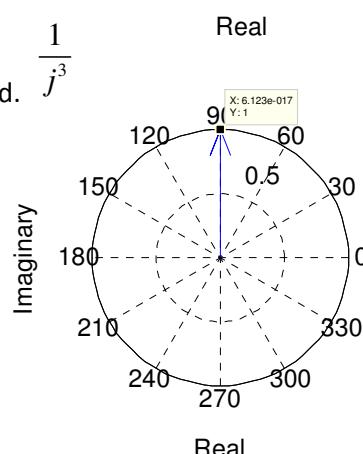

2. Give numerical answers to each of the following questions:

a. Rationalize  $\frac{-80-j60}{28-j96}$ . Express your answer in rectangular form.

$$\frac{-80-j60}{28-j96} = \frac{-80-j60}{28-j96} \cdot \frac{28+j96}{28+j96} = \frac{3520-j9360}{10k} = 0.352 - j0.936$$

- b. Find the polar form of  $(1+j)^*$   $\left( \sqrt{1+\frac{\sqrt{3}}{2}} - j\sqrt{1-\frac{\sqrt{3}}{2}} \right)^*$  (Note: The asterisk means conjugate.)

$$\begin{aligned}
 & (1+j)^* \left( \sqrt{1+\frac{\sqrt{3}}{2}} - j\sqrt{1-\frac{\sqrt{3}}{2}} \right)^* \\
 &= (1-j) \left( \sqrt{1+\frac{\sqrt{3}}{2}} + j\sqrt{1-\frac{\sqrt{3}}{2}} \right) \\
 &= \sqrt{2} \angle -45^\circ \cdot \sqrt{\sqrt{1+\frac{\sqrt{3}}{2}}^2 + \sqrt{1-\frac{\sqrt{3}}{2}}^2} \angle \tan^{-1} \left( \frac{\sqrt{1-\frac{\sqrt{3}}{2}}}{\sqrt{1+\frac{\sqrt{3}}{2}}} \right) \\
 &= \sqrt{2} \angle -45^\circ \cdot \sqrt{1+\frac{\sqrt{3}}{2} + 1-\frac{\sqrt{3}}{2}} \angle \tan^{-1} \left( \frac{\sqrt{1-\frac{\sqrt{3}}{2}}}{\sqrt{1+\frac{\sqrt{3}}{2}}} \right) \\
 &= \sqrt{2} \angle -45^\circ \cdot \sqrt{2} \angle 15^\circ = 2 \angle -30^\circ
 \end{aligned}$$

- c. Find the following phasor:  $P[3\sin(25kt - 120^\circ)]$ .

$$\begin{aligned}
 P[3\sin(25kt - 120^\circ)] &= -j3 \angle -120^\circ = 1 \angle -90^\circ \cdot 3 \angle -120^\circ \\
 &= 3 \angle -210^\circ = 3 \angle 150^\circ
 \end{aligned}$$

- d. Find the magnitude of  $\frac{(1-j7)2e^{-j10^\circ}}{1-e^{j90^\circ}}$ .

d) The magnitude of a product or quotient is the product or quotient of the magnitudes:

$$\left| \frac{(1-j7)2e^{-j10^\circ}}{1-e^{j90^\circ}} \right| = \frac{|1-j7|2|e^{-j10^\circ}|}{|1-e^{j90^\circ}|}$$

$|e^{-j\theta}| = 1$  for any real  $\theta$ , and  $e^{j90^\circ} = j$ :

$$\left| \frac{(1-j7)2e^{-j10^\circ}}{1-e^{j90^\circ}} \right| = \frac{\sqrt{1^2 + 7^2} \cdot 2 \cdot 1}{|1-j|} = \frac{\sqrt{50} \cdot 2 \cdot 1}{\sqrt{2}} = 10$$

or

$$\left| \frac{(1-j7)2e^{-j10^\circ}}{1-e^{j90^\circ}} \right| = \frac{\sqrt{50} \cdot 2 \cdot 1}{\sqrt{2}} = 10$$

- e. Find the imaginary part of  $\frac{1+j\sqrt{3}}{e^{-j30^\circ}}$ .

$$\operatorname{Im} \left[ \frac{1+j\sqrt{3}}{e^{-j30^\circ}} \right] = \operatorname{Im} \left[ \frac{1+j\sqrt{3}}{\frac{\sqrt{3}}{2} - j\frac{1}{2}} \right] = \operatorname{Im} \left[ \frac{1+j\sqrt{3}}{\frac{\sqrt{3}}{2} - j\frac{1}{2}} \cdot \frac{\frac{\sqrt{3}}{2} + j\frac{1}{2}}{\frac{\sqrt{3}}{2} + j\frac{1}{2}} \right]$$

or

$$\operatorname{Im} \left[ \frac{1+j\sqrt{3}}{e^{-j30^\circ}} \right] = \operatorname{Im} \left[ \frac{\frac{\sqrt{3}}{2} - \frac{\sqrt{3}}{2} + j\left(\frac{3}{2} + \frac{1}{2}\right)}{1} \right]$$

or

$$\operatorname{Im} \left[ \frac{1+j\sqrt{3}}{e^{-j30^\circ}} \right] = \operatorname{Im} [j2] = 2$$

3. a. Write phasors (as both  $Ae^{j\phi}$  and  $A\angle\phi$ ) for each of the following signals:

i.  $v(t)=9\cos(2kt+30^\circ)V \Rightarrow V=9e^{j30}$

ii.  $i(t)=2\sin(\omega t+10^\circ)mA=2\cos(\omega t-90^\circ+10^\circ)mA \Rightarrow I=2e^{-j80}$

iii.  $v(t)=\cos(5t+30^\circ)V+5\sin(5t-30^\circ)V=$   
 $V=e^{j30}+5e^{j-120}=\cos(30)+j\sin(30)+5\cos(-120)+j\sin(-120)=-1.6340 - 3.8301j$   
 $\Rightarrow V=4.2e^{j247}$


- b. Given  $w=3\text{krad/sec}$ , write inverse phasors for each of the following signals:

i.  $I=34e^{j20^\circ} A \Rightarrow i(t)=34\cos(3kt+20^\circ)A$


ii.  $V=-j^3V \Rightarrow v(t)=\cos(3kt+90^\circ)V$

iii.  $I=3e^{+\pi-j20^\circ} A \Rightarrow i(t)=3e^{+\pi}\cos(3kt-20^\circ)A$

4.

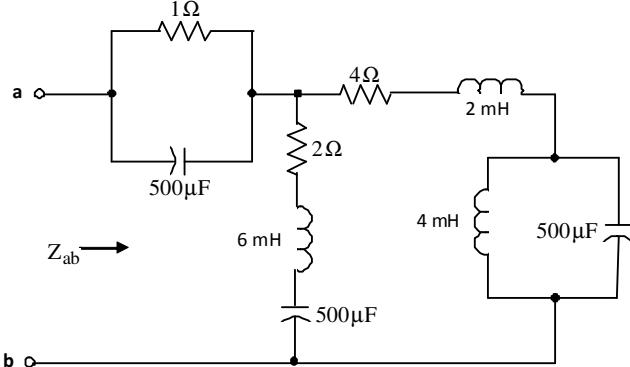Given  $\omega = 1k \text{ rad/sec}$ , find  $Z_{ab}$ .

## HOMWORK #1 SOLUTIONS

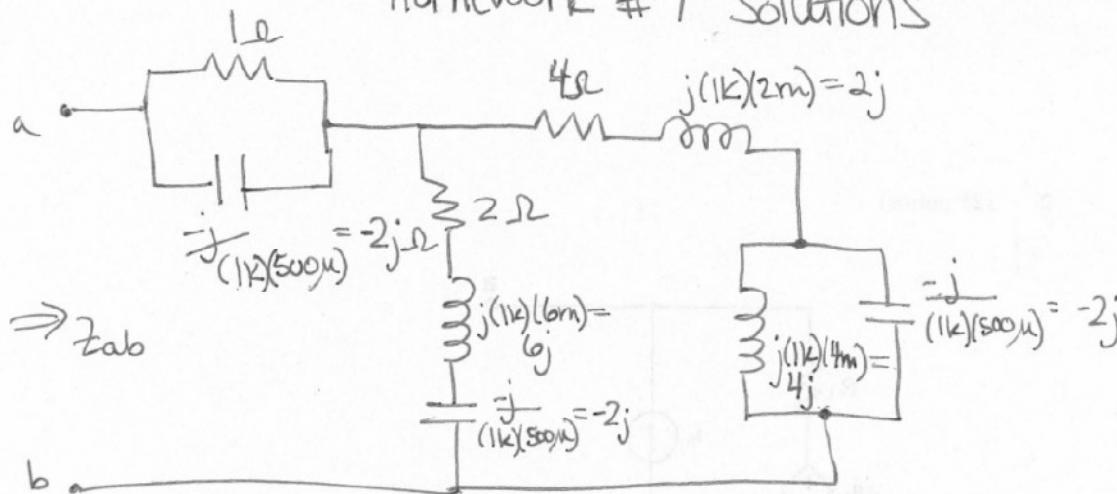

$$Z_{ab} = (1 \parallel -2j) + (2 + (j - 2j)) \parallel [(4 + 2j) + (4j \parallel -2j)]$$

$$Z_{ab} = \frac{1(-2j)}{1-2j} + (2+4j) \parallel (4+2j + \frac{4j(-2j)}{4j-2j}) = \frac{-2j}{1-2j} + (2+4j) \parallel (4+2j + \frac{8j}{2j})$$



$$Z_{ab} = \frac{-2j(1+2j)}{(1-2j)(1+2j)} + \frac{(2+4j)(4-2j)}{(2+4j+4-2j)} = \frac{-2j+4}{5} + \frac{8-4j+16j-8j^2}{6+2j}$$

$$Z_{ab} = -\frac{2}{5}j + \frac{4}{5} + \frac{16+12j}{6+2j} \approx -\frac{2}{5}j + \frac{4}{5} + \frac{20e^{j37^\circ}}{2\sqrt{10} e^{j18^\circ}} = -\frac{2}{5}j + \frac{4}{5} + 3.16 e^{j19^\circ}$$

$$Z_{ab} = -\frac{2}{5}j + \frac{4}{5} + 3.16 \cos(19^\circ) + 3.16j \sin(19^\circ)$$

$$Z_{ab} \approx -\frac{2}{5}j + \frac{4}{5} + 3 + j = \boxed{(3.8 + 0.6j) \Omega}$$


5.

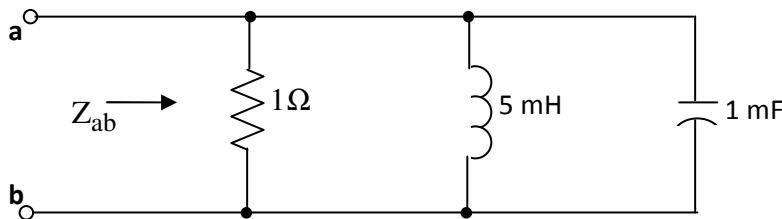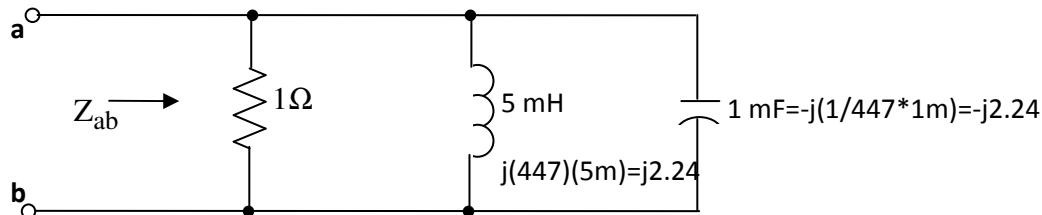Given  $\omega = 447$  rad/sec, find  $Z_{ab}$ .

$$\begin{aligned}
 Z_{ab} &= 1 \parallel j2.24 \parallel -j2.24 = \frac{1}{\frac{1}{1} + \frac{1}{j2.24} + \frac{1}{-j2.24}} = \frac{1}{\frac{-j2.24}{-j2.24} + \frac{-1}{-j2.24} + \frac{1}{-j2.24}} \\
 &= \frac{1}{\frac{-j2.24}{-j2.24}} = 1
 \end{aligned}$$

6 and 7.
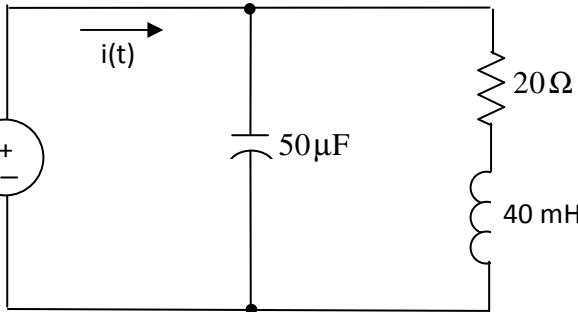
$$\begin{aligned}
 V(t) &= \\
 120\sin(377t+60^\circ)V
 \end{aligned}$$




- a. Find the phasor value for  $V(t)$ .  
 b. Draw the frequency-domain circuit diagram, including the phasor value for  $V(t)$  and the impedance values for components.

a.  $v(t) = 120 \sin(377t + 60^\circ) = 120 \cos(377t + 60^\circ - 90^\circ)$

$\boxed{V = 120 \angle -30^\circ}$  or  $\boxed{V = 120e^{-j30^\circ}}$

b.

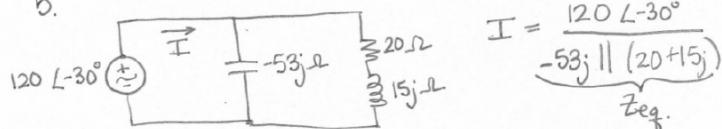

$$I = \frac{120 \angle -30^\circ}{-53j \parallel (20 + 15j)}$$

$\underbrace{\hspace{1cm}}_{Z_{eq.}}$


$$Z_{eq.} = \frac{-53j(20+15j)}{20-53j+15j} = \frac{-1060j+795}{(20-38j)} = \frac{1325 \angle -53^\circ}{43 \angle -62^\circ} = 30.8 \angle 9^\circ$$

$$I = \frac{120 \angle -30^\circ}{30.8 \angle 9^\circ} \approx 4 \angle (-30^\circ - 9^\circ) = \boxed{4 \angle -39^\circ} \text{ or } 4e^{-j39^\circ} \text{ OR } 4\angle^{321^\circ}$$

$i(t) \approx 4 \cos(377t - 39^\circ) A$

8 and 9.

$$V(t) = 120 \cos(31t)$$

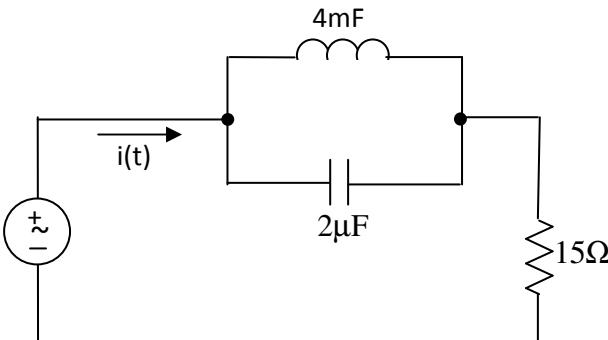


- a. Find the phasor value for  $V(t)$ .
- b. Draw the frequency-domain circuit diagram, including the phasor value for  $V(t)$  and the impedance values for components.
9. Find the phasor value for  $i(t)$  for the circuit in Problem 8.

a) Find the phasor value for  $V(t)$

$$V(t) = 120 \cos(31t) = 120 \angle 0^\circ \text{ V}$$

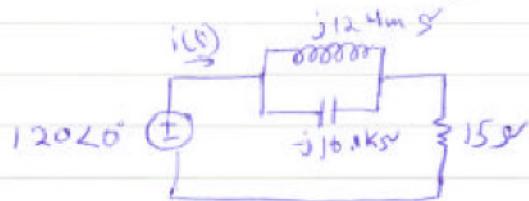b) Draw the frequency-domain circuit diagram



$$Z_L = j31 \times 4m = j12.4 \text{ m } \Omega$$

$$Z_C = \frac{-j}{31 \times 2\pi} = -j16.1 \text{ k } \Omega$$


$$i(t) = \frac{v(t)}{Z}$$

$$Z = (Z_L \parallel Z_C) + 15$$

$$= \frac{-j16.1 \text{ k} \times j12.4 \text{ m}}{j12.4 \text{ m} \parallel j16.1 \text{ k}} + 15 = \frac{2 \text{ k}}{-j16.1 \text{ k}} + 15 = j0.124 + 15$$

$$Z = 15e^{j0.473}$$

$$I = 120/Z = 8e^{-j0.473}$$

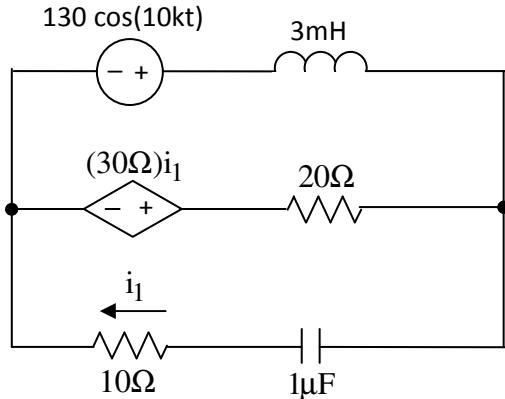10. Find  $i_1(t)$ .

Take the lower loop

$$(30\Omega)i_1 - 20i_2 - \frac{-j}{10 \times 10^3} i_1 - 10i_1 = 0$$

$$(30\Omega)i_1 - 20i_2 + j100i_1 - 10i_1 = 0$$

$$20i_2 = 30i_1 - 10i_1 + j100i_1$$

$$i_2 = i_1 + j5i_1 = i_1 \cdot 5.1 \angle \tan^{-1}\left(\frac{5}{1}\right)$$

$$i_2 = i_1 \cdot 5.1 \angle 78.7^\circ$$

$$i = i_1 - i_2$$

$$i = \frac{V(t)}{Z} \quad , \quad \omega = 10k \text{ rad/sec}$$

$$Z = j \times 10k \times 3m + ((Z_{eq} + 20\Omega) // \left(\frac{-j}{10k \times 10^3} + 10\Omega\right))$$

$Z_{eq}$  is impedance of the dependant source.

$$Z_{eq} = \frac{V}{i} = \frac{30i_1}{i_2} = \frac{30i_1}{i_1 \cdot 5.1 \angle 78.7^\circ} = 5.88 \angle -78.7^\circ$$

$$\text{or } \frac{30i_1}{i_1 + j5i_1} = \frac{30(1-j5)}{1+25} = 1.15 - j5.77$$

$$\begin{aligned}
 Z &= j30 + ((1.15 - j5.77 + 20) // (-j100 + 10)) \\
 &= j30 + ((21.15 - j5.77) // (-j100 + 10)) \\
 &= j30 + \frac{(21.15 - j5.77)(-j100 + 10)}{21.15 - j5.77 - j100 + 10} \\
 &= j30 + \frac{-j21.15k + 211.5 - 577 - j57.7}{31.15 - j105.77} \\
 &= j30 + \frac{-j2.16k - 365.5}{31.15 - j105.77} \times \frac{31.15 + j105.77}{31.15 + j105.77} \\
 &= j30 + \frac{-j67.3k - j38.7k + 228.5k - 11.4k}{12.16k} \\
 &= j30 + 17.85 - j8.72 \\
 &= 17.85 + j21.28 \\
 &= 27.77 \angle \tan^{-1} \frac{21.28}{17.85} \\
 &= 27.77 \angle 50^\circ \text{ SV}
 \end{aligned}$$

$$i = \frac{130 \angle 0^\circ}{27.77 \angle 50^\circ} = 4.68 \angle -50^\circ$$

$$\begin{aligned}
 i = i_1 - i_2 &= i_1 - i_1(1+j5) = i_1(1-1-j5) \\
 &\Rightarrow i = -j5 i_1
 \end{aligned}$$

$$i_1 = \frac{i}{-j5} = \frac{j}{5} i = \frac{1}{5} \angle 90^\circ i$$

$$i_1 = 4.68 \angle -50^\circ \times 0.2 \angle 90^\circ = 0.936 \angle 40^\circ A$$

$$i(t) = 0.936 \cos(10kt + 40)$$