

for the directions drawn above:

$$I_1 = -19 - 0 = -19 \text{ mA} = \frac{8 \text{ k}\Omega}{19 \text{ mA}} \text{ (the negative means current flows from bottom to top)}$$

$$I_2 = -19 = \frac{10 \text{ k}\Omega}{-19} = -19 \text{ mA}$$



$$I_3 = -18 - (-6) = -12 = \frac{6 \text{ k}\Omega}{-12} = -2 \text{ mA}$$

$$I_4 = (V_2 - V_3) / (7 \text{ k}\Omega + 5 \text{ k}\Omega) = \frac{-15 - (-19)}{12 \text{ k}\Omega} = \frac{4}{12 \text{ k}\Omega} = \frac{1}{3} \text{ mA}$$


$$I_5 = (V_3 - V_4) / 6 \text{ k}\Omega = \frac{-19 - (-18)}{6 \text{ k}\Omega} = -\frac{1}{6} \text{ mA}$$

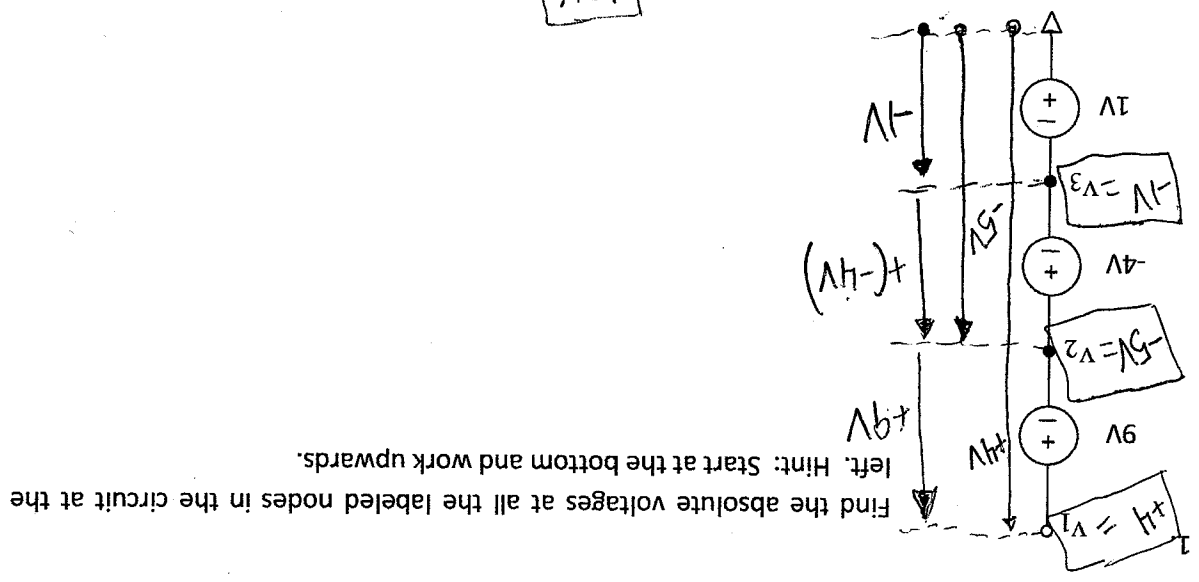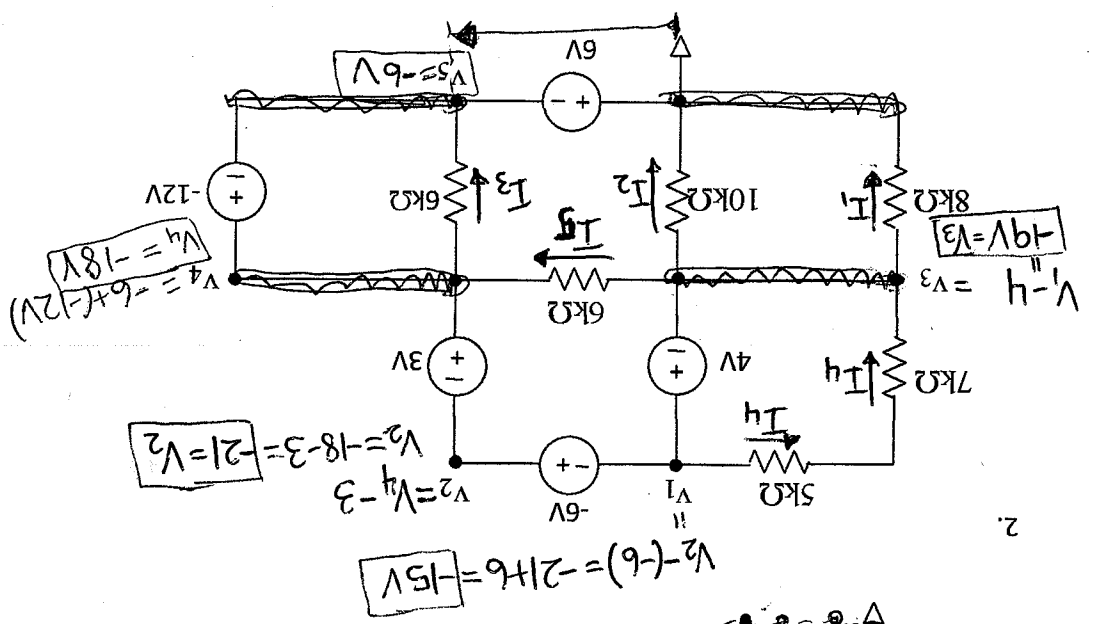3. Using Ohm's law and the node voltages found in Problem 2, find the currents for all the resistors in Problem 2. inspection.

Find the absolute voltages at all the labeled nodes in the above circuit. Hint: This may be done by inspection.




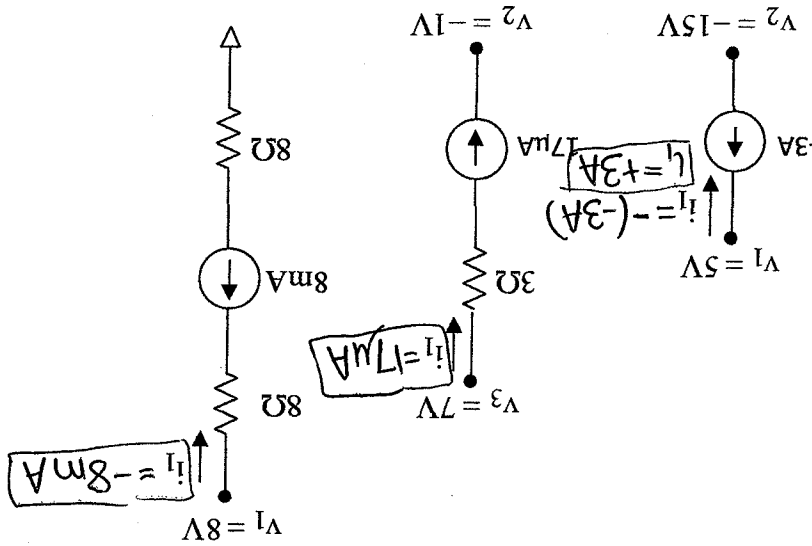Find the value of current,  $I_1$ , for each of the above circuits.



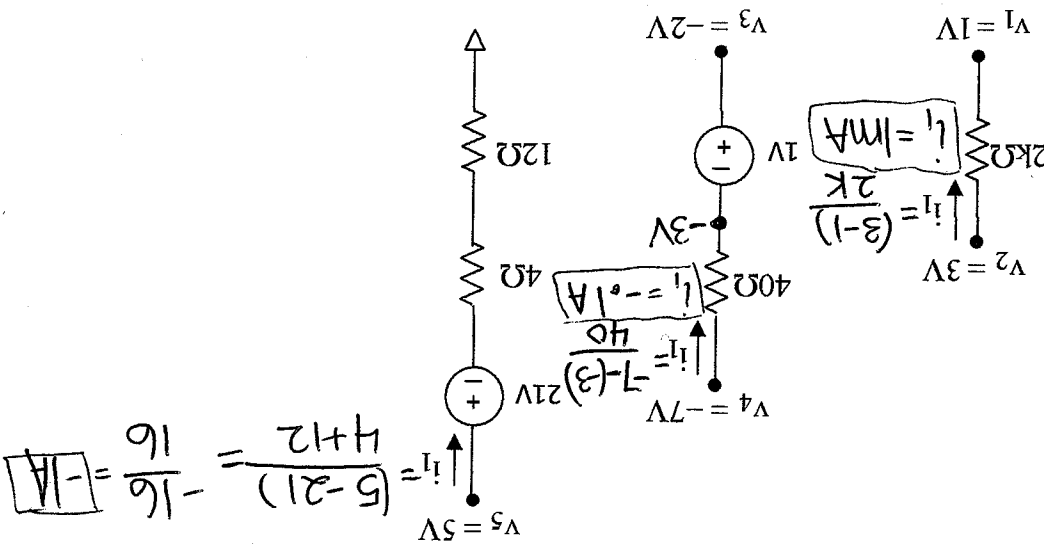5.

Find the value of current,  $I_1$ , for each of the above circuits.



4.

$$V_0 = V_1 = -12V$$

$$I_1 = \frac{V_1}{6\Omega} = -\frac{12}{6} = -2A$$

$$V_1 = -3.2 \left( \frac{16}{60} \right) = -12V$$


$$V_1 \left( \frac{60}{60} + \frac{60}{60} \right) = -3.2$$


$$V_1 \left( \frac{1}{6} + \frac{1}{10} \right) = -8 + 4.8$$

at  $V_1$  node:  $+8 + \frac{6}{V_1} + \frac{10}{(V_1 - 48)} = 0$

$$V_1 = V_0$$

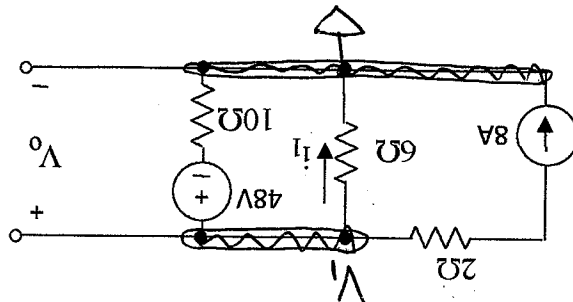Use the node-voltage method to find  $I_1$  and  $V_0$ .



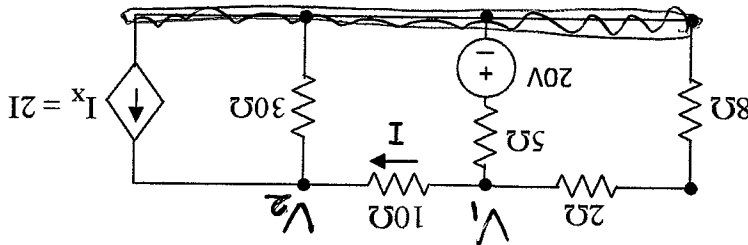

Use the node-voltage method to determine  $I_x$ .

$$\textcircled{1} \quad V_1 - 20 + \frac{5}{V_1} + \frac{10}{V_1} + \frac{10}{(V_1 - V_2)} = 0$$

$$\textcircled{2} \quad -(V_2 - V_1) + \frac{10}{V_2} - 2I = 0$$

$$I = \frac{10}{(V_1 - V_2)}$$

Rewrite  $\textcircled{2}$

$$(V_1 - V_2) \frac{10}{V_2} + \frac{30}{V_2} - 2(V_1 - V_2) \frac{10}{(V_1 - V_2)} = 0 \Rightarrow V_1 \left( \frac{1}{V_2} - \frac{1}{V_1} \right) + V_2 \left( \frac{1}{V_2} - \frac{1}{V_1} \right) = 0$$

Rewrite  $\textcircled{1}$


$$V_1 \left( \frac{1}{5} + \frac{1}{10} + \frac{1}{10} \right) = 4 + \frac{10}{V_2}$$

$$V_1 \left( \frac{2+1+1}{10} \right) = 4 + \frac{10}{V_2}$$

$$V_1 = \frac{4 + \frac{10}{V_2}}{\frac{4}{10}} = 4 \left( \frac{10}{4} \right) + \frac{10}{V_2} \left( \frac{10}{4} \right) = 10 + \frac{4}{V_2}$$

$$\textcircled{1} \rightarrow \textcircled{2} \quad \left( 10 + \frac{4}{V_2} \right) \left( -\frac{1}{10} \right) + V_2 \left( \frac{1}{-3+6} \right) = 0 \Rightarrow V_2 \left( -\frac{1}{3} + \frac{1}{6} + \frac{1}{10} \right) = +1$$
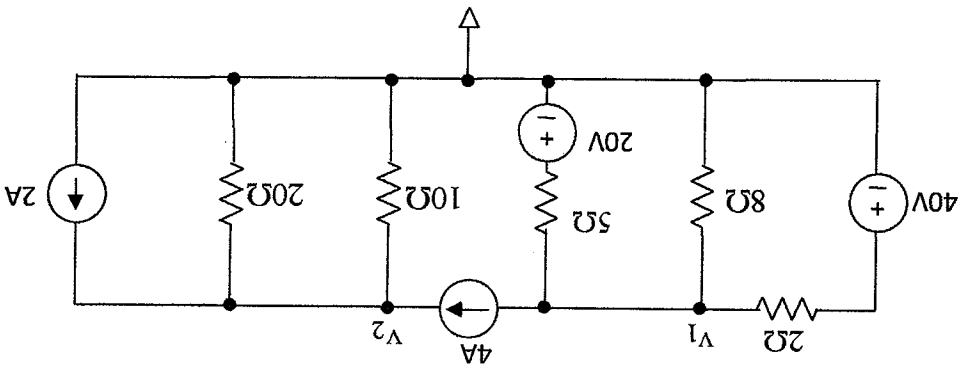
$$V_2 = \frac{13}{120} = 9.2V \Rightarrow V_1 = 10 + \frac{10}{120} \approx 12.3 \Rightarrow I = \frac{10}{(12.3 - 9.2)} = \boxed{0.3A}$$



a. Use the node-voltage method to find  $V_1$  and  $V_2$ .

b. Determine the amount of power supplied by the voltage source.

$$\textcircled{1} (V_1 - 40) + \frac{2}{8} + \frac{5}{V_1 - 20} + 4 = 0$$

$$\textcircled{2} -4 + \frac{V_2}{10} + \frac{20}{V_2} - 2 = 0$$

$$V_2 \left( \frac{1}{10} + \frac{20}{V_2} \right) = 6 \Rightarrow V_2 = \frac{6}{\frac{3}{20}} = 20(2) = 40V$$

$$\textcircled{1} V_1 \left( \frac{1}{2} + \frac{8}{V_1} + \frac{5}{V_1 - 20} \right) = 20 + 4 - 4$$


$$V_1 \left( \frac{20 + 5 + 8}{20} \right) = 20$$

$$V_1 = 20 \left( \frac{40}{33} \right) = \frac{800}{33} V$$

$$\text{power}_{-40V} = 40 \times (V_1 - 40) = 40 \times \left( \frac{800}{33} - 20 \right) = 40 \times \frac{2(33) - 20(33)}{33} = 40 \times \frac{5(33) - 4}{33} \approx -315W$$

$$\text{power}_{-20V} = 20 \times (V_1 - 20) = 20 \times \left( \frac{800}{33} - 20 \right) = 20 \times \frac{5(33) - 4}{33} \approx +17W$$

(remember - means supplying)

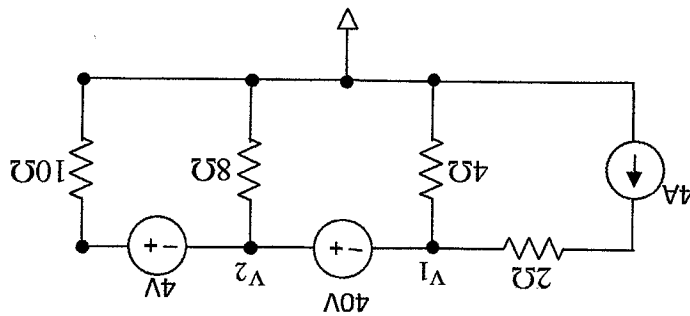

Use the node-voltage method to find  $V_1$  and  $V_2$ .

$$-4 + \frac{V_1}{4} + \frac{8}{V_2} + (V_2 + 4) \frac{10}{10} = 0$$

$$(V_2 - V_1) = 40$$

$$V_2 = V_1 + 40$$

$$-4 + (V_1 + 40) \left( \frac{1}{4} + \frac{1}{10} \right) + \frac{V_1}{4} + \frac{10}{4} = 0$$

$$-40 + 4 + V_1 \left( \frac{40}{5+4+10} \right) + 40 \left( \frac{10+8}{80} \right) = 0$$

$$V_1 \left( \frac{40}{19} \right) = \frac{36}{80} + \frac{10}{-40(18)}$$

$$V_1 = \left[ \frac{36}{80} - \frac{10}{40(18)} \right] \left( \frac{19}{40} \right) \approx -11.14 \text{ V}$$

$$V_2 = V_1 + 40 \approx +28.86 \text{ V}$$

$$V_1 = V_a \left( \frac{1}{4} \right) + V_2 \left( \frac{1}{2} \right) + \left( \frac{1}{4} + \frac{1}{2} \right) = 0$$

$$V_1 \left( \frac{1}{4} + \frac{1}{2} + \frac{1}{4} \right) + V_2 \left( \frac{1}{2} \right) = 0$$

$$V_1 \left( 1 + \frac{1}{2} + \frac{1}{4} \right) + (-V_a) - \frac{V_2}{4} = 0$$

$$V_1 \left( \frac{4+2+1}{4} \right) = V_a + \frac{V_2}{4}$$

$$V_1 = V_a \left( \frac{7}{4} \right) + V_2 \left( \frac{1}{4} \right)$$

$$\textcircled{1} \rightarrow \textcircled{2}: V_1 \left( -\frac{1}{4} + \frac{1}{2} \right) + V_2 \left( \frac{1}{4} + \frac{1}{4} + \frac{1}{4} \right) = 0$$

$$\left[ V_a \left( \frac{7}{4} \right) + V_2 \left( \frac{1}{4} \right) \right] \left( \frac{1}{4} \right) + V_2 \left( \frac{3}{4} \right) = 0$$

$$V_2 \left( \frac{1}{4} + \frac{21}{28} + \frac{21}{28} \right) = -V_a \left( \frac{7}{4} \right) \left( \frac{1}{4} \right)$$

$$V_2 = -V_a \left( \frac{1}{7} \right) \left( \frac{28}{28} \right) = -\frac{11}{28} V_a$$

$$V_1 = V_a \left( \frac{7}{4} \right) + \left( -\frac{11}{28} V_a \right) \left( \frac{1}{4} \right) = \left( \frac{77}{28} - \frac{11}{28} \right) V_a$$

$$V_1 = +\frac{11}{6} V_a$$

Use the node-voltage method to find  $V_1$  and  $V_2$ .

