


UNIVERSITY OF UTAH
ELECTRICAL & COMPUTER ENGINEERING DEPARTMENT

ECE 1270


HOMEWORK #5

Summer 2010

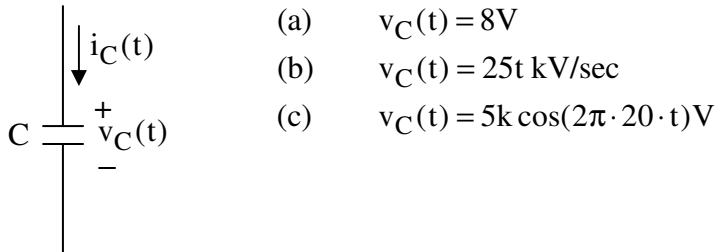1. In a-c, the voltage $v_C(t)$ across a 5nF capacitor is listed. Find the current, $i_C(t)$, flowing in the capacitor in each case as a function of time:



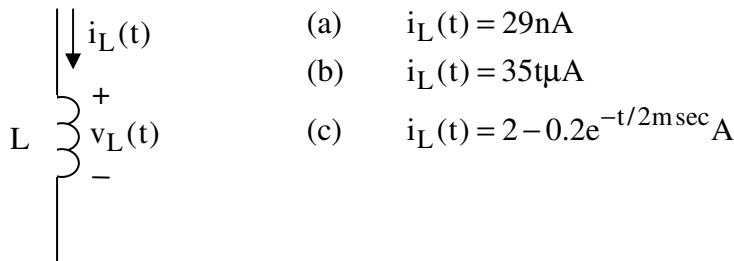2. In a-c, the current $i_L(t)$ flowing into a 3μH inductor is listed. Find the voltage, $v_L(t)$, across the inductor in each case as a function of time.




3. The following equation describes the voltage, v_C , across a capacitor as a function of time. Find the time, t , at which v_C is equal to -6V. Plot $v_C(t)$. You may use Matlab.

$$v_C(t) = 6 - 6(1 - e^{-t/10\mu s}) V$$


4. The following equation describes the voltage, v_L , across an inductor as a function of time. Find an expression for the current, $i_L(t)$, through the inductor as a function of time. Assume that $i_L(t=0) = 0A$. Plot $i_L(t)$. You may use Matlab.

$$v_L(t) = 2e^{-t/20\text{ms}} V$$

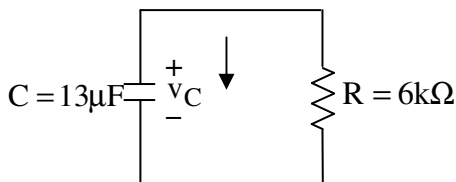
5. Find the voltage, v_C , on the capacitor in the circuit below as a function of time if the initial condition is $v_C(t=0^+) = 2V$.



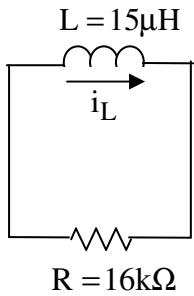6. Find the current, i_L , through the inductor in the circuit below for $t > 0$ if $i_L(t = 0) = 13\text{mA}$.



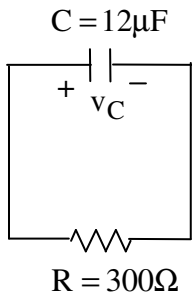
7. Find the voltage, v_C , across the capacitor in the circuit below for $t > 0$ if $v_C(t = 0) = 5\text{V}$.




8. After being open for a long time, the switch closes at $t = 0$.

(a) Find an expression for $v_C(t)$ for $t \geq 0$.

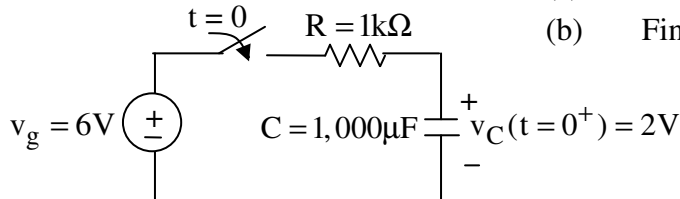(b) Find the energy stored in the capacitor at time $t = 2\text{s}$.




9.

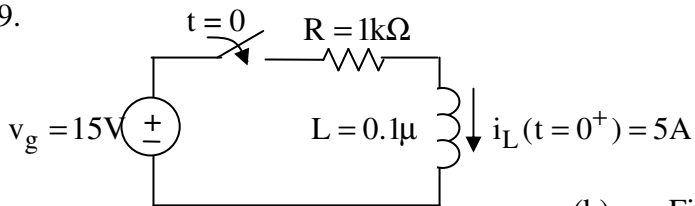

(a) Find an expression for $i_L(t)$ for $t \geq 0$.
Note: Assume the initial current in the L is created by circuitry not shown in the diagram.

(b) Find the energy stored in the inductor at time $t = 1\text{ms}$.

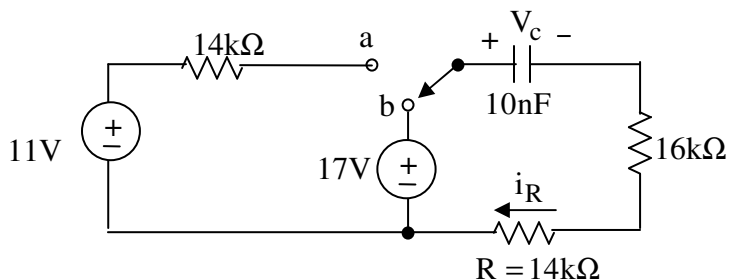10. The switch has been in a position a for a long time. It is switched to position b at $t = 0$.



(a) Find an expression for $V_C(t)$ for $t > 0$.

(b) Find the current, i_R , in R as a function of time.