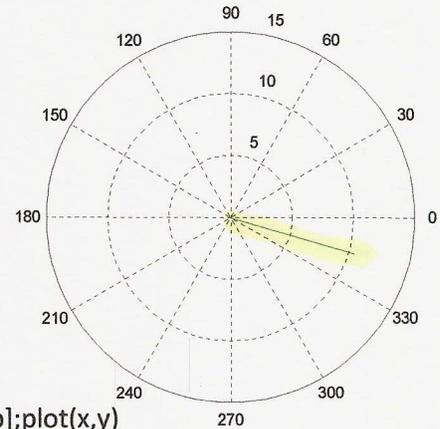




1. Plot each of the following complex numbers as vector in the complex plane:

a. $(10-3j)$ Matlab: `[t,r]=cart2pol(10,-3);theta=[0,t];rho=[0,r];polar(theta,rho)`





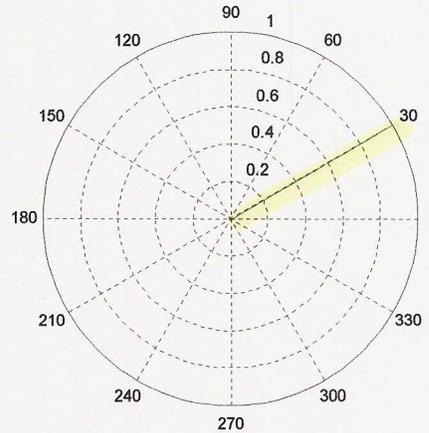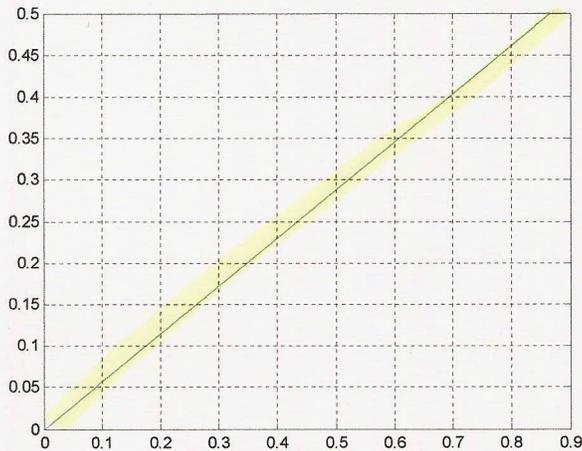b. $e^{j\pi/6}$ matlab: `[a,b]=pol2cart(pi/6,1); x=[0,a]; y=[0,b];plot(x,y)`

`theta=[0,pi/6];rho=[0,1];polar(theta,rho)`





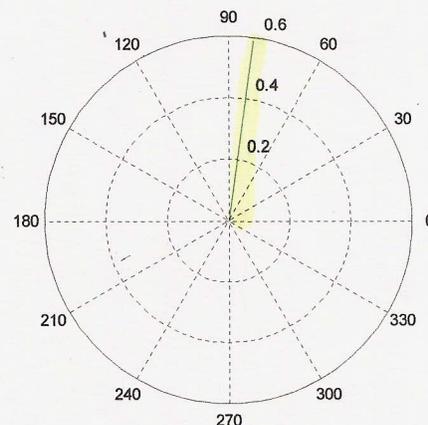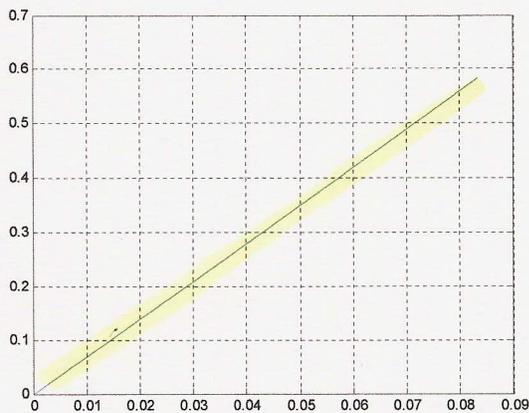c. $\frac{2+2j}{6} - \frac{1-j}{4} = 0.0833 + 0.5833j$ Matlab: `a=real(((2+2i)/6)-((1-i)/4));`
`b=imag(((2+2i)/6)-((1-i)/4));x=[0,a]; y=[0,b];plot(x,y)`
`[t,r]=cart2pol(0.08330,0.5833);theta=[0,t];rho=[0,r];polar(theta,rho)`





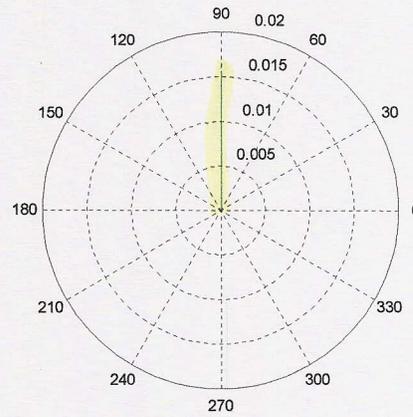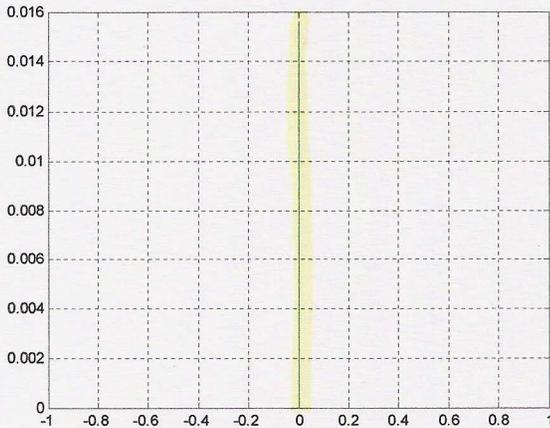d. $\frac{1}{4j^3}$ which equals $0 + 0.0156i$ Matlab: `a=real(1/(4i^3));b=imag((1/(4i^3)));x=[0,a];`
`y=[0,b];plot(x,y)`

`theta=[0,pi/2];rho=[0,0.0156];polar(theta,rho)`



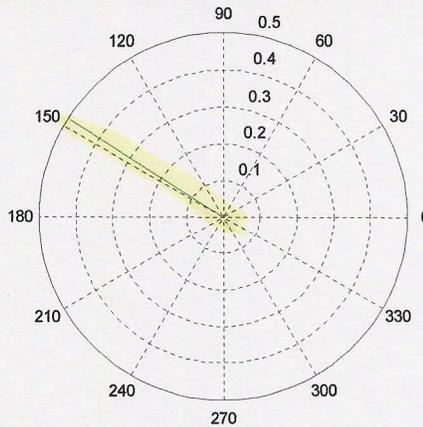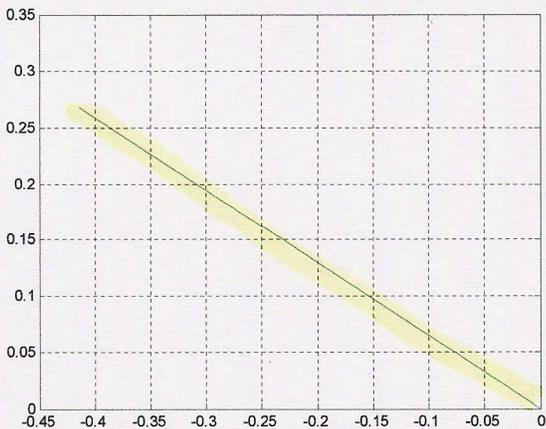e. $\frac{1-3j}{-5+4j}$ which equals $-0.4146 + 0.2683i$ Matlab: `a=real((1-3i)/(-5+4i));b=imag((1-3i)/(-5+4i));x=[0,a]; y=[0,b];plot(x,y)`
`[t,r]=cart2pol(-.4146,0.2683);theta=[0,t];rho=[0,r];polar(theta,rho)`



2. Give numerical answers to each of the following questions:

a. Rationalize $\frac{-30k \cdot (j1k)}{30k + j1k}$. Express your answer in rectangular form.

$$\frac{-30k \cdot (j1k)}{(30k + j1k)} \cdot \frac{(30k - j1k)}{(30k - j1k)} = \frac{-9e11j - 3e10}{30k^2 + 1e3^2} = -999j - 33$$

- b. Find the polar form of $(e^{j45^\circ})^* \left(\sqrt{1 + \frac{5}{4}} - j\sqrt{1 - \frac{5}{4}} \right)^*$ (Note: The asterisk means conjugate.)

$$(e^{-j45^\circ})(1.5 + 0.5j) = (e^{-j45^\circ})(1.58e^{j18.4^\circ}) = 1.58e^{-j26.6^\circ}$$

- c. Find the following phasor: $P[8 \sin(3kt + 115^\circ)] = P[8 \cos(3kt + 115^\circ - 90^\circ)]$
 $8e^{+j25}$

- d. Find the magnitude of $\frac{(1-4j)2e^{-j50^\circ}}{2+2e^{j90^\circ}}$.

$$\left| \frac{(\sqrt{1^2 + 4^2} e^{-j \tan^{-1}(-4/1)}) 2e^{-j50^\circ}}{2 + 2j} \right| = \left| \frac{(4.12 e^{-j76^\circ}) 2e^{-j50^\circ}}{2.83 e^{j45^\circ}} \right| = 2.9$$

- e. Find the imaginary part of $\frac{1-5j}{e^{-j60^\circ}}$.

$$\text{Im} \left[\frac{5e^{-j79^\circ}}{e^{-j60^\circ}} \right] = \text{Im} [5e^{-j19^\circ}] = 5 \sin(-19^\circ) = -1.6$$

3. a. Write phasors (as both $Ae^{j\phi}$ and $A\angle\phi$) for each of the following signals:

i. $v(t) = 18 \cos(5t + 80^\circ) \text{V} \Rightarrow 18e^{j80^\circ} \quad 18\angle 80^\circ$

ii. $i(t) = 4 \sin(\omega t + 143^\circ) \text{mA} \Rightarrow 4me^{j143^\circ} \quad 4m\angle 143^\circ$

iii. $v(t) = \cos(10t + 30^\circ) \text{V} + 7 \sin(10t - 30^\circ) \text{V} =$
 $e^{j30^\circ} + 7e^{-j120^\circ} = \cos(30) + \sin(30)j + 7 \cos(-120) + 7 \sin(-120)j = -2.6 - 5.6j = 6.1e^{-j115^\circ}$


- b. Given $\omega = 9 \text{krad/sec}$, write inverse phasors for each of the following signals:

i. $\mathbf{I} = 56.8e^{j37^\circ} \text{A} \Rightarrow 56.8 \cos(9kt + 37^\circ)$

ii. $\mathbf{V} = -5j^3 \text{V} \Rightarrow 5e^{j90^\circ} = 5 \cos(9kt + 90^\circ)$

iii. $\mathbf{I} = 3e^{+\frac{\pi}{2} - j63^\circ} = 3e^{+\frac{\pi}{2}} e^{-j63^\circ} \text{A} \Rightarrow 3e^{+\frac{\pi}{2}} \cos(9kt - 63^\circ)$

4.

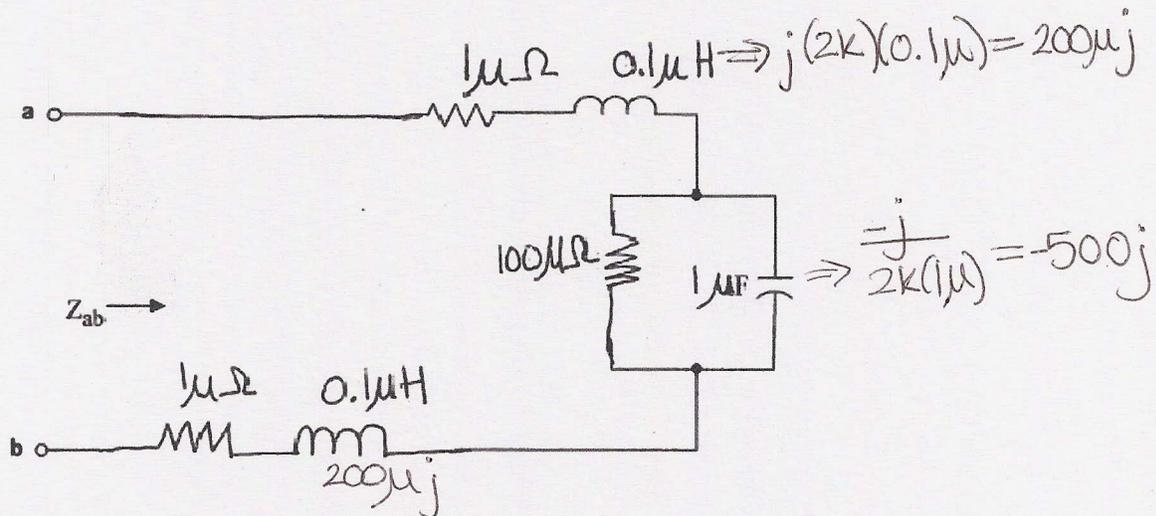Given $\omega = 2\text{k rad/sec}$, find Z_{ab} .



$$Z_{ab} = 1 \mu + 200 \mu j + (100 \mu \parallel -500 j) + 200 \mu j + 1 \mu = 0$$

$$2 \mu + 400 \mu j + \frac{100 \mu (-500 j)}{(-500 j + 100 \mu)} \cdot \frac{(100 \mu + 500 j)}{(100 \mu + 500 j)} =$$

$$= 2 \mu + 400 \mu j + \frac{-5 \mu j + 25 j^2}{100 \mu^2 + 500^2} = 2 \mu + 400 \mu j - 2 \text{m} j + 100 \mu$$

$$Z_{ab} = 102 \mu - 1.6 \text{m} j$$

5.

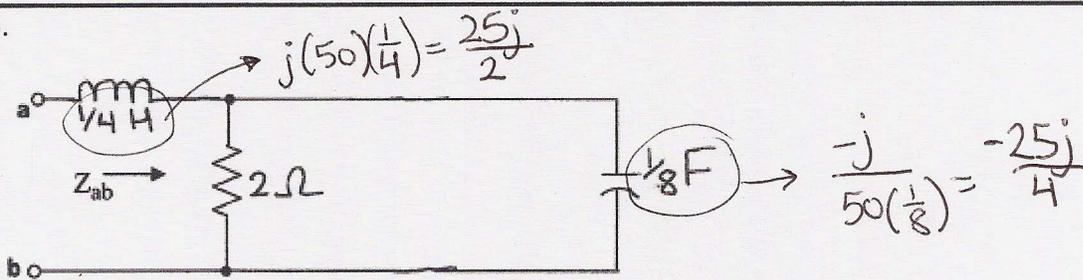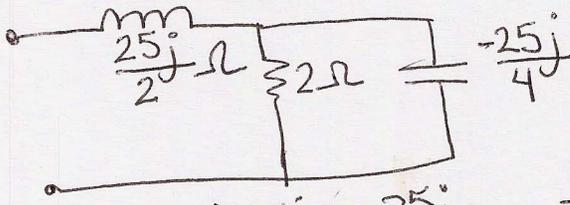Given $\omega = 50$ rad/sec, find Z_{ab} .

$$Z_{ab} = 2 \parallel -\frac{25j}{4} + \frac{25j}{2} = \frac{1}{\frac{1}{2} + \frac{-25j}{4}} + \frac{25j}{2} = \frac{4}{2-25j} + \frac{25j}{2}$$

Rationalizing:


$$Z_{ab} = \frac{4(2+25j)}{4+25^2} + \frac{25j}{2} = \frac{2(8+100j)}{2(629)} + \frac{25j(629)}{2(629)} = \frac{16+15925j}{1258}$$

$$Z_{ab} \approx 12.7m + 12.7j$$

6.

$$i_s(t) = 10 \cos(2t) \text{ A}$$

$$\begin{aligned} I_s &= 10 e^{j0^\circ} \\ &= 10 \angle 0^\circ \\ &= 10 \end{aligned}$$

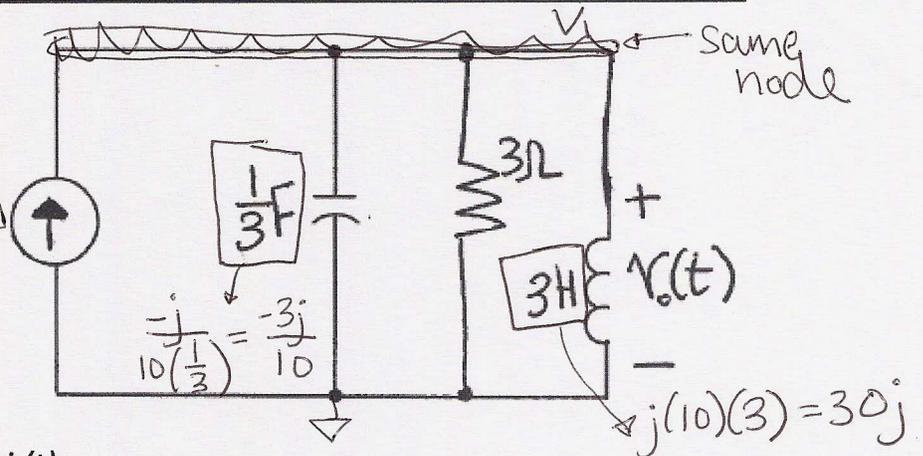a. Find the phasor value for $i_s(t)$.b. Draw the frequency-domain circuit diagram, including the phasor value for $i_s(t)$ and the impedance values for components.7. Find the phasor value for $V_o(t)$ from the circuit in Problem 6.

$$V_i = V_o(t)$$

$$-10 + \frac{V_i(10)}{-3j} + \frac{V_i}{3} + \frac{V_i}{30j} = 0$$

Use common-denominator of $30j$


$$-\frac{V_i(10)(10)}{30j} + \frac{V_i(10j)}{30j} + \frac{V_i}{30j} = 10$$

$$V_i \left(\frac{-1000}{30j} + \frac{10j}{30j} + \frac{1}{30j} \right) = 10$$

$$V_i \left(\frac{-999 + 10j}{30j} \right) = 10 \Rightarrow V_i = \left[\frac{10(30j)}{-999 + 10j} \right]$$

$$V_i = \frac{10(30j)}{\sqrt{999^2 + 10^2}} e^{\tan^{-1}(-\frac{10}{999})} = \frac{300j}{999} e^{-j0.6} = 0.3 e^{j90.6} = V_o$$

8.

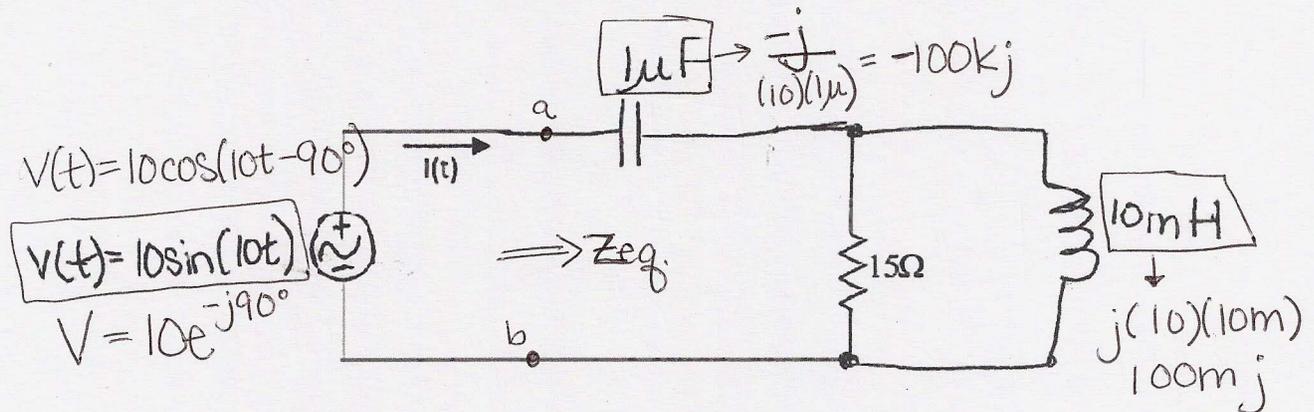

- Find the phasor value for $V(t)$.
- Draw the frequency-domain circuit diagram, including the phasor value for $V(t)$ and the impedance values for components.

9. Find the phasor value for $i(t)$ for the circuit in Problem 8.

$$I = \frac{V}{Z_{eq}}$$


$$Z_{eq} = -100kj + 15 \parallel 100mj = -100kj + \frac{15(100mj)}{15 + 100mj}$$

$$Z_{eq} = -100kj + \frac{15(100mj)(15 - 100mj)}{15^2 + 100m^2} = \frac{22.5j + 150m}{225 + 10m} - 100kj$$

$$Z_{eq} \approx 100mj - 100kj + 667\mu \approx -100kj$$

$$\therefore I = \frac{10e^{-j90^\circ}}{+100ke^{j90^\circ}} = 100\mu A$$

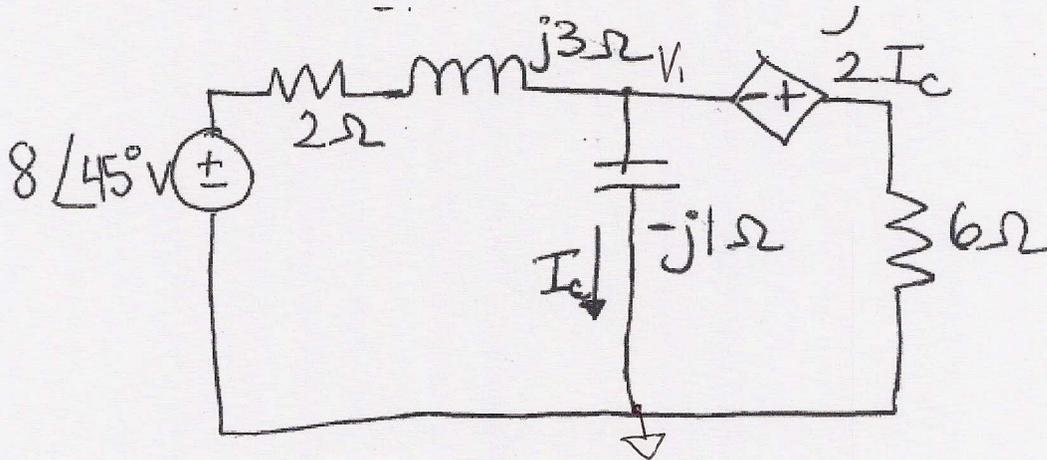10. Determine I_c for the following circuit. Write the answer in phasor form.



Using node-voltage :

$$\frac{V_1 - 8e^{j45^\circ}}{2+3j} + \frac{V_1}{-j} + \frac{V_1 + (+2I_c)}{6} = 0 \quad \text{where } I_c = \frac{V_1}{-j} = V_1 j$$

$$V_1 \left(\frac{1}{2+3j} + j + \frac{1}{6} + \frac{2j}{6} \right) = \frac{8e^{j45^\circ}}{2+3j}$$

$$V_1 \left(\frac{6 + (2+3j)j6 + (2+3j) + 2j(2+3j)}{6(2+3j)} \right) = \frac{8e^{j45^\circ}}{(2+3j)}$$

$$V_1 \left(\frac{6 + 12j + 18j^2 + 2+3j + 4j + 6j^2}{6(2+3j)} \right) = \frac{8e^{j45^\circ}}{(2+3j)}$$

$$V_1 \Rightarrow \left(\frac{-16+19j}{6(2+3j)} \right) V_1 = \frac{8e^{j45^\circ}}{(2+3j)} \frac{6(2+3j)}{-16+19j}$$

$$V_1 = \frac{8e^{j45^\circ}}{\sqrt{16^2+19^2} e^{j \tan^{-1} \left(\frac{19}{-16} \right)}}$$

$$I_c = V_1 j \cong \frac{8e^{j45^\circ}}{25e^{-j50^\circ}} = \boxed{0.32e^{j95^\circ}}$$