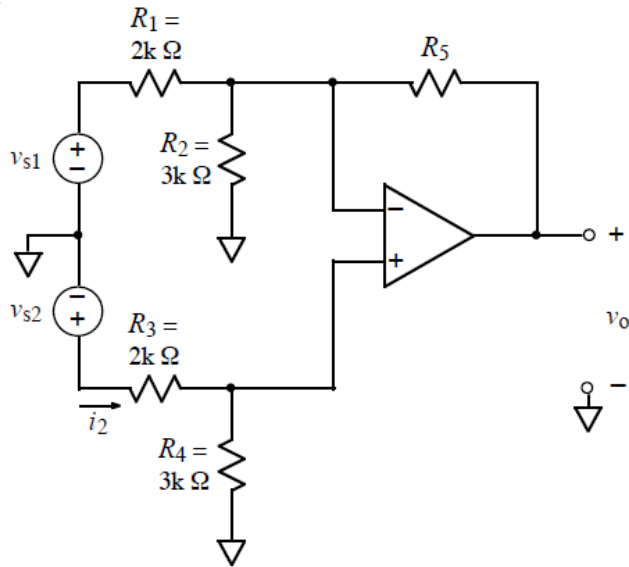


(Each problem is worth double points)

1.





The above circuit operates in linear mode. Derive a symbolic expression for v_o . The expression must contain not more than the parameters v_{s1} , v_{s2} , R_1 , R_2 , R_3 , R_4 , and R_5 .

2. Using the solution for Problem 1: if $v_{s1} = 0$ V and $v_{s2} = 1$ V, find the value of R_5 that will yield an output voltage of $v_o = 1$ V.
3. Using the circuit in Problem 1: Find the numerical value of the circuit's input resistance, R_{in} , as seen by source v_{s2} . In other words, write a formula for voltage, v_{s2} , divided by i_2 :

$$R_{in} \equiv \frac{v_{s2}}{i_2}$$


Write R_{in} in terms of not more (and possibly less) than R_1 , R_2 , R_3 , R_4 , and R_5 .

4.

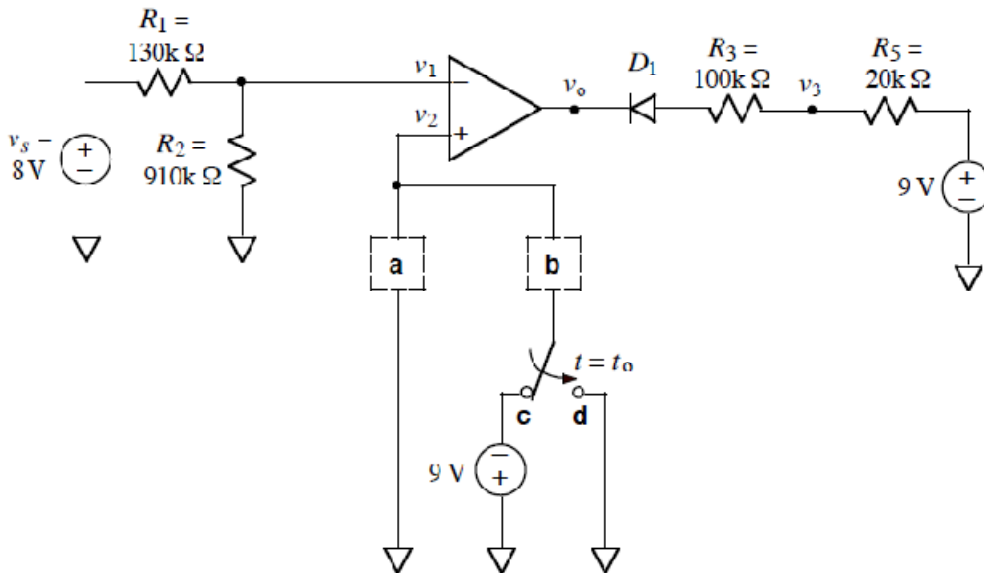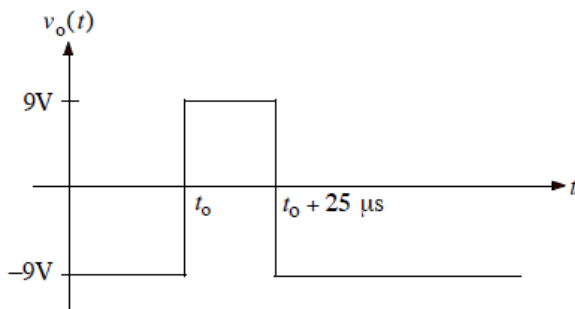Rail Voltages= ± 9 After being at c for a long time, the switch moves to d at time $t = t_0$.

- a) Choose either an R or C to go in box **a** and either an R or C to go in box **b** to produce the $v_o(t)$ shown above. Use at least one R , and use $2\text{ k}\Omega$ for the R value or values. Also, note that v_o stays low forever after $t_0 + 25\ \mu\text{s}$. Specify which element goes in each box and its value.
- Sketch $v_1(t)$, showing numerical values appropriately.
 - Sketch $v_2(t)$, showing numerical values appropriately.
 - Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 25\ \mu\text{s}$, and for $t > t_0 + 25\ \mu\text{s}$. Use the ideal model of the diode: when forward biased, its resistance is zero, (a wire); when reverse biased, its resistance is infinite, (an open).


8.

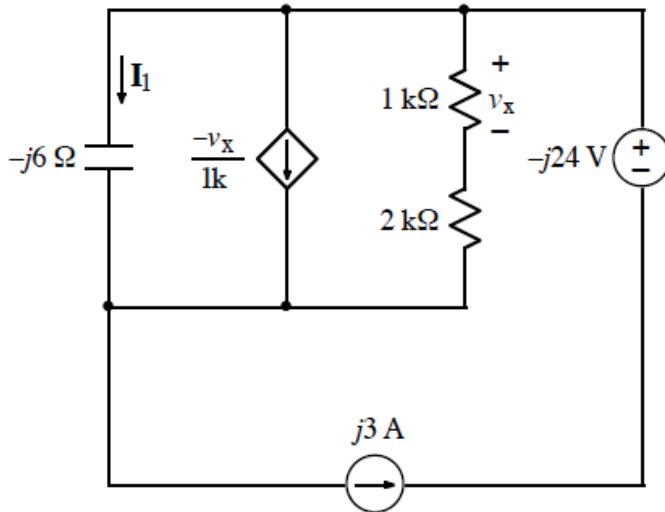

A frequency-domain circuit is shown above. Write the value of phasor current \mathbf{I}_1 in rectangular form.

9. Given $\omega = 25\text{k rad/s}$, write a numerical time-domain expression for $i_1(t)$, the inverse phasor of \mathbf{I}_1 .

10.

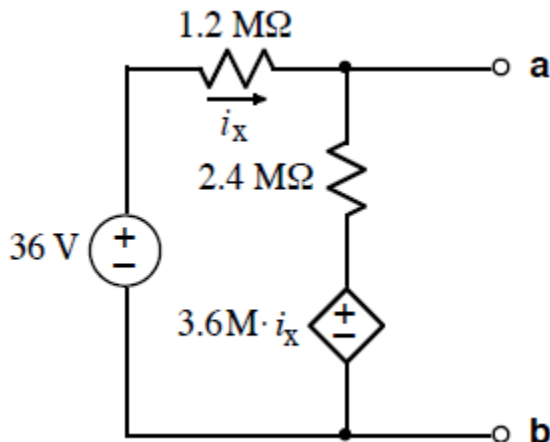

(a) If we attach R_L to terminals **a** and **b**, find the value of R_L that will absorb maximum power.

(b) Calculate the value of that maximum power absorbed by R_L .