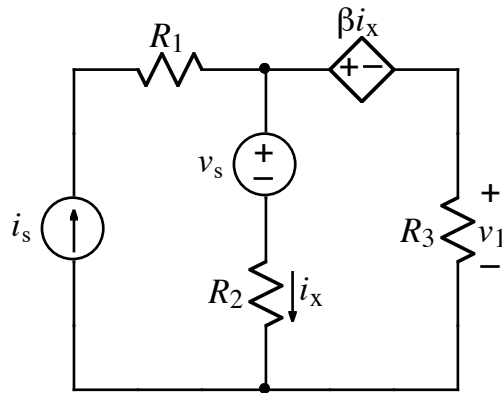



Ex:




Using superposition, derive an expression for  $v_1$  that contains no circuit quantities other than  $i_s$ ,  $v_s$ ,  $R_1$ ,  $R_2$ ,  $R_3$ , and  $\beta$ , where  $\beta > 0$ .

Sol'n: We turn on one independent source at a time. (We never turn off independent sources, since they act like R's.)

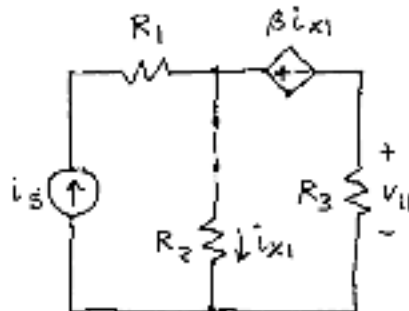case I:  $i_s$  on,  $v_s$  off (v src off = wire)



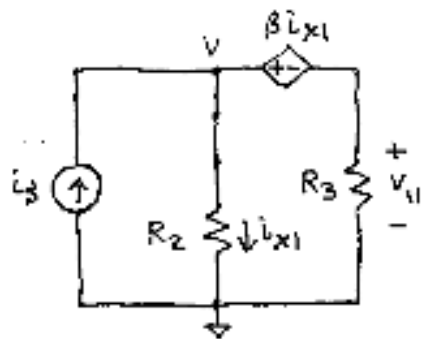Note: Since  $R_1$  is in series with a current source and the problem does not ask about  $i$  or  $v$  for  $R_1$ , we may ignore  $R_1$  and replace it with a wire.



We add a reference and use the node- $v$  method:

$$-i_s + \frac{v}{R_2} + \frac{\left(v - \beta \frac{v}{R_2}\right)}{R_3} = 0A$$

$$v \left( \frac{1}{R_2} + \frac{1}{R_3} - \frac{\beta}{R_2 R_3} \right) = i_s$$

$$v = \frac{i_s}{\frac{1}{R_2} + \frac{1}{R_3} - \frac{\beta}{R_2 R_3}} = i_s \cdot R_2 \parallel R_3 \parallel \left( \frac{-R_2 R_3}{\beta} \right)$$

For  $v_{11}$ , we use  $v$  and the dependent src


$$v_{11} = v - \beta \frac{v}{R_2} = v \left( 1 - \frac{\beta}{R_2} \right)$$

$$v_{11} = i_s \cdot R_2 \parallel R_3 \parallel \left( \frac{-R_2 R_3}{\beta} \right) \cdot \left( 1 - \frac{\beta}{R_2} \right)$$


With some effort doing algebra, this may also be written as follows:

$$v_{11} = i_s \cdot (R_2 - \beta) \parallel R_3$$

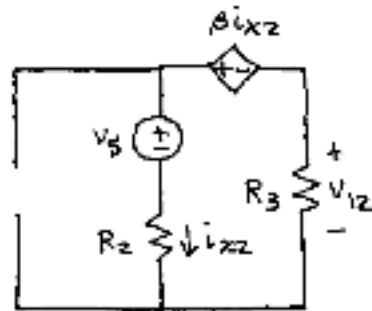case II:  $i_s$  off ( $i_s$  src off = open),  $v_s$  on




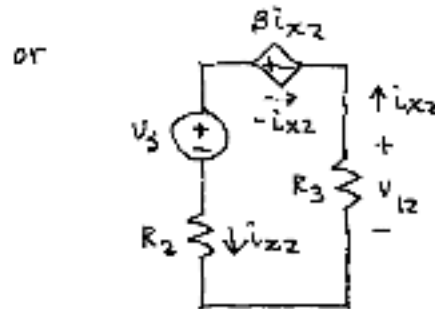Again, we may ignore  $R_1$  in series with  $i_s$  src.



Here, we may replace the dependent source with an  $R_{eq} = v/i =$

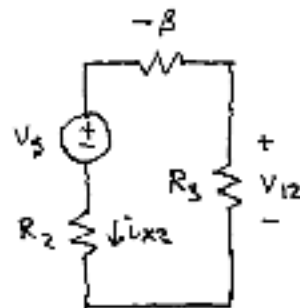
$$R_{eq} = \frac{\beta i_{x2}}{-i_{x2}} = -\beta$$




Now we use a v-divider:

$$v_{12} = v_s \cdot \frac{R_3}{R_2 - \beta + R_3}$$

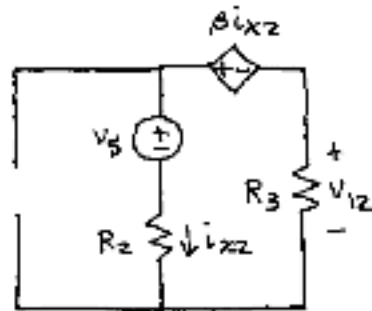case II:  $i_s$  off ( $i_s$  src off = open),  $v_s$  on




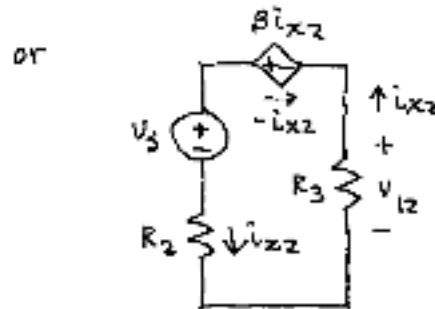Again, we may ignore  $R_1$  in series with  $i_s$  src.




Here, we may replace the dependent source with an  $R_{eq} = v/i =$
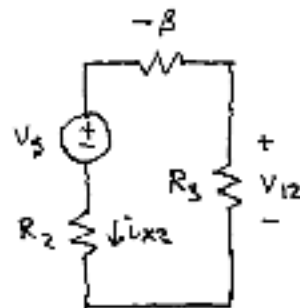
$$R_{eq} = \frac{\beta i_{x2}}{-i_{x2}} = -\beta$$



Now we use a v-divider:

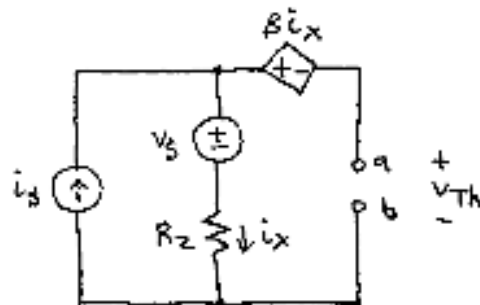
$$v_{12} = v_s \cdot \frac{R_3}{R_2 - \beta + R_3}$$



Now we use superposition or any other method of our choosing to find  $V_{TH}$ . As always,  $V_{TH}$  equals the open circuit voltage from a to b.

Here, we use superposition as directed in the problem.


case I:  $i_s$  on,  $v_s$  off = wire

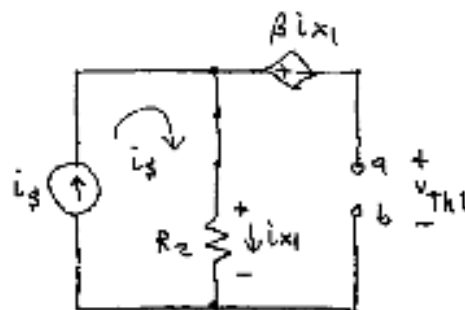

We observe that  $i_{x1} = i_s$ , and  
 $V_{TH1} = i_{x1} R_2 - \beta i_{x1} = i_s (R_2 - \beta)$

(This is significantly simpler than the earlier superposition approach. There is more to be done before we are finished here, however.)

case II:  $i_s$  off = open,  $V_s$  on

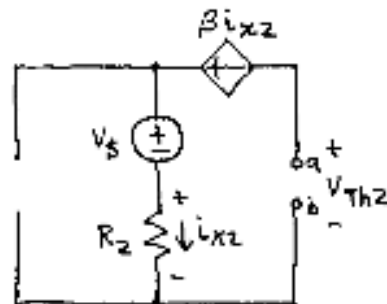

Here,  $i_{x2} = 0$  since there is no complete circuit. Thus, we 0V across  $R_2$  and across the dependent source. It follows (from a v-loop on the right side) that

$$V_{Th2} = V_s$$


Summing results, we have

$$V_{Th} = V_{Th1} + V_{Th2} = i_s(R_2 - \beta) + V_s$$

To find  $R_{Th}$ , we turn off independent sources and attach a 1V source to a, b. We measure the current,  $i_a$ , flowing into the 'a' terminal and use Ohm's law:

$$R_{Th} = \frac{1V}{i_a} \quad (\text{independent src's off})$$

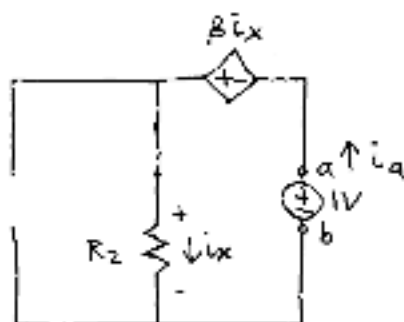Note: this method simplifies calculations for circuits with multiple independent sources.



From v-loop on the right side, we have

$$i_x R_2 - \beta i_x - 1V = 0V$$

$$\text{or } i_x = \frac{1V}{R_2 - \beta}$$


We also have that  $i_x = i_a$ .

$$\text{Thus, } i_a = \frac{1V}{R_2 - \beta}$$


and

$$R_{Th} = \frac{1V}{i_a} = \frac{1V}{\frac{1V}{R_2 - \beta}} = R_2 - \beta$$

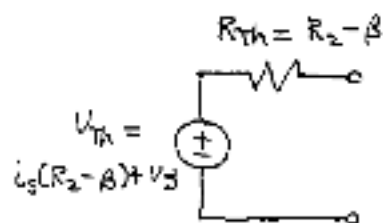Our Thevenin equivalent without  $R_3$  is



Now we add  $R_3$  and find  $V_1$ :

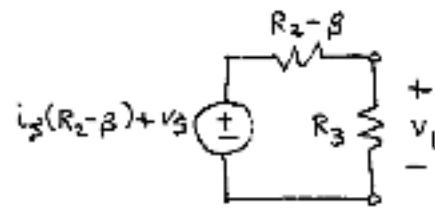

$$v_1 = \left[ i_2 (R_2 - \beta) + v_3 \right] \frac{R_3}{R_2 - \beta + R_3}$$

This is the same result as earlier  
but with dramatically less algebra.