

1.    a)  $\frac{251}{325} - j\frac{207}{325}$   
      b)  $\sqrt{2} - j\sqrt{2}$   
      c)  $6\sqrt{2} \cos(40^\circ) \cos(9t + 45^\circ)$   
      d)  $\frac{1}{17}$   
      e) -10
2.     $L$
3.     $L = 9 \text{ mH}$
4.    Draw circuit diagram with following values:  
phasor  $\mathbf{I}_s = 7\angle 30^\circ \text{ A}$ ,  $-j1250 \Omega$  (C),  $j40 \Omega$  (L),  $30 \Omega$  (R), current arrow labeled  $\mathbf{I}_x$ ,  
dependent source labeled  $15\mathbf{I}_x$ .
5.     $\mathbf{V}_{Th} = 21\sqrt{73}\angle 46.3^\circ \text{ V} \approx 124 + j129.7 \text{ V}$   
 $z_{Th} = 3\sqrt{73}\angle 16.3^\circ \Omega = 24.6 + j7.2 \Omega$