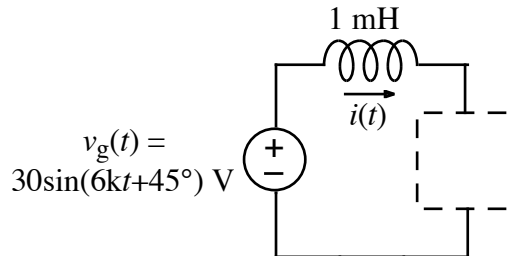


Ex:



- Choose an R, an L, or a C to be placed in the dashed-line box to make $i(t) = 0.5 \cos(6kt - 135^\circ)$ A.
- State the value of the component you chose for Problem 2. Note that the value of the component cannot be negative.


sol'n: We first transform the circuit to the frequency domain.

$$V_g = 30 \cdot (-j) \cdot 1 \angle 45^\circ = 30 \angle 45^\circ - 90^\circ = 30 \angle -45^\circ$$

$$\text{Note: } -j = 1 \angle -90^\circ$$

$$j\omega L = j6k \cdot 1\text{mH} = j6 \Omega$$
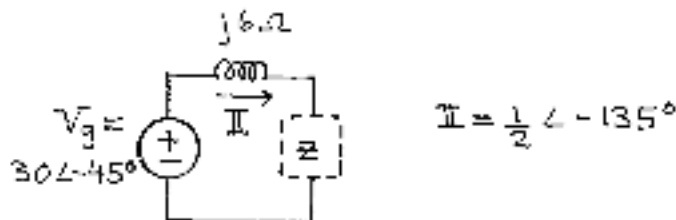
$$I = \frac{1}{2} \angle -135^\circ \text{ A}$$



$$\text{By Ohm's law, } I = \frac{V_g}{Z + j6 \Omega}$$

$$\text{or } z + j6\Omega = \frac{V_g}{\mathbb{I}}$$

We could solve for z directly in this case, but it is instructive to solve the problem using phase and magnitude separately.

$$\angle(z + j6\Omega) = \angle V_g - \angle \mathbb{I}$$

$$\text{Notes: } \angle\left(\frac{V_g}{\mathbb{I}}\right) = \angle V_g - \angle \mathbb{I}$$

$$\angle(z + j6\Omega) = -45^\circ - (-135^\circ) = 90^\circ$$

We conclude that $z + j6\Omega$ must be purely imaginary and positive.

This means that z might be an L or a C. If it is a C, however, it must be large enough that z is smaller in magnitude than $j6\Omega$.

In either case, (L or C), we can write

$$z + j6\Omega = jk$$

where k is a positive constant.

Now we consider magnitude.

$$|z + j6\omega| = \left| \frac{V_3}{\mathbb{I}} \right| = \frac{|V_3|}{|\mathbb{I}|} = \frac{30}{\frac{1}{2}} = 60$$

Since we know $z + j6 = jk$, we have

$$|z + j6| = k = 60$$

$$z = j60 - j6 = j54$$

We must use an L to get a positive imaginary z :

$$z = j\omega L = j \cdot 6k \cdot L = j54$$

$$L = \frac{54}{6k} = 9 \text{ mH}$$