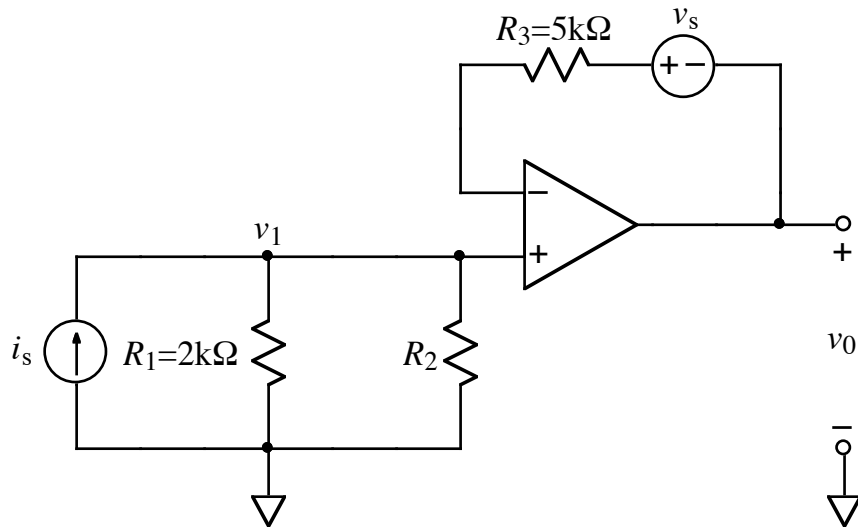


Ex:



Rail voltage = ± 9 V

- The above circuit operates in linear mode. Derive a symbolic expression for v_0 . The expression must contain not more than the parameters i_s , v_s , R_1 , R_2 , and R_3 .
- If $v_s = 0$ V, find the value of R_2 that will yield an output voltage of $v_0 = 1$ V when $i_s = 1$ mA.
- Using the value of R_2 from part (a), find the value of v_s that will yield $v_0 = 1$ V when $i_s = 0$ A.
- Using the value of R_2 from part (a), calculate the input resistance, $R_{in} = v_1/i_s$, seen by the i_s source.

sol'n: a) First, we find the voltage, v_1 , at the + input of the op-amp.

$$v_1 = i_s \cdot R_1 \parallel R_2$$

Second, we assume the voltage, v_n , at the - input of the op-amp = v_1

$$V_n = i_s \cdot R_1 \parallel R_2$$

Third, we find the value of V_o that yields the above value of V_n .

Since no current flows into the op-amp inputs, no current flows in R_3 , and R_3 has no voltage drop.

$$\therefore V_o = V_n - V_s$$

$$\text{or } V_o = i_s \cdot R_1 \parallel R_2 - V_s$$

- b) Given $V_s = 0V$ and $i_s = 1mA$ we are to find the value of R_2 that yields $V_o = 1V$.

Using the expression in (a) for V_o we have

$$1V = 1mA \cdot 2k\Omega \parallel R_2 - 0V$$

$$\text{or } 2k\Omega \parallel R_2 = 1k\Omega$$

$$\text{or } R_2 = 2k\Omega$$

- c) We have $1V = 0A \cdot \cancel{2k\Omega} \parallel 2k\Omega - V_s$ ^{0V}

$$\text{or } V_s = -1V$$

d) From part (a), we have the following:

$$v_1 = i_5 \cdot R_1 \parallel R_2$$

$$R_{in} \equiv \frac{v_1}{i_5} = R_1 \parallel R_2 = 1k\Omega$$